

**LECTURE NOTE ON
SWITCH GEAR & PROTECTIVE DEVICE
6TH SEM ELECTRICAL ENGINEERING**

Prepared By
Er. Sachin Kumar Satpathy
(Lect. In Electrical Engg.)
B.I.T ,SAMBALPUR

CH-01.

* Introduction to Switch gear:-

- Now a days there is a great requirement of electric energy in lighting, Heating, Domestic appliances, Industrial electrical machinery and electric traction.
- The importance of electric supply in every day life has reached in such a stage that it is desirable to protect the power system from harm during fault condition and maintain continuity of supply.
- For this purpose means Switch (ON) or (OFF) generator, transmission line, distributor and other equipments under both normal and abnormal condition, the switch gear components are highly necessary; So a switch gear essentially consist of switching and protecting devices such as (Switch, fuses, Circuit Breaker, relays, etc.).
- During normal operation switch gear permits to switch ON or OFF generator, transmission lines, distributor and other electrical equipments.
- On the other hand when failure occurs in part of the power system a heavy current flow through the equipments causing interruption of service to the consumer.
- However the switch gear detect the fault & disconnects the unhealthy portion or section from the system and maintain continuity of supply to other part of the system.
- Normally the switch gear apparatus are used for switching controlling and protecting the electrical circuit and equipments.

IMP

* Essential features of Switch gear:-

① COMPLETE RELIABILITY →

- When fault occurs on any section or part of the power system

The switch gear must operate ~~to~~ isolate the faulty section from healthy section, so with continued trend of interconnection and increasing capacity of generating station there is need of reliable of switch gear but very important.

② ABSOLUTE CERTAIN DISCRIMINATION →

→ When fault occur on any section of the power system the switch gear must be able to discriminate between the faulty section & healthy section. It should isolate the faulty section from the system without affecting healthy section which ensure continuity of a supply.

③ QUICK OPERATION (as fast as possible) →

→ When fault occurs on any part of the power system the switch gear must operate quickly so that no damage is done to generator, transformer and other power equipments due to short circuit currents. If fault is not clear by switch gear quickly it might spread into healthy parts and cause complete shutdown of system.

④ PROVISION FOR MANUAL CONTROL →

→ A switch gear must have provision for manual control in case of automatic control fails, then the necessary operations can be carried out by manually.

⑤ PROVISION FOR INSTRUMENTS →

→ There must be provision for instruments which may be required. The instruments may be ammeter, voltmeter, frequency meter, etc. for indicate proper line parameters.

* Switch Gear Equipments:-

→ Switch gears are the equipments used for switching and interrupting current under normal & abnormal condition.

→ It includes switch, fuse, circuit breaker, relays & other equipments.

* Switch → These are the device which are used for open or close an electrical circuit in a conventional way but can't interrupt the circuit during fault condition.

→ There are different types of switch like air switch, oil switch, isolator.

* Fuse → It is a short piece of wire or thin strip which melts when excessive current flows through it for a sufficient time.

→ It is inserted in series with the circuit to be protected.

→ Under normal operating condition it takes normal current or normal load current without over heating.

→ However when short circuit or overload occurs the current through the fuse element reaches it beyond its capacity and melts the fuse element disconnecting the circuit from the main current after clearing of fault the fuse again re-usable.

not used
Doubt
10/10/19

* Circuit Breaker:-


→ A CB is an equipment which can open or close a circuit under all conditions i.e. No-load, full-load & fault condition.

→ It can be designed or created manually or automatically under fault condition.

→ A CB essentially consists of fixed & moving contacts enclosed inside a metal tank and emerged with Oil, Air, gas (SF6).

* Relay: A relay is a device which detect the faults and supplies information to the breaker for act interruption.

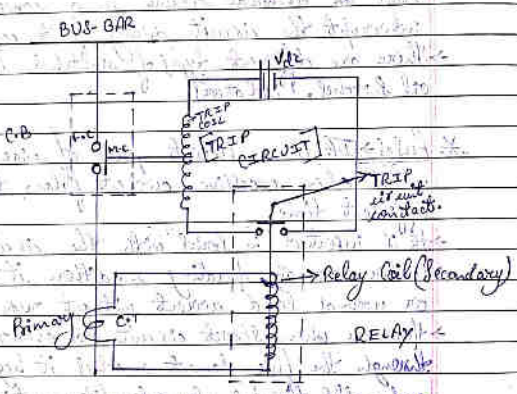→ The typical diagram shows the relay protection scheme of a BUS-Bar.



→ Under normal load condition the emf of the secondary winding of C.T is small and current flowing through the relay operating coil (C.T secondary) is insufficient to close the relay contacts; so TRIP circuit remain unenergized. when fault occur a large current flows through the primary of the C.T, this in crease the secondary emf and current through the relay operating coil is high.

→ The relay coil get energized enough to pull the trip circuit contact. Now, trip act get energized and tripping coil pull the circuit breaker (C.B) moving contact (M.C).
→ Hence, the ~~busbar~~ causing disconnected of BUS-Bar from the main circuit.

TRIP


* BUS-BAR arrangements: When a no. of generators are feed out operating at the same voltage and directly connected electrically, ~~the~~ BUS-BAR'S are used as the common electrical component.

→ The BUS-BAR'S are copper-rod or thin wall-tube & operated at constant voltage.
→ There are different BUS-BAR arrangement systems as follows:
(a) Single BUS-BAR arrangement.
(b) Single BUS-BAR arrangement with sectionalisation.
(c) Duplicate BUS-BAR system.

→ All the diagram's of BUS-BAR arrangement are 3-phase but are shown in single-line for simplicity.

TRIP

① Single BUS-BAR arrangement:-

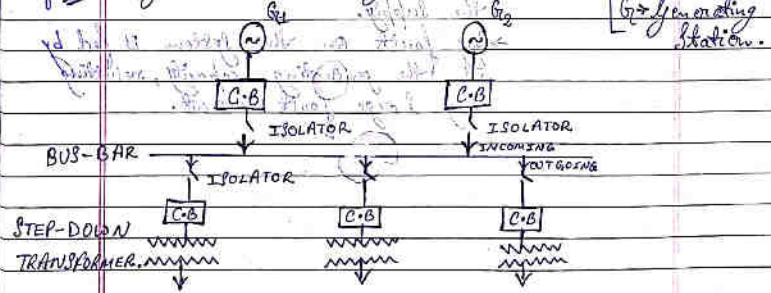

→ The single BUS-BAR system has the simplest design and is used for small outdoor sub-station where few outgoing or incoming feeders are found.

→ The generator, outgoing feeder, and transformer are connected to the BUS-BAR.

→ Each of its components is controlled by a circuit breaker (C.B).


→ The isolator permit to isolate generator, feeders & transformers manually during maintenance.

Advantages → Simple in construction.
 → Less initial cost & less maintenance.
 → Simple in operation.


Disadvantages → The BUS-BAR cannot be cleaned, repaired and tested without de-energizing the whole system.

→ If a fault occurs in the BUS-BAR itself there is a complete interruption of the supply.

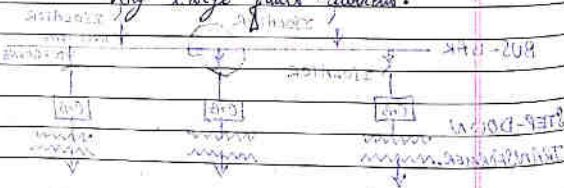→ Any fault on the system is fed by all the generating capacity, resulting very large fault current.



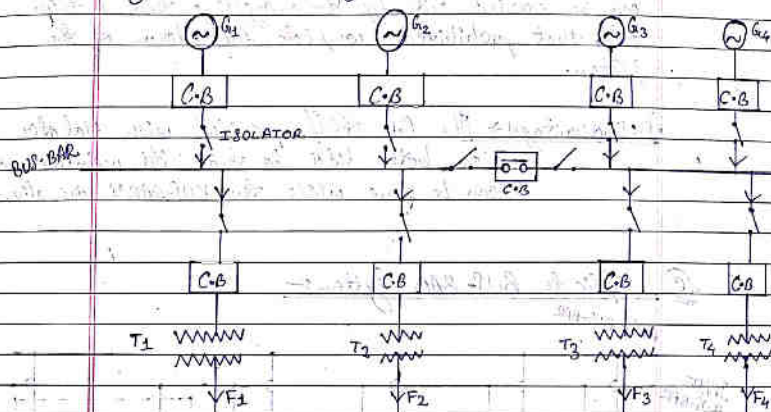(D) Single BUS-BAR arrangement with sectionalisation:



→ In large generating station where several units are installed, it is a common practice to sectionalise the BUS so that fault on any section of the BUS-BAR will not cause complete shut-down.

→ The BUS-BAR is divided into sections connected by a C.B & isolator.


Advantages → If a fault occurs in any section of the BUS-BAR that section can be isolated without affecting the other sections.

→ Feeder (F) → If fault occur in any feeder, the fault current is lower than in sectionalised BUS-BAR system which permit use of lower rating C.B.

→ Repair & maintenance of any section of the BUS-BAR can be carried out by de-energizing that section only that prohibited complete shut-down of the system.

Disadvantage → The C.B. itself provided with isolator on both side so that its maintenance can be done while the BUS-BAR'S are alive.

② Duplicate BUS-BAR System :-

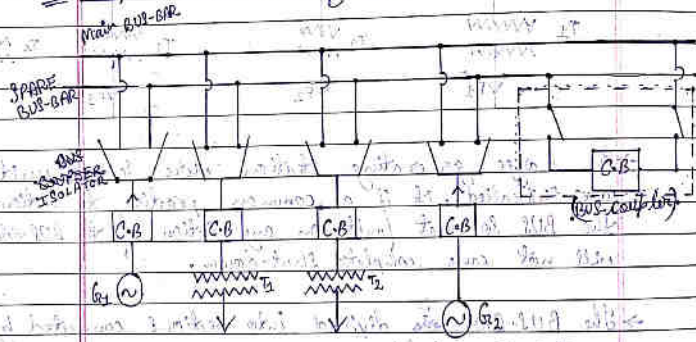

→ In large station where there is importance of continuity of supply & not interfere by break-down & maintenance of bus-bar, in order to achieve this we used Duplicate BUS-BAR System.

→ In this system we found 2 BUS-BAR named as Main BUS-BAR & Spare BUS-BAR.

→ Each generator and feeder may be connected on either BUS-BAR by the help of BUS-Coupler which consists of C.B. and Isolator.

→ In this scheme of BUS-BAR arrangement circuit interrupted during switch-over from one BUS to another.

Advantage → Repair & maintenance carried out in main bus-bar need not be interrupted entire load and transfer to spare-bus.

→ Testing of feeder, C.B. can be done by putting them on spare-bus, causing main-bus undisturbed.

→ If fault occur on the bus-bar the continuity of the supply can be maintain by transferring all load to spare-bus.

$$V = IR$$

$$I = \frac{V}{R}$$

$$R = \frac{V}{I}$$

$$P = VI$$

$$P = I^2 R$$

$$P = \frac{V^2}{R}$$

$$R = \frac{V^2}{P}$$

$$R = \frac{V^2}{P}$$

$$R = \frac{V^2}{P}$$

$$R = \frac{V^2}{P}$$

$$R = \frac{V^2}{P}$$

$$R = \frac{V^2}{P}$$

$$R = \frac{V^2}{P}$$

$$R = \frac{V^2}{P}$$


$$R = \frac{V^2}{P}$$

$$R = \frac{V^2}{P}$$

$$R = \frac{V^2}{P}$$

* Short Circuits

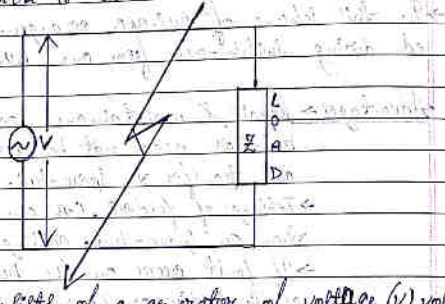→ Whenever a fault occur on a network such that a large current flow in one or more lines [or phases] then the condition is called short ckt condition.



Let,
 A ckt consists of a generator of voltage (V) volt having internal impedance (Z_i) & load of (Z).
 → Under normal operating condition the current in the circuit is limited by internal impedance (Z_i) & load impedance (Z) i.e. $I = \frac{V}{Z + Z_i}$.

→ If any fault occurs across the load terminals and get shorted at that time the load impedance [$Z = 0$] and (Z_i) value is very small.

→ Hence, a large short ckt current starts flowing in the circuit that is also called as ~~over load~~ short circuited.

→ On the other hand in an over load case if load greater than design value of the system, the voltage near over load point is zero. Hence, the current in the over load equipment are substantially high.

Causes - Internal Effect

→ The internal effects are cause by breakdown of equipments or transmission lines, deterioration of insulation of generator, etc.
 → Such troubles may be due to edging of insulation, inadequate design or improper insulation.

- External Effect

→ The external effect causing due to insulation failure cause due to lightning surges, overloads of equipment causing heating excessive, mechanical damage by public, etc.

Effect of SC - When Short Circuit occurs the current in the system increase to an abnormal high value and the system voltage also reduce to a low value.

→ Due to this heavy current excessive heat is produced in the system & may result fire explosion.

→ Sometimes the short circuit takes of an "Arc" causes considerable damage of system.

→ The low voltage created due to short circuit and remain for a few seconds, the consumer loads may shut down and a unstable condⁿ created across the power system.

* Fault in a Power System :-

- A fault occurs when two or more conductors that normally operated at different potentials come in contact with each other.
- This may be due to sudden failure of a piece of equipment, accidentally damage, insulation failure, ageing effect, lightning, surge, etc.
- So the fault in a 3φ system is divided into 2 types;
 - Symmetrical fault.
 - Unsymmetrical fault.

①. Unsymmetrical fault → Those fault which give rise to unsymmetrical fault current i.e. unequal line current and unequal phase displacement.

• Ex → Single line to ground, line to line fault, double line to ground.


CH-02.

* Symmetrical fault → Those fault on the power system which give symmetrical fault current i.e. equal fault current, equal displacement in each line. (120° displacement).

• Ex → Line to line to line fault (LLL).


→ The symmetrical fault occur when all the 3 conductors of a 3-φ line brought together simultaneously into a short circuit condition.

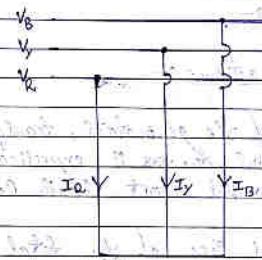→ This type of fault give rise to symmetrical fault current which is 120° apart from each other.



- The symmetrical fault rarely occurs in practice, the majority of the faults are unsymmetrical.
- The symmetrical fault is most severe & imposes more heavy duty on circuit breaker.

Date 14/04/2019

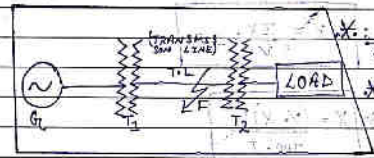

* Symmetrical fault Calculation :-
* Limitation of fault currents :-

- When short circuit occurs at any point of the system the short circuit current is limited by the impedance of the system upto point of fault.
- In the above diagram, if fault occur at F (fault) then the short circuit current of the G.S (generating station) will have value limited by impedance of generator, transformer & transmission line upto point of fault.
- So we have proper knowledge about impedance of various equipments & circuits for determination of SC current.

* Different terms:-

* Percentage of Reactance:-

→ The reactance of the generator, transformer, transmission line and reactor, etc. are expressed in percentage of reactance for rapid short circuit calculation.

→ So it is defined as %age of the total phase voltage drop in the circuit when full-load current is flowing through it.

Let X = reactance of the system in Ω per phase.
 I = full-load current.
 V = phase voltage of the system.

So, $\%X = \frac{IX}{V} \times 100$

$X = \frac{(\%X)V}{100 \cdot I}$

$X = \frac{(\%X) \cdot V \cdot V}{100 \cdot V \cdot I}$

$X = \frac{(\%X) \times \frac{V}{1000} \times \frac{V}{1000} \times 1000}{100 \times V \cdot I}$

$X = \frac{(\%X)(KV)^2 \cdot 10}{1000 KVA}$

$X = \frac{(\%X)(KV)^2 \times 10}{KVA}$

So, $\frac{X(KVA)}{I \times X(KV^2)} = \%X$

→ So, Short Circuit Current (I_{sc}) = $\frac{V}{X}$

or; $\frac{V}{X} = \frac{I}{\%X} \times 100 \Rightarrow I_{sc} = \frac{I}{\%X} \times 100$

where; I = normal full-load current.

* %age of reactance and base KVA:-

→ So from the above, it is seen that the %age of reactance (X) depends upon [KVA] rating.

→ Generally, the various equipment used in the power system have different [KVA] rating. Therefore, it is necessary to find out %age of reactance (X) of all the elements on a common 1000 [KVA] rating, known as base KVA.

- The base KVA of the power system may be;
 - Equal to the largest plant capacity.
 - Equal to the total plant capacity.
 - Any arbitrary value.

→ So, now all the %age of (X) at of rated KVA (KVA) is to be convert %age of (X) at base KVA.

So; $\%X = \frac{\text{Base KVA}}{\text{Base KVA}} \times \%X_{\text{Rated KVA}}$

* Short Circuit KVA :-

→ The product of normal system voltage (V) & short circuit current (I_{sc}) at the point of fault is expressed in KVA known as short circuit KVA.

We know that; $I_{sc} = \frac{I}{\%X} \times 100$

So; Short Circuit KVA = $\frac{3V \times I_{sc}}{1000}$

$= \frac{3V \times \frac{I}{\%X} \times 100}{1000}$

$= \frac{3VI}{1000} \times \frac{100}{\%X}$

⇒ Short Ckt KVA = $\text{Base KVA} \times \frac{100}{\%X}$

where; %X = % of reactance upto point of fault.

* Steps for Symmetrical fault Calculations:-

Step 1 → Draw the single line diagram of the complete network indicating the rating, voltage & % of reactance of each element of the network.

Step 2 → Choose a numerically convenient value of base KVA and convert all %X to that base value.

Step 3 → Corresponding to the single line diagram of the network draw the reactance diagram showing it of the system & neutral. Indicate the %X on the base KVA in the reactance diagram. The X^s in the system should be represented by a reactance in series.


Step 4 → Find total %X of the network upto point of fault & total %X_r.

Step 5 → Then we have to find out full-load current corresponding to base KVA and normal system voltage at the point of fault.

Step 6 → So short circuit current (I_{sc}) = $\frac{I}{\%X} \times 100$

and; Short Ckt KVA = $\text{Base KVA} \times \frac{100}{\%X}$

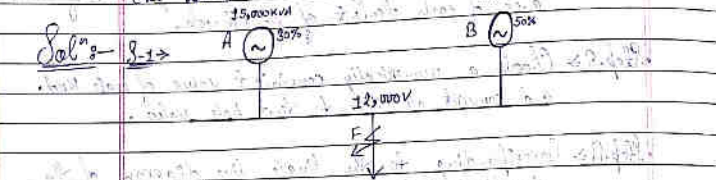Problem-01. In the single line diagram of a 3φ system, the %X of each alternator is based on its capacity. Find the short circuit current that will flow into a complete 3φ short ckt. At 'F'.



Solⁿ: S-1 →
 S-2 → Let the base KVA = 15,000 + 20,000 = 35,000 KVA


$$\%X_A = \frac{\text{Base KVA}}{\text{Rated KVA}} \times \%X_{\text{rated KVA}}$$

$$= \frac{35,000}{15,000} \times 80 = 186.67\%$$

$$= 70\%$$

and; $\%X_B = \frac{\text{Base KVA}}{\text{Rated KVA}} \times \%X_{\text{rated KVA}}$
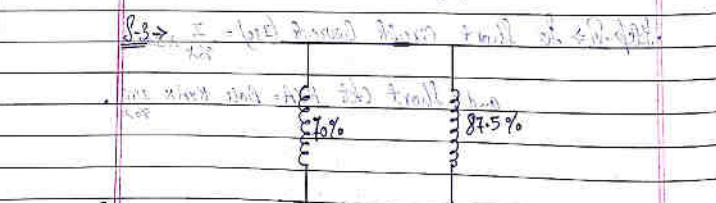
$$= \frac{35,000}{20,000} \times 50 = 87.5\%$$



S-4 → $\%X_{\text{upto point of fault}} = \%X_A // \%X_B$

$$\Rightarrow \%X_{\text{upto point of fault}} = \frac{X_A \cdot X_B}{X_A + X_B}$$

$$= \frac{70 \times 87.5}{70 + 87.5}$$

$$= 38.89\%$$

S-5 → $I_{\text{base kVA}} = \frac{35,000 \text{ KVA}}{\sqrt{3} \times 12 \times 10^3}$

$$= \frac{35,000 \times 1000}{\sqrt{3} \times 12 \times 10^3}$$

$$= 1684 \text{ Amp.}$$


S-6 → $I_{sc} = \frac{I}{\%X_T} \times 100$

$$= \frac{1684}{38.89} \times 100$$

$$= 4330 \text{ Amp.}$$

Date: 23/02/2019

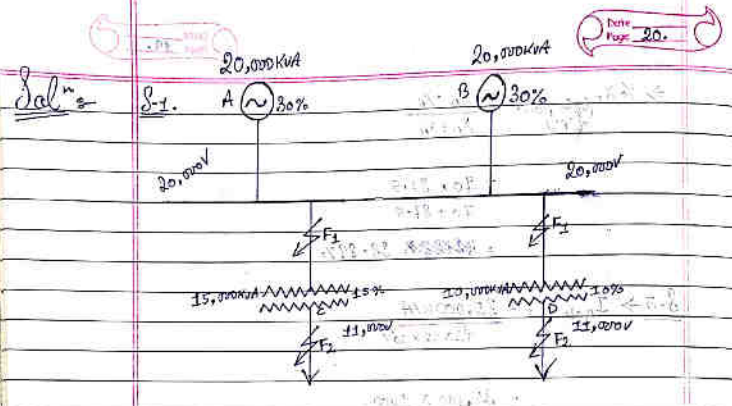Problem-02. A power system consists of 2 generators having capacity of 20,000 KVA each. It is connected to a bus-bar having voltage 20,000 volts. 2 X's of capacity 15,000 KVA & 10,000 KVA are taking tapping from the above bus-bar and obtained a voltage of 11,000 volts. If the fault occurs on both HT/LT side of the X's, what should be the rating of the ckt breaker installed on both side to protect under short ckt condition. I also find out max^m short ckt current on both sides; having generating % of 30% each & X% of 15% & 10%.




8-2. Taking base KVA = 20,000 + 20,000 + 15,000 + 10,000
 = 65,000 KVA

So, %X_A = $\frac{\text{Base KVA}}{\text{Rated KVA}} \times \%X_{\text{rated}}$
 = $\frac{65,000}{20,000} \times 30$
 = 97.5%

$\Rightarrow \%X_B = \frac{65,000}{20,000} \times 30$

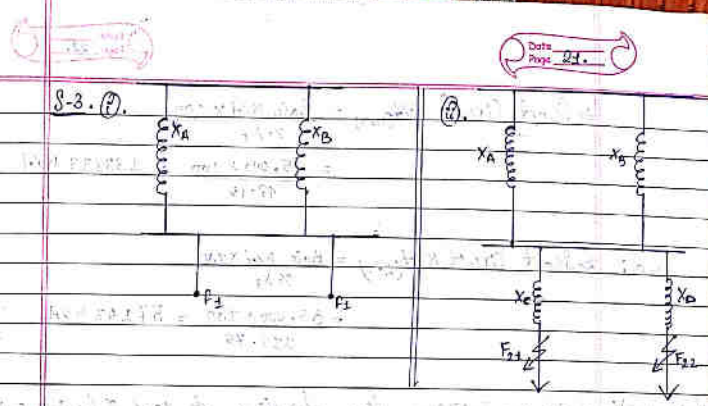in final answer = 97.5%
 $\Rightarrow \%X_A = \frac{65,000}{20,000} \times 30 = 97.5\%$
 $\Rightarrow \%X_B = \frac{65,000}{20,000} \times 30 = 97.5\%$
 $\Rightarrow \%X_C = \frac{65,000}{15,000} \times 15 = 65\%$
 $\Rightarrow \%X_D = \frac{65,000}{10,000} \times 10 = 65\%$



8-4. (P) %X_{T1} = $\frac{X_A \cdot X_B}{X_A + X_B} \left(\frac{X_A}{X_B} \right)$

(ii) %X_{T2} = $\frac{(X_A // X_B) + X_C}{X_A + X_B + X_C}$
 = $\frac{97.5 \times 97.5}{97.5 + 97.5} + 65$
 = 113.75%

$\Rightarrow \%X_{T2} = \frac{(X_A // X_B) + X_C}{X_A + X_B + X_C}$
 = $\frac{97.5 \times 97.5}{97.5 + 97.5} + 65$
 = 113.75%

Here; X_{T1} = X_{T2}

8-5. I_{HT} (Base KVA) = $\frac{\text{Base KVA}}{\sqrt{3} \times 20,000} = \frac{65,000 \text{ KVA}}{\sqrt{3} \times 20,000} = \frac{65,000 \times 10^3}{\sqrt{3} \times 20 \times 10^3} = 1877 \text{ A}$

$\Rightarrow I_{LT} (\text{Base KVA}) = \frac{65,000 \text{ KVA}}{\sqrt{3} \times 11,000} = \frac{65,000 \times 10^3}{\sqrt{3} \times 11 \times 10^3} = 3412 \text{ Amp}$

8-6. I_{sc(LV)} = $\frac{I_{HT}}{\%X_{T1}} \times 100 = \frac{1877}{97.5} \times 100 = 1915 \text{ Amp}$

I_{sc(LV)} = $\frac{I_{HT}}{\%X_{T2}} \times 100 = \frac{1877}{113.75} \times 100 = 1651 \text{ Amp}$

$$\Rightarrow \text{Short Circuit KVA}_{(H.V.)} = \frac{\text{Base KVA} \times 100}{\% X_T}$$


$$= \frac{65,000 \times 100}{47.75} = 133333 \text{ KVA}$$

and;
$$\Rightarrow \text{Short Circuit KVA}_{(L.V.)} = \frac{\text{Base KVA} \times 100}{\% X_T}$$

$$= \frac{65,000 \times 100}{113.75} = 57143 \text{ KVA}$$

Problem-03.* A 3 ϕ transmission line operating at 10kV & having a reactance of 7 Ω & reactance of 4 Ω is connected to generating station bus-bar through 5MVA step-up XT having reactance of 5%. The bus-bars are supplied by a 10MVA alternator having 10% reactance. Calculate the SC KVA fed to symmetrical fault between phases if it occurs.
 (i) At the load end of transmission line.
 (ii) At the high voltage terminal of the XT.

Solⁿ:-

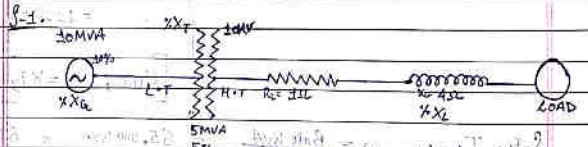

S-2. Taking base KVA = 10MVA = 10 x 10³ KVA


$$\Rightarrow \% X_a = \frac{10 \times 10^3 \times 10}{10 \times 10^3 \times 10} = 10\%$$

$$\Rightarrow \% X_T = \frac{10,000 \times 5}{5,000} = 10\%$$

$$\Rightarrow \% X_L = \frac{\text{Base KVA} \times X_L}{10 \times 10^3 \times 4} = \frac{10 \times 10^3 \times 4}{10 \times 10^3} = 40\%$$

$$\Rightarrow \% R_L = \frac{\text{Base KVA} \times R_L}{10 \times 10^3 \times 1} = \frac{10,000 \times 1}{10 \times 10^3} = 10\%$$

S-3. Reactance diagram.

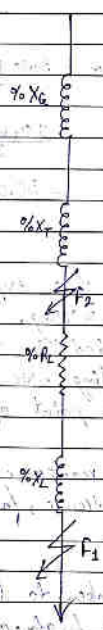

S-4.
$$\% X_1 = \% X_a + \% X_T + \% X_L$$

$$\Rightarrow \% Z_1 = \sqrt{(\% R_1)^2 + (\% X_1)^2} = \sqrt{10^2 + 60^2}$$

$$= 60.82\%$$

$$\therefore \text{SC KVA}_1 = \frac{\text{Base KVA} \times 100}{\% Z_1}$$

$$= \frac{10,000 \times 100}{60.82} = 16442 \text{ KVA}$$

(ii) $\% X_2 = \% X_0 + \% X_T$
 $= 10\% + 10\%$
 $= 20\%$

$\% S_o, S_c \text{ KVA} = \frac{S_{base} \text{ KVA} \times 100}{\% X_2}$
 $= \frac{10,000 \times 100}{20}$
 $= 50,000 \text{ KVA}$

Date: 15/02/2019

- * Reactors:— In the expanding power system the fault level is also rising.
- The C.B. connected in the skt (or) power system must have capable of dealing with max^m possible s.c. current, that can occur at their point of connection.
- Generally, the reactance of the ^{system} ~~skt~~ under fault condition is very low. Hence, fault current rises dangerously to a high value.
- If no step taken to limit that value the duty imposed in C.B. is very high, and may damage the equipment.
- In order to limit the short circuit current to a value which the C.B. can handle additional reactance known as reactors are connected in series with ~~the~~ the system at suitable points.
- A reactor is a coil of number of turns designed to have a large inductance.
- As the reactors have low resistance hence the drop will be low & may little change on efficiency.

* Advantages:-


- Limit fault current & prevents the over-heating of equipments & from failure due to destructive mechanical forces.
- Troubles or faults are localised or isolated at the point where they originate without communicating their disturbing effect to other parts of the power system.
- This permits lower rating of C.B. to be installed

* Locations of Reactors:-

- The reactors may be connected in series with each generator, in series with feeder & in series with bus-bar.

* Generator Reactors:-

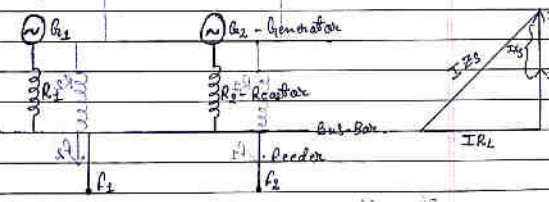- When the reactors are connected in series with each generator, they are known as generator reactors.




→ Like the reactor may be considered as a part of leakage reactance of the generator; hence its effect is to protect the generator in case of any short skt beyond the reactor.

* Disadvantages

- There is a constant voltage drop & power loss in reactors even during normal operation.
- If fault occurs in bus-bar & feeder the voltage value of bus-bar reduced to a low value causing generator to fall out of step.
- If any fault occurs at any feeder, the continuity of the supply is likely to be affected.
- Due to these disadvantages the reactors are no longer connected in series with generator.

* Feeder Reactors

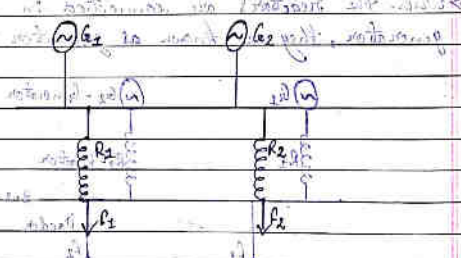


→ When the reactors are connected in series with each feeder they are known as feeder reactors. As most of the faults are near the feeder, a large number of reactors are used for such circuit.

- * Advantages - If fault occurs on any feeder the voltage drop in the reactor will not affect the bus-bar voltage, so there is no loss of synchronism of generator.
- The fault occurs on any feeder will not affect other feeders & continuity of the fault are localised.

* Disadvantages

- There is a constant power loss & voltage drop in the reactors even during normal operation.
- If fault occurs in bus-bar, no protection is provided to the generator; only the fault current limited by leakage reactance of the generator.
- If the no. of generator is increased, the size of feeder reactor will have to be increased to keep the short circuit current within the ratings of the feeder circuit breaker.

* Bus Bar Reactors

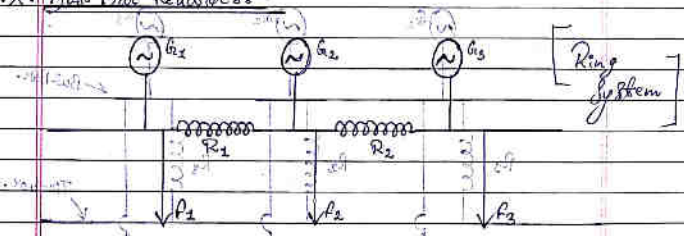


→ From the above two types of reactor locations, there is a continuous voltage drop & power loss in all conditions. So in order to avoid this, the reactors are to be located in the bus-bar with two methods of arrangement:

1. Ring System
2. Tie bar System

A. Ring System

- In this system bus-bar is divided into section and these sections are connected through reactors.
- Under normal operating conditions, each generator will supply its own section of the load & little power fed from other generator; this results low power loss & voltage drop in reactor.
- The advantage is that if fault occurs on any feeder only the generator mainly feeds the fault current while the current from other generator is small due to presence of reactor.
- Only that portion of the bus-bar is get affected.

B. Tie bar System

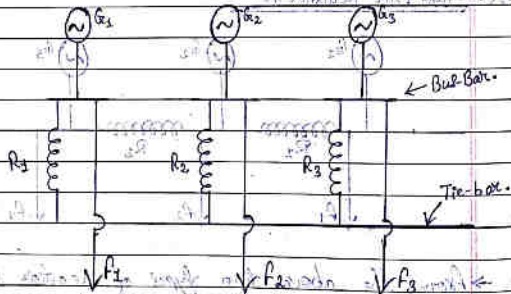


→ When we compare Tie-bar system with ring system, there are effectively 2 reactors in series between sections, so that reactor must have half of the reactance, that used in ring system.

- Tie-bar System (advantage) if a additional generator may be connected to the system without requiring changes in the existing generator.
- However, there is a disadvantage that is, it requires a additional bus-bar.

Date: 17/04/2019

*. Problem → A 3φ transmission line operating at 33KV & having resistance of 5Ω & reactance 10Ω is connected to the generating station through 15000KVA step-up transformer connected to the bus-bar with 2 alternators of one 10,000 KVA each with 10% reactance and 5000 KVA with 7.5% reactance. Calculate the S.C KVA fed to the symmetrical fault between phases if it occurs;

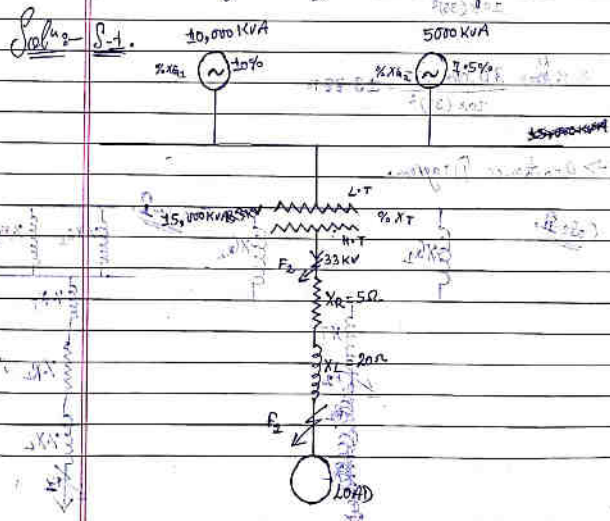- At the end of the transmission line.
- At the high voltage terminal of the X.



S-2 → Taking base KVA = 10,000 + 5,000 + 15,000 = 30,000 KVA

$$\Rightarrow \%X_{G1} = \frac{30,000}{10,000} \times 10\% = 30\%$$


$$\Rightarrow \%X_{G2} = \frac{30,000}{5,000} \times 7.5\% = 45\%$$

$$\Rightarrow \%X_T = \frac{30,000}{45,000} \times 10.2\% = 8.0\%$$

$$\Rightarrow \%X_L = \frac{30,000}{10 \times (33)^2} \times 20 = 55.5\%$$

$$\Rightarrow \%R = \frac{30,000}{10 \times (33)^2} \times 5 = 13.77\%$$

S-3 → Reactance Diagram.

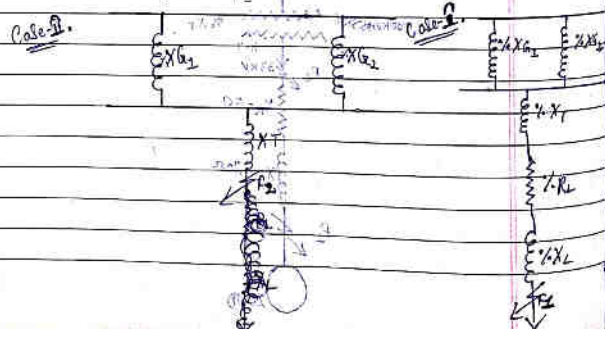

S-4 → Total $\%X_2 = \left(\%X_{G1} // \%X_{G2} \right) + \%X_T + \%X_L$

$$= \frac{30 \times 45}{30 + 45} + 8 + 55$$

$$= 97\%$$

$$\Rightarrow \%Z_2 = \sqrt{\%R^2 + \%X_2^2} = \sqrt{(13.77)^2 + (97)^2} = 97.97\%$$

[for Case-I]

→ Total $\%X_2 = \left(\%X_{G1} // \%X_{G2} \right) + \%X_T$

$$= \frac{30 \times 45}{30 + 45} + 8$$

$$= 42\%$$

[for Case-II]

S-5 → Case-I → Short Ckt KVA = Base KVA × 100

$$\%Z_2$$

$$= \frac{30,000}{97.97} \times 100$$

$$= 3062.1 \text{ KVA}$$

Case-II → S.C. KVA = Base KVA × 100

$$\%X_2$$

$$= \frac{30,000}{42} \times 100$$

$$= 71.428 \text{ KVA}$$

* Circuit Breaker:-

- > A power system consists of various circuit like transmission lines, distributors, feeders, generating plants, transformer, etc.
- > Under normal & abnormal condition the power system control by different protective element like fuse, C.B., relay, etc. & P.T., etc.
- > In the installation voltage and current different protective equipments are installed.
- > If the power system is low voltage, ^{low current} ~~high current~~ fuses are installed in the line which is blown out when there is fault & again it is rewireable after clearing of faults.
- > In high voltage & high current power system, the value of voltage & current is highly sensitive; if it increases from rated value it cause serious fault; so for high voltage installation C.B., relay, C.T. & P.T., etc. are used.

- * C.B -> C.B is a piece of equipment which can;
- Make or break a ckt either manually or by remote control under normal condition.
 - Break the circuit automatically under fault condition.
 - Break the circuit either manually or remote control under fault condition.

* Operating Principle of C.B:-

- > A C.B is a manual or automatic operating device essentially consists of fixed & moving contact called electrodes.
- > Under normal operating condition this contacts are remain closed and will not open automatically until and unless the system is faulty.
- > Although the contacts can be open manually or by remote control whenever desired.
- > When fault occurs at any part of the system the trip coil of the relay get energised and energised the C.B. Hence the moving contact pulled a part by some mechanism and thus opening the main circuit.
- > When the contacts of the C.B are separated under fault condition an arc (spark) is struck between fixed & moving contact. This current is thus able to continue until the discharge ceases.
- > The production of arc not only delays the current interruption process but also produce enormous amount of heat is produced, which may damage the C.B. itself.
- > So the main problem is extinguishing of arc in shortest possible time.

$$\left[\text{Current/Unit Area} = \text{Current Density} \right]$$

IMP

X. Arc Phenomenon:-

or fault
 → When short ckt occurs, a heavy current flows through the contacts of the C.B. before they are opened by protective system.
 → At the instant the contacts are begin to separate the contact area decreases rapidly. At that time the fault current is very large, so the current density is increased which cause rise of temperature of the contacts.
 → The heat produced in the medium betⁿ the contacts is sufficient to ionised the air or vapourised the oil.
 → The ionised air or vapour will act as a conductor and current starts to flow in that medium which been at a arc betⁿ the contacts.
 → The potential difference betⁿ the contacts is quite small and it just sufficient to maintain the arc.
 → The arc provides low resistance path for current & the contacts will remain unaltered. So long as arc ~~is present~~ persists.

$$V_{arc} = \frac{V_{supply}}{2} + \frac{V_{supply}}{2} = V_{supply}$$

→ The factors which influence the arc phenomenon depends upon the arc resistance.
 → The greater the arc resistance, smaller the current flow between the contacts. So the arc resistance depends upon following factors;

(A) Degree of Ionisation → The arc resistance increased with the decrease in the no. of ionised particles between the contacts.
 (B) Length of the Arc → The arc resistance increases with the length of the arc i.e. the separation betⁿ the 2 contacts increases then the resistance of the arc also increases.
 (C) Cross-sectional area of arc → The arc resistance increases with decrease in the area of cross-section of the arc.

X Principle of Arc Extinction →
 → The factors responsible for arc betⁿ the contacts are;
 (A) Potential difference betⁿ the contacts.
 (B) Ionised particles betⁿ the contacts.
 (C) When the contacts (P.C) are in a small separation, the potential difference betⁿ them is sufficient to maintain the arc. One way to extinguish of arc is to separate the contacts to such a distance that potential difference becomes inadequate to maintain the arc.
 However, this method is not practicable in high voltage system because the separation of many inches may be required.

(ii) → The ionised particles betn the contacts tends to maintain the arc. If the arc path is de-ionised the arc extinction will be facilitated. So, this may be achieved by cooling the arc or by bodily removing the ionised particles from the space betn the contacts.

IMP * Method of Arc Extinction:-

→ There are two methods used for extinction of arc i.e.

- (i) High resist. method.
- (ii) Low resist. method (or) Current Zero method.

(i) High resist. method → In this method the arc resistance is made to increase with time so that current is reduced to a value which is insufficient to maintain the arc consequently the arc is extinguished.

→ The principal & chief drawback of this method is that enormous amount of heat is developed in the arc. Therefore, it is employed only in dc C.B or low capacity ac C.B.

→ The resist. of the arc may be increased by four ways:

(i) Lengthening the arc:- The resist. of the arc is directly proportional to the length of the arc. So the length of the arc can be increased by increasing the gap betn the contacts.

(ii) Cooling the arc:- Cooling helps de-ionised the medium betn the contacts which increases arc resist. So, this can be achieved by blowing a gas blast directed along the arc.

ac → cross-section

(iii) Reducing (or) section of the arc:- If the area of cross-section of the arc is reduced the voltage necessary to maintain the arc is increased. In other word, the resist. of the arc path is increased by decreasing the cross-section of the arc by letting the arc pass through a small narrow opening or by smaller area of contacts.

(iv) Splitting the arc:- The resist. of the arc can be increased by splitting the arc into a no. of smaller arcs in series. Each one of this arc experienced the effect of lengthening & cooling.

→ The arc may be split by introducing some conducting plates or horn betn the contacts known as arcing horns.

IMP (ii) Low resist. method → This method is employed for arc extinction in ac cbts only. In this method arc resist. is kept low until current is zero when the arc extinguishes naturally and it prevents from restriking inspite of the rising voltage across the contacts. All modern high voltage C.B employes this method of arc extinction.

→ In a ac system the current reduced to zero in every half cycle. At every current zero the arc extinguishes for a brief moment. Now the medium cost and ions of electrons so that it has small dielectric strength and can be easily broken down by rising contact voltage known as re-igniting voltage. If such a breakdown occur the arc persists for next half cycle. But immediately current zero, the dielectric strength betn the contact built-up more rapidly than the voltage across the contact (rate of increasing of dielectric strength > voltage develop across the contact).

→ Hence, the arc fails to re-strike & current will be interrupted.

→ The rapid ~~increase~~ increase of dielectric strength of the medium near current zero can be achieved by causing the ionic particles in the space between the contact to re-combine into neutral molecules or sweeping away ionised particles and replacing them by un-ionised particles.

~~between the contact~~
~~Disturbing of the gap~~

→ The dielectric strength between the contact can be achieved

$$C = \epsilon_0 \frac{A}{d}$$

$$\epsilon_0 = \frac{ed}{A}$$

by;

(i) Lengthening of the gap → The dielectric strength of the medium is proportional to the length of gap between the contacts therefore, by opening the contacts rapidly ~~more~~ higher dielectric strength of the medium can be ~~also~~ achieved.

(ii) High pressure → If the pressure of the arc increases then the density of ~~particles~~ the ionic particles decreases. Hence, dielectric strength of the medium ~~is also~~ increases.

(iii) Cooling → Natural combination of ionic particles takes place more rapidly if they are allowed to cool. Hence dielectric strength of the medium increases.

(iv) Bluff Effect → If the ionised particles of both the contacts are swept away and replaced by ~~more~~ neutral molecules then dielectric strength of the medium increases.

* Important terms:-

(i) Arcing Voltage → It is the voltage that appears across the contacts of the C.B. during the arcing period. At soon as ~~the~~ the contact of the C.B. separate an arc is formed; the voltage that appears ~~over~~ across the contact during arcing period is called as arcing voltage. Its value is low ^{except} ~~except~~ for the period near current zero.

→ So at that time (near current zero) the arc voltage rises rapidly to a peak value and this peak voltage tends to maintain the peak current flow, in the form of arc.

(ii) Re-striking Voltage → It is the transient voltage (unwanted frequency voltage) that appears across the contact at or near current zero during arcing period.

→ At current zero a high frequency transient voltage appears across the contact ~~is~~ and is caused by rapid distribution of energy between the magnetic & electric fields associated with part of transmission line of the system. This transient voltage is known as re-striking voltage.

→ The current interruption will be depend upon this voltage.

→ If the rate of rise of re-striking voltage is higher than rate of build-up of dielectric strength then ~~arc~~ arc - persists for another half-cycle.

→ On the other hand if dielectric strength of the medium build-up more rapidly than re-striking voltage, the arc fails to re-striking.

3. Recovery Voltage → It is the normal frequency rms voltage that appears across the contacts of the C.B. after final arc extinction, which is equal to the normal system voltage.

→ When contacts of C.B. are opened current drops to zero after some half-cycle. At contacts are separated sufficiently apart from each other, the dielectric strength of the medium is so high that it removes the ionised particles hence, the re-striking voltage is breakdown to further re-ignite of the arc and arc extinction takes place finally.

→ When ~~arc~~ interruption takes place the voltage that appears across the contact has no transient part and still normal system voltage is called recovery voltage.

Date: 22/01/2024 * Classification of Circuit Breaker:-

- According to the basis of medium use for arc extinction, there are several types of C.B.
- (i) Oil Circuit Breaker (use oil for extinction medium).
- (ii) Air Blast Circuit Breaker (here in which high pressure air use for extinction).
- (iii) SF6 Sulphur hexa fluoride (SF6 gas used as extinction).
- (iv) Vacuum Circuit Breaker (Vacuum used as arc extinction).
- (v) **Oil Circuit Breaker** → In this type of C.B., oil (insulating oil) used as arc quenching medium.
 - The contacts are opened under oil & arc is struck between them.
 - The heat of the arc dissociated or evaporated the surrounding oil into hydrogen gas.

→ The hydrogen gas occupies the volume about 1000 times that of oil displaced. So the oil is therefore pushed away from the arc & expanding hydrogen gas bubble surrounds the arc.

→ The nature of hydrogen gas is that, it is high heat conductivity & pushed the arc and their other hand it sets a turbulence in the oil & forces it into the space between the contacts, which eliminates arcing product from arc path.


Advantages → It absorbs the arc energy to decompose the oil into gas have excellent cooling properties.

- It acts as an insulator which permits smaller clearance between live conductor & earthed conductor/component.
- The surrounding oil presents cooling surface in close proximity to arc.


Disadvantages → The oil is inflammable & there is a risk of fire.

- It may be formed an explosive mixture with air.
- The arcing products remain in the oil. Hence quality deteriorates with successive operation.

Types of Oil C.B.:-

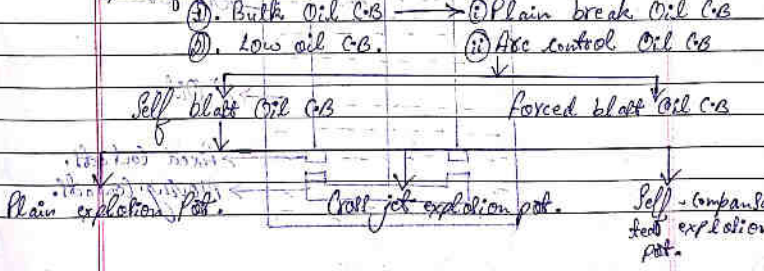


Classification of C.B. :-

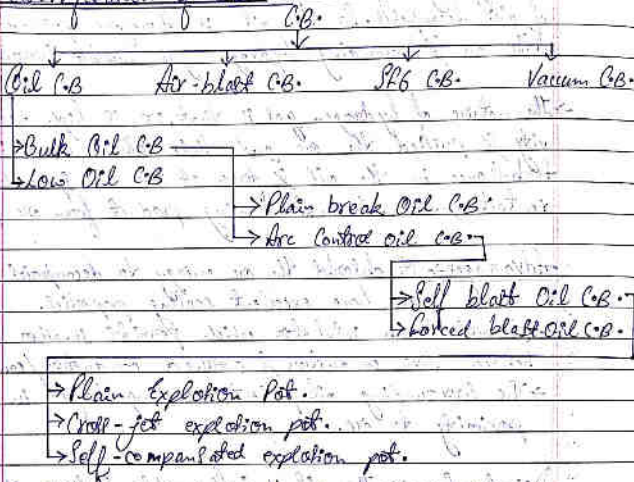

* Bulk Oil C.B. :-

① Plain Break Oil C.B. :-

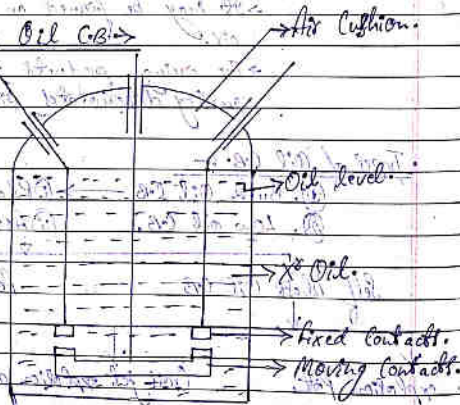

- This C.B. involves simple process of separating the contacts under whole of the oil in the tank.
- There is no special system of arc control, other than increase in length caused by separation of the contacts i.e. the arc extinction takes place in the oil medium with a critical gap bet. the contacts.
- This type of Oil C.B. is a earliest type which has very simple construction.
- It consists of fixed & moving contacts enclosed inside a weather/air tight covered tank containing oil upto a certain level.
- The tank provided with a air cushion above the oil level which allow sufficient space arc gap without generating unsafe pressure.
- It is also a double break oil C.B. because it provides two breaks simultaneously.
- Under normal operating condition, the F.C. & M.C. remain closed to start each other and breaker carries normal current.
- When fault occurs the m.c. are pushed down by protective system & an arc is struck bet. F.C. & m.c. which vaporizes oil into hydrogen gas.
- The hydrogen gas bubbles generated around the arc which cool the arc column & deionization of the medium bet. the contacts.
- The gas set-up turbulence in the oil & helps to clean-up the arc lengthen due to separating contacts the dielectric strength bet. the medium increases, so arc extinction takes place.

Disadvantages
 → There is no special control over the arc other than increase in length.
 → These breakers have long arcing time.
 → It doesn't permit high speed of interruption.


Used
 → Up to 11KV.
 → Used for low voltage installation.

Date 25/02/2019


(ii) Arc Control Oil C.B.s
 → In case of plain break oil C.B. there is a little control over the arc; so there if a long arc length is essential in order to produce ~~distance~~ ^{distance} in the oil; so in order to achieve short contact length some arc control is incorporated. Such breakers are known as Arc Control Oil C.B.s or Self-blatt Oil C.B.
 → Arc Control Oil C.B. is one of 2 types:
 (a) Self-blatt C.B.
 (b) Forced blatt C.B.
 → Self-blatt Oil C.B. In this type of C.B. the gas produced during arcing are confined to a small volume by the use of insulating rigid pressure chamber or pot surrounding the contacts.
 → So the space available for arc gas is restricted by the chamber and a high pressure is developed inside the oil which forces the oil around the arc & extinguish it.

→ So according to the construction of the chamber for produced self pressure it is of upto 3 types:
 (a) Plain explosion pot.
 (b) Cross-jet explosion pot.
 (c) Self compensated explosion pot.


(a) Plain explosion pot:-

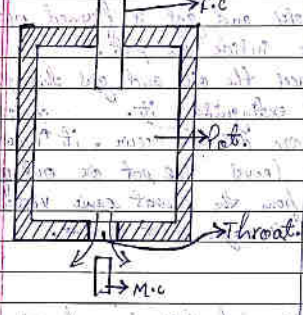

(b) Cross-jet explosion pot:-

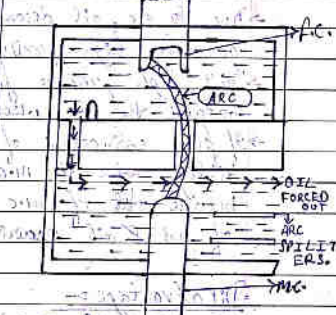

(c) Self compensated explosion pot:-

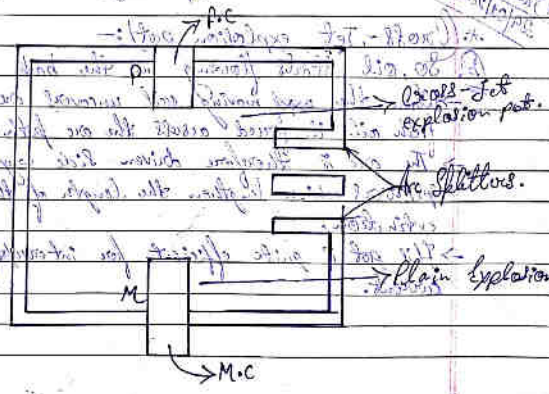

* (Plain explosion pot):-

Q. It is a rigid cylinder of insulating material (bakelite) and encloses the fixed & moving contacts. The moving contact is a cylindrical rod which is passing through a restricted opening (throat).

→ When fault occurs the contacts are get separated and arc is struck between F.C & M.C.

→ Due to arc, oil decomposes and gas is formed which generate high pressure inside the pot.

→ This high pressure forces the oil and gas through and around the arcs which extinguish it.

→ If final extinction of arc doesn't occur, it occurs immediately after the m.c. leaves the pot or out of throat, because oil of m.c. from the throat cause violent rush of gas & oil occurs through that throat.

Disadvantage:-

→ The principal limitation of this type of pot is that it cannot be used for very low & very high current.

* (Cross-Jet explosion pot):-

Q. So, oil starts flowing in the back space.

→ When the moving coil uncovers arc splitter ducts, fresh oil is forced across the arc path.

→ The arc is therefore driven side ways & touches the arc splitters which lengthen the length of the arc causing arc extinction.

→ This pot is quite efficient for interrupting the heavy fault current.



J.M.

* (Self-Compensated explosion pot):-

Q. It is a plain combination of plain explosion pot & cross-jet explosion pot; so it can interrupt low fault current & heavy fault current.

→ It consists of 2 chambers, the upper chamber is cross-jet explosion pot with two-arc splitters while the lower chamber is plain explosion pot; when short circuit occurs the rate of generation of gas is very high it acts as a cross-jet explosion pot and extinction takes place when moving contact uncovers 1st & 2nd arc splitter.

→ However, on low short circuit current the rate of gas generation is small and the trip of the moving contact reaches the lower chamber as it has enough time.

→ And during this time the gas build-up sufficient pressure and when moving contact is out of throat the arc extinction completely takes place.

B. → Forced blast oil circuit breaker:- In the self-blast C.B. the pressure will be generate by own construction device. So, the arcing time is very high.

→ In order to minimize the arcing time necessary pressure generated device externally connected to the chamber in case of force blast C.B.

→ In force blast C.B. the oil pressure is generated by the piston cylinder arrangement, so when fault occurs the m.c. separate from fixed contact & arc is struck at that time the piston cylinder arrangement provide necessary pressure inside the chamber as it is coupled with moving contact.


→ So, due to that oil jet pressure arc extinguish.

Date 30/01/2019

Date Page 48

Date Page 49

Imp. X. Low Oil Circuit Breaker

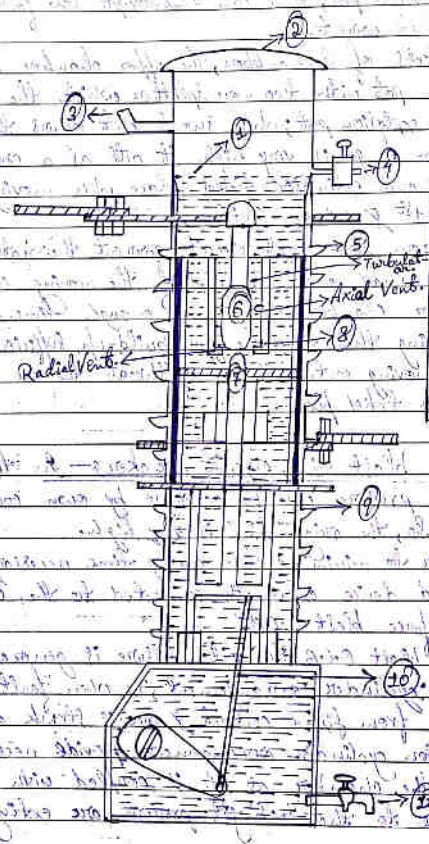

- 1. Oil level.
- 2. Top Chamber.
- 3. Rad. Vent.
- 4. Breather.
- 5. Oil Breaking Chamber
- 6. Fixed Contact.
- 7. Moving Contact.
- 8. Arc extinction device.
- 9. Supporting Chamber.
- 10. Operating Rod.
- 11. Drain Valve.

The oil use in the circuit breaker perform 2 functions
 1. It acts as an arc quenching medium & secondly
 it separate to 2 live parts.
 → It is seen that only small qty of oil actually used for
 arc extinction whereas the major part portion used as
 insulation.
 → So, for this reason if voltage rating increased the quantity
 of oil required also increases in case of bulk oil C.B.
 which not only increases the expenses, tank size &
 weight of the breaker but also increase the risk of fire
 as well as maintenance problems.
 → So, in order to minimize the problem low oil C.B. develop
 ed.
 → In case of low oil C.B, solid material is used for
 insulation purpose whereas it uses small quantity of oil
 sufficient for arc extinction.

Construction

→ It consists of 2 chambers; the upper chamber is the
 circuit breaking chamber whereas the lower chamber is
 known as supporting chamber.
 → The 2 chambers are separated by a partition, i.e. it
 prevent mixing of oil of 2 chamber.
 Supporting Chamber → It is a porcelain chamber mounted
 on a metal chamber. It is filled with oil which is
 physically separated from circuit breaking chamber.
 → The inner side of the supporting chamber of the
 annular space ^{Form} between the porcelain insulation & bakeli-
 -te wood insulator ^{Form} is employed for insulation purpose.

* Circuit Breaking Chamber -> In the circuit breaking chamber we found 3 elements:

- (i) Fixed Contact.
- (ii) Moving Contact.
- (iii) Turbulator.

-> The moving contact is a hollow cylinder which moves down by a piston.

-> There are 2 types of vents found in the turbulator i.e.

- (A) Radial Vent.
- (B) Axial Vent.

-> If the fault current is low the axial vent helps in the interruption where when fault current is high, radial vent is used.

* Top Chamber -> It is a metal chamber mounted above the circuit breaking chamber.

-> It provides space for the expansion of oil during circuit breaking.

-> It also provides with gal-vents & breathers for safety of the circuit breaker.

* Operation:-

-> Under normal operating condition the moving contact remains engaged with fixed contact & normal current flows through it.

-> When fault occurs the magnet is pulled down by tripping spring and arc is struck.

-> Due to arc the oil gets vaporised and gases produced under pressure.

-> Now, with pressure the oil & gases pass through central hole of the moving contact and gases to be outlet causing turbulence. So due to that turbulence inside the chamber

Separation of arcing products from arc path and arc get ruptured and circuit interruption caused.

* Advantages:-

- > It requires low oil.
- > It also requires smaller space.
- > It reduced risk of fire.
- > Maintenance problem low.

* Disadvantages:-

- > Due to smaller amount of oil the degree of carbonisation is high.
- > The dielectric strength of the oil deteriorates rapidly due to high carbonisation.

* Air-Blast Circuit Breaker:-

-> In this type of C.B. high pressure air blast acts as a arc quenching medium. As soon as the contacts are separated during fault, an air blast established by opening

the valve which results sweep away of arcing products to the atmosphere and also pulls the arc & contacts.

-> This causing rapidly increase of dielectric strength between the contacts, and arc is extinguish, current get interrupted.

* Advantages:-

- > The risk of fire is eliminated.
- > As arcing products are completely remove by the blast from the chamber, the degree of dielectric strength build-up is high.

→ There is no need of replacement of air at start of D.C.B.
 → Arcing time is low at the rate of dielectric strength build-up is high.
 → This C.B is used where there is frequent fault occurs due to lesser arc energy loss.


* Disadvantages - The air has relatively inferior arc-extinguishing properties.
 → Continuous maintenance required to compressor plant (air-blatt equipment).

* Volt - Upto voltage beyond 110KV.

* Types - There are 3 types of air blatt C.B.


- ① Axial Blatt type.
- ② Cross Blatt type.
- ③ Radial Blatt type.

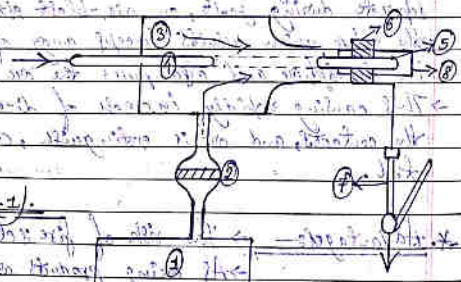① Axial Blatt → In this type of air blatt C.B, the air flows along the arc path.



(Fig-1)

- | | |
|-------------------|--------------------|
| ① Air Reservoir. | ⑥ Spring. |
| ② Air Valve. | ⑦ Sinter Isolator. |
| ③ Arcing Chamber. | ⑧ Piston. |
| ④ Fixed Contact. | |
| ⑤ Moving Contact. | |

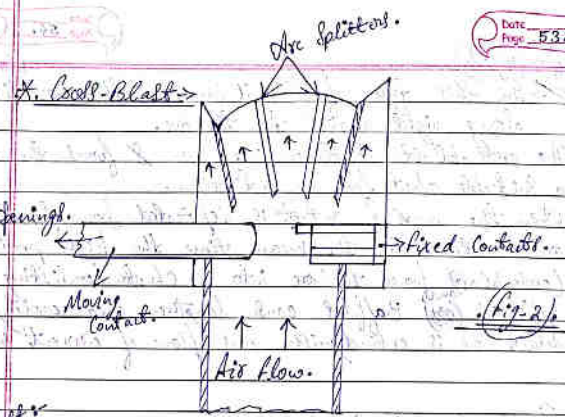

(Fig-2)

* Axial Blatt

- In this type of C.B the f.c & m.c are held together by spring pressure under normal condition. (Fig-1)
- The 2 contacts are enclosed inside an arcing chamber which is connected to a air reservoir through air valve, and this valve closed under normal condition. when fault occurs the tripping impulse open the air valve and air rushes inside the arcing chamber from air reservoir.
- Due to high pressure of air, the arc starts separated from f.c and arc is struck.
- At the same time high pressure air-blatt flows along the arc & takes away the ionised particles from the path.
- Due to this effect the dielectric strength rapidly build-up and arc gets extinguished and arcout get interrupted.
- In this type of air blatt C.B the separation length is generally small (1.75cm).


Cross blast (Fig. 2)

In this type of circuit breaker, the air is directed along right angles to the arc.

- The cross-blast lengthens the arc & forces the arc into a suitable chute for arc extinction.
- When the moving contact is separated from fixed contact arc is struck at the mean time the high pressure air (cross-blast) force the arc into a chute consisting of arc splitting (and) baffle comb lengthens and cooling of arc.
- Result arc is extinguish and flow of current interrupted.

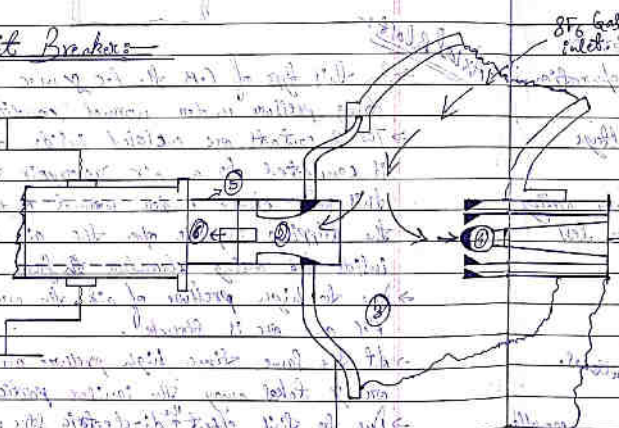X. SF₆ Circuit Breakers

- ①. Fixed Contact
- ②. Moving Contact
- ③. Arc Chamber
- ④. Spring Drive
- ⑤. Moving Member
- ⑥. Gas Out Let



Construction → It consists of fixed contact & moving contact enclosed in a chamber which is connected to a SF₆ gas reservoir.

- When contacts are separated the valve opens and SF₆ gas with high pressure inlet to the chamber.
- The fixed contact is a hollow cylinder carrying arc horn.
- Moving contact is also a hollow cylinder having rectangular hole at the centre.
- The tips of the fixed contact & moving contact are coated with copper-sulphur or resistive material.

As SF₆ gas is highly costly, so after each operation it is reconditioned and reclaimed by suitable machinery system and store in reservoir.

Working → When both the contacts are closed at normal operation the SF₆ gas surrounded the contacts at a pressure of 2.8 kg/cm².

- As soon as fault occur moving contact pulled apart from fixed contacts and the valve synchronised permits SF₆ gas at 14 kg/cm² pressure from reservoir to the arc chamber.
- This high pressure SF₆ gas absorb free electrons of the arc path & increase the dielectric strength of the medium, which cause extinction of arc.
- After extinction of arc the valve is closed by a set of spring.

Advantage → Due to superior arc quenching property of SF₆ gas the arcing time is very short.

- Dielectric strength builds up by SF₆ gas is more than 2-3 times of air.


In SF₆ gas SF₆ is used (Sulphur Hexafluoride) as arc quenching medium.

- SF₆ is a highly electro-negative gas i.e. it has strong tendency to absorb free electrons.
- All the free electrons are rapidly capture by gas to form immobile negative ions which build-up high dielectric strength both the contacts.

- It give smokeless & noiseless operation due to ~~extra~~ all closed gas circuit and no exhaust to atmosphere.
- All the chamber is closed no moisture found inside it.
- No risk of fire in such breakers.
- There is no carbon deposition.
- It has low maintenance cost.
- It is suitable for where there is explosion hazards exist such as coal mines.

Disadvantages → It is highly costly of gas.
→ Extra reconditioning is claimed ckt is needed for necessary after each operation.

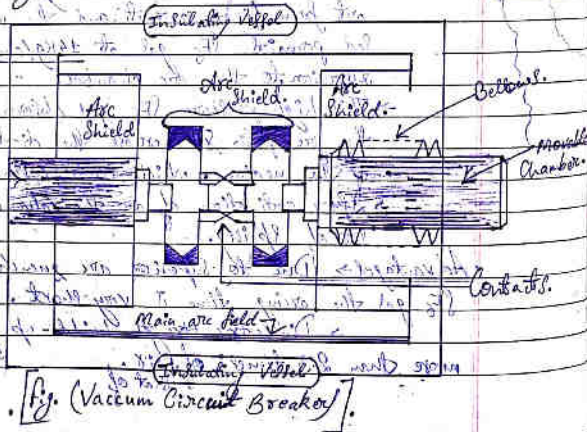Applications → It is able to dealing 60 kAmp in voltage range 50-80 KV.
→ It also used for 415 KV - 230 KV at power rating 10 MVA to 20 MVA, which is interrupting time less than 3 cycles.



Vacuum Circuit Breakers - In such breakers vacuum (Degree of vacuum) in the range of 10^{-7} to 10^{-5} torr, is used for arc quenching medium.

→ Since vacuum offer high insulating strength, so it has fast superior quenching properties ~~than~~ other ~~not~~ medium.

Principle - When the contacts of the breaker are opened in vacuum of range 10^{-7} to 10^{-5} torr an arc is produced between the contact due to ionization of metal vapour of the contact.

→ However, the arc quickly extinguish because the metal vapour, electrons & ions produced during arcing condensed rapidly due to vacuum.

Construction - In the diagram, it consists of f.c. & m.c. and arc shield (coating) mounted inside the vacuum chamber.
→ The moving member is connected to control mechanism by stainless steel bellows.
→ This allows permanent ~~gassing~~ sealing of the vacuum chamber & eliminate possibility of leak.
→ A glass vessel or ceramic vessel is used as outer insulating body.

→ The arc shield prevent deterioration of the natural dielectric strength by preventing metallic vapours ~~falling~~ falling on the inside surface of outer insulating cover.

Workings - When breaker operates the m.c. separates from f.c. and arc is struck.

The reproduction of arc is due to ionization of metal vapour and depends upon material of contact.

→ Arc is quickly extinguish because the metallic vapour & electrons are diffused ~~in a short time~~ a short time at the chamber is seized by moving & fixed member and arc shield.

→ Since vacuum has very fast rate of recovery of dielectric strength. so arc can extinguish in small separation (0.6 to 5 cm).

- Advantages:- They are compact, reliable & longer life.
- There are no fire hazards.
 - There is no gas generation.
 - They can interrupt any fault current.
 - It require less maint. charge.
 - It can withstand in lightning surge.
 - They has low arc energy.

Application:- It is used for protection of long distance transmission where the installation is outside.

→ It is used for outdoor application ranging from 22 KV to 66KV having power rating 60 to 100 MVA.

Date: 07/02/2019

Switch gear Components

1. Bushing.
2. Circuit Breaker contacts.
3. Instrument transformer.
4. Bus Bar and conductors.



Bushing:- When high voltage conductor passes through metal sheet or frame which is called as bushing. Insulation is provided in the form of bushing. So bushing helps to prevent electrical break down bet enclosed conductor and surrounding metal body.

→ It is mainly used in oil circuit breaker.

→ The failure of bushing occurs due to dielectric failure bet insulating material and conductor and secondly break-down may occur in the form of flash over before bushing get punctured.

Circuit-Breaker Contacts:- The C.B contacts are required to carry both normal current as well as short ckt currents. So they are designed such a way that the temp. should not rise specified limit and the voltage drop also low. So the C.B contacts are Tulip type contact, Finger & Wedge Contact & Butt Contact.


Date: 13/02/2019

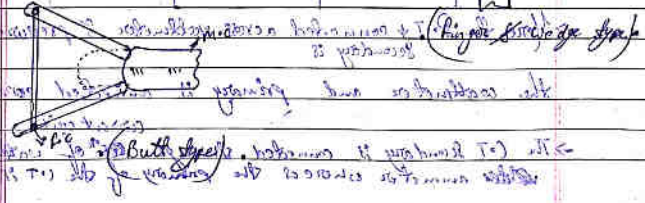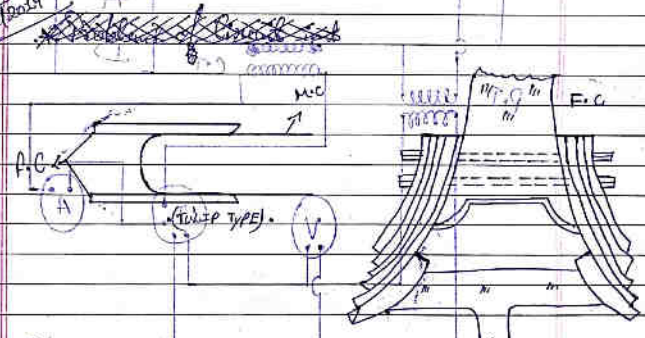

③ Instrument Transformers:- In a modern power system the circuits are operated at high voltage & high current in which the protective system & measuring system not work satisfactorily.

→ This difficulty is overcome by using instrument transformer. The function of instrument transformer is to transform voltage or currents in the power line to a value which is convenient for the operation of measuring instruments ^{as well as} relays.

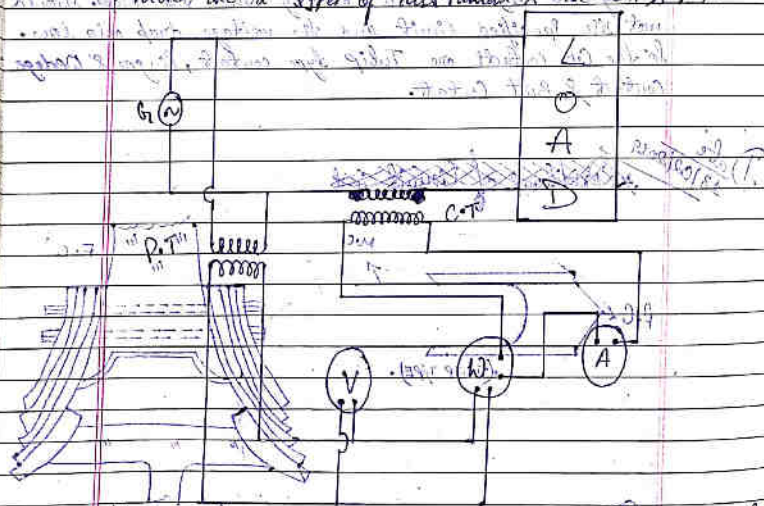→ There are 2 types of instrument transformer, C.T. & P.T.




→ Here the P.T. is connected across voltmeter & primary coil of the transformer and secondary is connected across the supply current coil.

→ The C.T. secondary is connected across secondary of voltmeter & primary of the C.T. is connected

series with the main circuit.

④ Bus-bar & conductors:- The current carrying members of the circuit breakers are P.C. & M.C. are connected external point of the breaker.

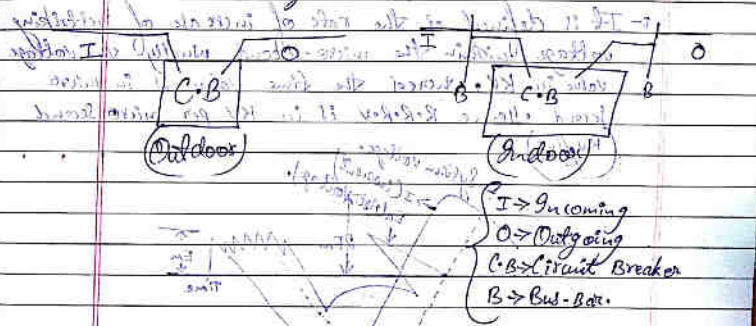→ If the switch gear is outdoor type then the 2 points are directly connected to supply line whereas if the switch gear is indoor type the incoming conductors for the C.B. connected through a bus-bar.




I → Incoming
O → Outgoing
C.B. → Circuit Breaker
B → Bus-Bar

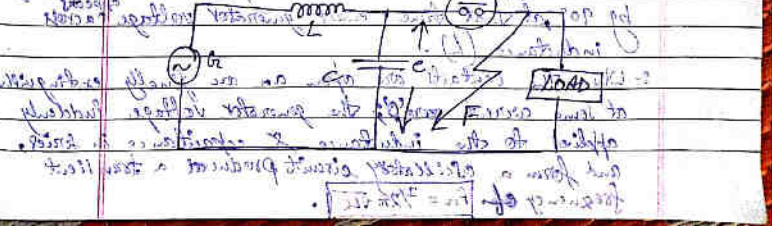* Problems of Circuit interruptions:-

→ The power system contains an appreciable amount of inductance & some capacitance. So when a fault occurs the energy stored in the system can be considerable.


→ This energy can't be dissipated within the circuit.



→ So it is (C.B) design such that it can easily dissipate the store energy.
 → In the diagram (L) is the inductance per phase upto point of fault & (C) is the capacitance per phase of the system & the resistance of the system is neglected as it is very small value.

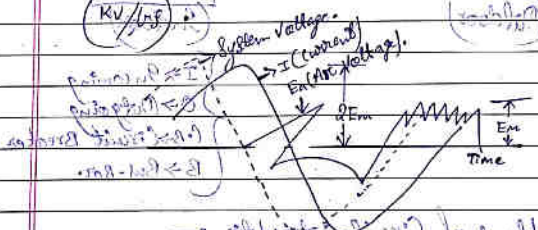(i) R.R.R.V. → Rate of rise of restriking voltage :-

It is defined as the rate of increase of restriking voltage within the micro-second usually the voltage value in KV, whereas the time value is in micro second. Hence R.R.R.V is in KV per micro second.



Consider opening of switch (C.B) during fault condition. Before switch interruption the capacitance (C) is short circuited by fault and only inductance (L) is present in the circuit.

So the short circuit current lag behind the voltage by 90° at that time active generator voltage across inductance (L).

When the contacts are open an arc finally extinguish at some current zero; the generator voltage suddenly applied to the inductance & capacitance in series and form a oscillatory circuit produced a transient frequency of $f_n = \frac{1}{2\pi\sqrt{LC}}$.

This frequency appears across capacitor (C) & Ckt breaker contact.

This transient voltage is known as re-striking voltage & may be reach instantaneously. 2 times of phase to neutral voltage i.e. 2EM and cause possibility of re-striking of arc between the contacts.

→ The rate of rise of re-striking voltage which decides whether arc restrike or not.

If R.R.R.V > R.R.R.V_{dielectric strength} Rate of rise of dielectric strength both the contacts than the arc will re-strike otherwise R.R.R.V < R.R.R.V_{dielectric strength} arc fails to re-strike. So R.R.R.V depends upon 2 factors i.e. Recovery Voltage & Natural Frequency of oscillation.

(Recovery voltage) :-
 It is the normal system voltage which is seen after extinction of arc both the 2 contacts.

(Natural Frequency of oscillation) :-
 It is the normal frequency of the system.

If short occurs near the power station then (C) is being small & natural frequency will be high & R.R.R.V also high.

(ii) Current Chopping :-

It is the phenomenon of current interruption before the natural current reaches to zero.
 → This it occurs mainly in air-blast circuit breaker, because they retain the same extinguishing power irrespective of any magnitude of current to be interrupted.

→ When it breaking low current the powerful deionizing effect of air-blast causes the current to fall ~~not~~ ~~not~~ zero before natural current zero. This phenomenon is called Current Chopping and it causes production of high voltage transient across the contact of C.B.

→ Considered one current (i) which has to be chopped down, as current chopped down therefore the energy stored in the inductor is $\frac{1}{2} Li^2$.

→ After current chopping the energy stored by the inductor will be transferred to line capacitance (C), and changing it to a voltage (v) [prospective voltage].

$$\frac{1}{2} Li^2 = \frac{1}{2} Ce^2$$

$$\Rightarrow e = i\sqrt{L/C}$$


→ The prospective voltage is very high as compare to the dielectric strength gain by the gaps. So the breaker again re-strikes.

→ As the de-ionizing effect still in action therefore chop occur again ~~and~~ ~~the~~ arc current is smaller in compare to previous case. This induces a lower prospective voltage so re-ignite the arc. So before current is sufficient severe chop may be occur until a low current is to be interrupted which produces a sufficient prospective voltage ~~and~~ arc fails to re-strike.

Date

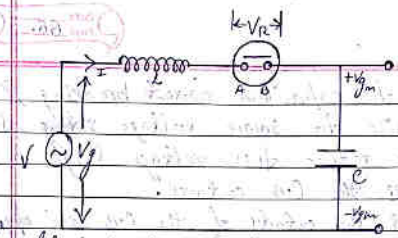(ii) Capacitive Current Breakings

→ Another cause of excessive voltage surge in the C.B. is interruption of a capacitive current. Such type of example is with power capacitor banks for power factor improvement.



→ At that time circuit actually carry capacitive current i.e. (I) leads the voltage (V) by 90° at that time the C.B. is open and the ~~capacitive~~ current reduced to zero.

→ At this instant the generating voltage (Vg) will be max (Vm) and lagging behind the current by a 90°.

→ At the opening of the C.B. leaves standing charge and charge up the capacitor (C).


→ Here (Vg) is the max voltage across C-B contacts which is initially zero and ~~increases~~ increased slowly in the beginning but after a half-cycle the plates of capacitor having the max voltage other plate (-ve) max and ~~become~~ $2V_m$.

→ This voltage is sufficient to re-strike the arc. So the separated parts of the C.B. joint by arc having low resistance.

→ This voltage increases further if further and attain voltage of value $4V_m, 8V_m$ and so on and arc further re-strike.

→ But due to leakage & corona loss this voltage max upto $5V_m$.

Resistance Switching

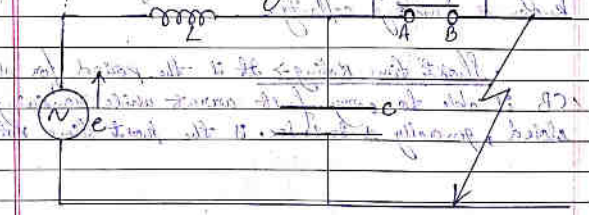

- We know that; the capacitive current breaking & current chopping give rise to source voltage oscillation. So in order to reduce this voltage surges a resistance (R) is placed across the C.B contacts.
- When fault occurs the contacts of the C.B are opened and arc is struck.
- All the contacts are shunted by resistance (R) part of the arc current diverted towards this resistance (R) continuously arc current reduces.
- A dielectric strength build-up is also continuous so arc path resistance also increases and this process continues until interruption of arc.
- The shunt resistance also helps to limit oscillatory growth of re-striking voltage i.e. $f_m = \frac{1}{2\pi} \sqrt{\frac{1}{LC}}$ $\frac{1}{4RC^2}$

Date: 18/02/2019

* Circuit Breaker Ratings *

- Breaking Capacity → It is defined as the RMS value of current that a CB is capable of breaking at a given recovery voltage under specified condition (Rated PF & Rated rise of re-striking voltage).
- Making Capacity → It is the peak value of current during the first cycle of the current after closure of CB is known as making capacity.
- Short time Rating → It is the period for which the CB is able to carry fault current while remaining arc closed, generally 2-4 sec. is the short time rating.

Date: 18/02/2019

" FUSES "

- A fuse is a short piece of metal inserted in the circuit which melts when excessive current flows through it & thus breaks the circuit.
- The fuse element is generally made up of material having low melting point & high conductivity and low deterioration due to oxidation. e.g. Silver, Copper, Gold, Platinum.
- It is inserted serial in the circuit to be protected.
- Under normal operating condition, the fuse element is at a temp. below its melting point. Therefore, it carries normal currents without overheating.
- However, when fault occurs (short ckt) or (over load) the current through the fuse increases beyond its rated value & increases the temp. of the fuse element and the fuse element melts (blown out).
- The time required for blown out of the fuse depends upon the magnitude of fault current. If fault current is greater then smaller is the blown out time & vice-versa.
- So due to this characteristics it is used for Over current protection.

* Advantages *

1. It is the cheapest form of protection.
2. Requires no maintenance.
3. Its operation is inherently automatic like CB.
4. It can break heavy short ckt current without noise & smoke.
5. The smaller size of fuse elements imposed a current limiting effect under short-ckt condition.
6. It obeys inverse time-current characteristic, suitable for overcurrent protection.
7. The minimum sizes of copper wires can be made much smaller than wires of the CB.

* Disadvantages:-

- ① Considerable time is lost in rewiring or replacing after each operation.
- ② On heavy short-circuit discrimination both fuses in series can't be obtained unless there is sufficient difference in sizes.
- ③ The current time characteristics of fuse can't always be co-related with that of protected apparatus.

* Characteristics of fuse elements:-

- Low melting point; (Tin (Sn) & lead (Pb)).
- High conductivity; (Silver & Cu).
- Free from deterioration due to oxidation; (Silver).
- Low cost; (lead, Cu, tin).

Date: _____
 * Fuse element materials:-

- The most commonly used fuse materials are lead, tin, Cu, Zn, Silver.
- For small current upto 10 amp (tin or an alloy of lead & tin) & lead 30% & tin 63%.
- For larger current we use (Cu, Silver).
- Zinc is a good fuse material which obey considerable time-lag characteristics.

* Imp. Terms:-

① Current Rating of fuse element → It is the maximum current which the fuse element can normally carry without over heating or melting.
 → It is depend upon temp. rise of the contact of fuse holder, fuse material & surrounding atmosphere.

② Fusing Current → It is the min^m current at which the fuse element melts and thus disconnect the circuit protected by it.

→ Fusing Current > Normal Current rating of the fuse.

③ Fusing factor → It is the ratio of min^m fusing current to the current rating of the fuse element.

$$\Rightarrow \text{Fusing factor} = \frac{\text{min}^m \text{ fusing current}}{\text{Current rating of fuse}}$$

→ This value is always > 1.

④ Prospective Current → It is the RMS value of the first loop of the fault current obtained if the fuse is replaced by an ordinary conductor of negligible resistance.

⑤ Cut-off current → It is the max^m value of fault current actually reached before the fuse melts.

* Type of fuse → It is of 2 types, i.e. low voltage & high voltage fuses.

Date: _____

① Low voltage fuse → (upto 100 amp) or (200 amp)

→ The low voltage fuse can be divided into 2 types, i.e.

- (i) Semi-enclosed or re-wireable fuse.
- (ii) HRC (High Rupturing capacity) fuse.

② Semi-enclosed re-wireable fuse →

→ This type of fuse is suitable where low value of fault current are to be interrupted.

→ It consists of base of porcelain and a fuse carrier also porcelain.

The fuse carrier holds the fuse element whereas the base carries in coming ^{at well as} outgoing terminal.

Working


- When fault occurs the fuse element is blown out and the circuit is to be interrupted.
- After clearing of fault the fuse carrier taken out and fuse element replaced by a new one and it is again inserted inside the base.

Advantages → The fuse carrier which is a detachable one which permits replacement of fuse element without danger.
→ The cost of the ~~fuse~~ replacement is negligible.

Disadvantages → There is possibility of renewal of fuse wire of wrong size and improper material.
→ This fuse has breaking capacity.
→ The fuse element is subjected to deterioration due to oxidation.

Uses → This type of fuse is made from 6 Amp, 16 Amp, 32 Amp, 48 Amp, 64 Amp, 100 Amp, 200 Amp, 400 Amp, 500 Amp.

HRC (High Rupturing Capacity) Fuse

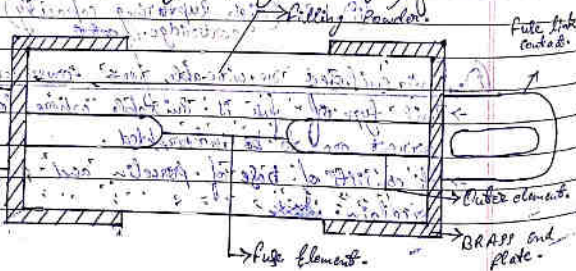

Construction

- The low & uncertain breaking ^{capacity} of the re-wirable fuse is overcome by HRC fuse.
- It consists of heating resisting ceramic body with 2 end metal caps.
- The inner side of the fuse consists of 2 outer elements which actually carry silver fuse element.
- The space inside the HRC fuse filled with filling powder i.e. Chalk, Plaster of Paris, Quartz & marble dust.
- The powder acts as HRC quenching medium or cooling medium.

Operation


- When fault occurs the fuse element melts before the fault current reaches first peak value.
- The heat produced during fuse element melts vaporised the powder and a high resistance material is formed which acts as HRC quenching medium.

Advantages → It is capable of clearing both high & low current.

- They don't deteriorate with age.
- They have high speed of operation.
- They provide reliable discrimination.
- They require no maintenance.
- Cheaper than other interrupting device.

Disadvantages → They have to be replaced after each operation.
→ Heat produced by the arc may be affected allied switches.

* HRC fuse with tripping device

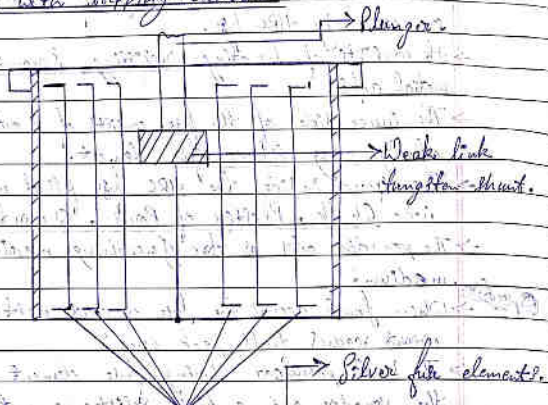

- Sometimes HRC fuse providing with tripping device.
- When the fuse blows out under fault condition, the tripping device (Plunger) cause circuit breaker to operate.
- In the diagram, the body of the fuse is a ceramic material.
- There is a fixed metallic cap, fixed rigidly at one end and the other side connected through a plunger.
- These metallic caps are joined to each other by a silver fuse elements.
- This plunger is electrically connected to metal caps through tungsten fuse element.
- When fault occurs the silver fuse elements are first blown out & now the current transfer to tungsten element and the weak link series with the tungsten wire get fused and the plunger forced outwards causes operation of C.B.

Working

- Advantages → In a case of a 1-φ fault on a 3-φ system the plunger operated and the tripping mechanism of the C.B. open 3-φ C.B. avoids 1-φing of the system.
 - By using this type of fuse full short-circuit current need not to be considered and relatively lower rating C.B. are use.
 - This type of fuse tripping C.B. generally capable of dealing small fault current.
- Use → This type of fuse may be used for breaking capacity 16,000 Amp. to 30,000 amp. at 440 Volt.


* High Voltage fuse

- ①. Cartridge fuse type → The construction of this type of fuse is similar to that of low-voltage type but some specially design features are employed.
 - In this type of fuse we found spiral helix type fuse element to avoid Corona effect at higher voltage.
 - There are 2 fuse elements are in parallel; one of low resistance (Silver) & other is high resistance (Tungsten).
- Under normal operating conditions the low resistance elements carry normal current. When fault occurs the low resistance element first blown out and the high resistance element reduce the short-circuit current and finally breaks the circuit.
- Use → It is used upto 33KV with breaking capacity about 8700 amp.

→ If operating voltage 132KV then breaking capacity 6300 Amp.

Date 02/03/2021

* Liquid type fuse :-

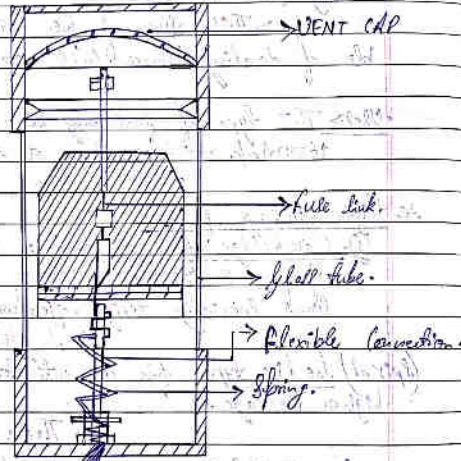

- The figure shows high voltage liquid type fuse. It consists of a glass tube filled with CCl_4 (Carbon tetrachloride) solution sealed at both ends with brass caps.
- The fuse wire is sealed at one end of the tube and the other end of the wire is held by strong phosphor-bronze spiral spring fixed at other end of the glass tube.
- When the current exceeds the prescribed limits then the fuse wire is blown out.


Wire is blown out.

- The spring retracts and through a baffle and draws fuse link inside the liquid.
- The small quantity of gas if generated at the point of fusion forces some parts of the liquid into the pocket through baffle and arc is extinguish.

IMP

* Protective Relays :-

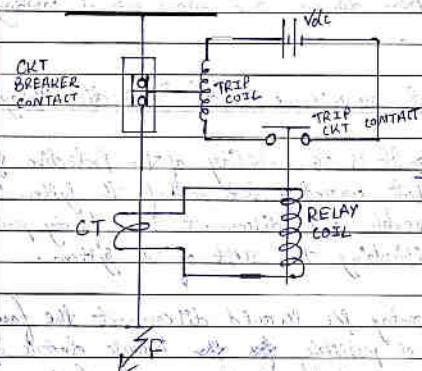→ A Protective relays is a device that detects the fault & initiates the operation of the C.B. to isolate the defective element from the rest of the system.



- The relay detects abnormal condition in the electrical circuit by constantly measuring the electrical quantities like current, voltage & frequency & phase angle which changes under fault condition.
- The typical relay system can be divided into 3 parts: i.e.
 - First part is primary winding of the CT which is connected series with the line to be protected.

secondary winding of the

- (i). Second part consists of C.T. or relay operating coil.
- (ii). Third part is the tripping circuit which may be either as on the source of supply and operate the trip ~~breaker~~ coil & CB breaker contacts.

→ When short ckt occurs at ^{the point} (P) on the transmission line the current flowing in the line is very high which results heavy current flow in relay coil and causing the relay to operate trip contacts.

→ This closes the trip circuit and making the CB to open.

→ In this way relay ensure the safety of the circuit of equipments from damage and allow normal working of the healthy portion.

IMP

* Fundamental requirements of Protective Relays:-

1. Selectivity → It is the ability of the protection system to select correctly that part of the system it is to be disconnected without disturbing the rest of the system.
2. Speed → The relay should disconnect the faulty part as fast as possible ~~for~~ because electric apparatus may be damaged if it is carrying fault current for a long time, not affected the ~~area~~ near healthy portion and prevent possibility of severe fault.
3. Sensitivity → It is the ability of the relay system to operate with low value of operating quantity.

generally

→ Relays are rated in volt-ampere. Such that the lower rated ~~relays~~ relays is higher sensitive than high rating relay. Among 1VA & 3VA relays; 1VA is high sensitive.

4. Reliability → It is the ability of the relay to operate under the pre-determined condition; without reliability the protection would be rendered largely ineffective.
5. Simplicity → The relaying system should be simple to such that it can be easily maintained. So simplicity & reliability are co-related.
6. Economic → The most imp. factor is the choice of particular protection scheme according to economic aspect. → As per the rule the protective cost should not be more than 5% of the total cost. → When the apparatus to be protected is almost importance like generator, XT & main transmission line economic considerations are often sub-ordinate to reliability.

Date: 08/03/2019

* Basic Relays:-

→ The basic relays used in power system operate by current & voltage supplied by C.T or P.T.


→ So there is change in electrical quantity under fault condition such that the relay operates according to the variation of electrical quantity.

→ Most of the relay operated according to two principles;

- i. Electro-magnetic attraction type.
- ii. Electro-magnetic induction type.


* Electro-magnetic Attraction type:-

(i) Attached structure type:-

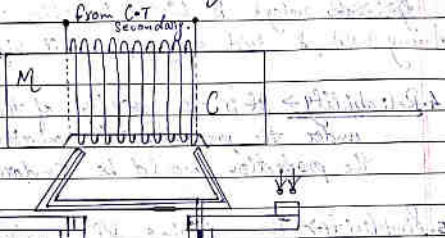

- It consists of laminated electromagnet (M) which carry coil (C).
- Below the electromagnet a pivoted laminated armature balanced by counter weight & spring attached to one side of the chamber.
- The other side of the iron armature hold the tripping contacts.
- When fault occurs the current through the relay coil increase sufficiently and armature attracted towards the electromagnet by overcome the counter weight force.
- Hence the trip circuit contact get closed & initiate the operation of C.B.


(ii) Bolt and type:-

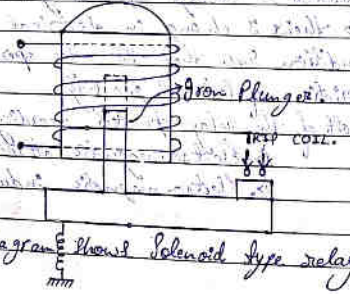

→ The above diagram shows Solenoid type relays under

fault condition the current through the relay coil more than the pick-up value causing plunger to be attracted by the solenoid by overcome plunger gravity pull & spring pressure and closed the trip circuit causing operating of C.B.

(iii) Balance Beam type:-

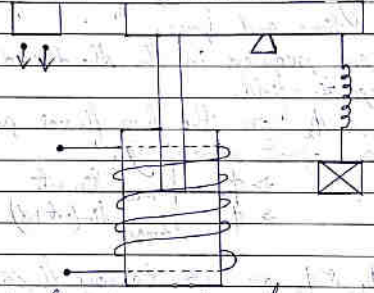

- It consists of iron armature fastened to a balance beam.
- Under normal operating condition the current through the relay coil is not so high and the beam is in horizontal position.
- On occurrence of fault the current reaches relay pick-up value and the beam is attracted downwards by the coil. This causing operation of C.B.

* Electro-magnetic induction type relay :-

- This type of relay operates on the principle of induction motor & widely used for protective relaying purpose involving ac quantities, so there is not used of dc electrical quantities in the principle of operation.
- It consists of an Al. disc which is pivoted between 2 alternating electro-magnets of same frequency but displaced in time and space.
- The torque produced in the Al. disc due to interaction of 2 magnetic field.
- Let ϕ_1 & ϕ_2 are the two fluxes produced by upper & lower magnet respectively.

$$\begin{cases} i_1 = I_m \sin \omega t \\ \phi \propto I \\ \phi = \phi_m \sin \omega t \end{cases}$$

$$\Rightarrow \phi_1 = \phi_{1max} \sin \omega t$$

$$\Rightarrow \phi_2 = \phi_{2max} \sin(\omega t + \alpha)$$

where; ϕ_1 & ϕ_2 are instantaneous fluxes and the (ϕ_2) leads (ϕ_1) by an angle (α) .


$$\Rightarrow i_1 = N_1 \frac{d\phi_1}{dt}$$

$$\Rightarrow i_1 \propto \frac{d}{dt} (\phi_{1max} \sin \omega t)$$

$$\Rightarrow i_1 \propto \phi_{1max} \cos \omega t$$

Similarly;
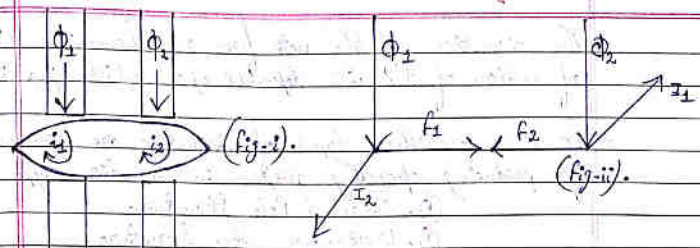
$$\Rightarrow i_2 \propto \phi_{2max} \cos(\omega t + \alpha)$$



Now; $F_1 \propto \phi_1 I_2$
 $F_2 \propto \phi_2 I_1$

Therefore; Net force $(F) \propto F_1 - F_2$

$$\Rightarrow F \propto (\phi_1 I_2) - (\phi_2 I_1)$$

$$\Rightarrow F \propto (\phi_{1max} \sin \omega t \cdot \phi_{2max} \cos(\omega t + \alpha)) - (\phi_{2max} \sin(\omega t + \alpha) \cdot \phi_{1max} \cos \omega t)$$

$$\Rightarrow F \propto \phi_{1max} \phi_{2max} [\sin \omega t \cos(\omega t + \alpha) - \sin(\omega t + \alpha) \cos \omega t]$$

$$\Rightarrow F \propto \phi_{1max} \phi_{2max} \{ \sin(\omega t - (\omega t + \alpha)) \}$$

$$\Rightarrow F \propto \phi_{1max} \phi_{2max} \cdot \sin \alpha$$

$$\Rightarrow F \propto \phi_1 \cdot \phi_2 \cdot \sin \alpha$$

→ From the above expression the net force (F) produced in the Al. disc is proportional to $\phi_1 \cdot \phi_2$ and the angle between ϕ_1 & ϕ_2 (α).


→ The force will be greater if (α) between the fluxes is greater and maximum when $(\alpha = 90^\circ)$.

→ The direction of the net force and hence the direction of motion of the disc depends upon which flux is leading.

→ So there are three types of structures are commonly used for producing operating torque in induction type relay.

- ①. Shaded pole structure.
- ②. Watt-hour meter structure.
- ③. Induction-Cup structure.

→ Shaded Pole Structure:-

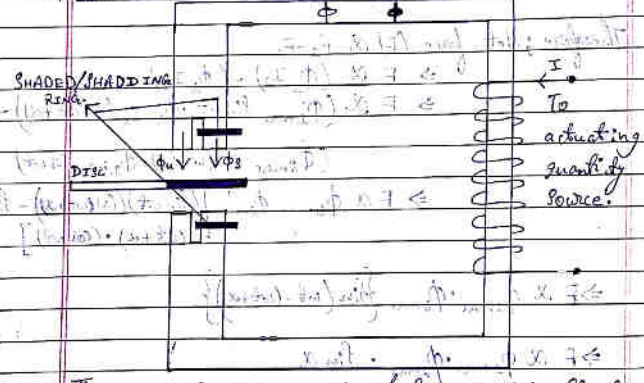

→ The general arrangement of shaded pole structure shown in the figure.

→ It consists of a pivoted Al. disc which is free to rotate in the air-gap of electro-magnet. One-half of each pole of the magnet is surrounded by a Cu-band it known as shading-ring.

→ ϕ_s = flux produced in the shaded portion of the pole.


→ ϕ_u = flux produced in the unshaded portion of the pole and (ϕ_u) lags behind (ϕ_s) by (α) .

→ Due to interaction of two magnetic field (ϕ_s & ϕ_u) torque will produced in the Al. disc. So;
 $\Rightarrow T \propto \phi_s \phi_u \sin \alpha$

→ If in the same core (ϕ_s & ϕ_u) are produced by current (I); So $\Rightarrow T \propto I \cdot I \sin \alpha$
 $\Rightarrow T \propto I^2 \sin \alpha$

→ The torque (driving torque) produced in the Al. disc is proportional to square of the current in the relay coil.

→ Watt-hour meter Structure:-

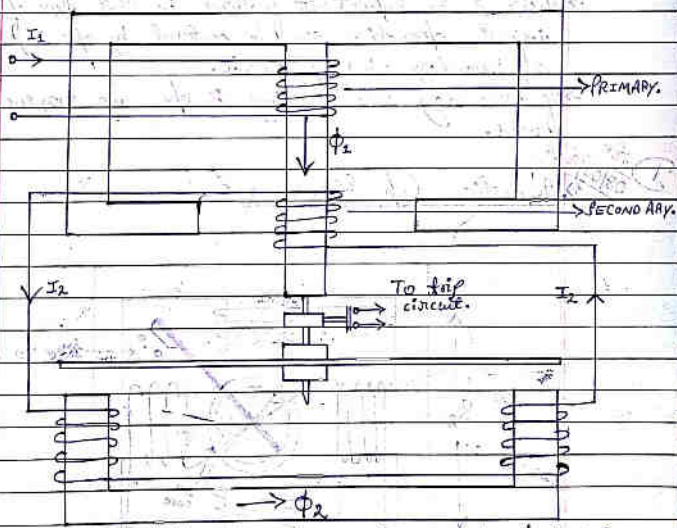

→ It consists of Al. disc arrange to rotate freely between the poles of two-electromagnet.

→ The upper-electromagnet carries 2 winding, primary and part of secondary winding whereas the lower magnet carries other part of the secondary winding.


- The primary winding carries current (I_1) and produces flux (Φ_1) which is linked with the secondary winding, produce current (I_2).
- Now, (I_2) current circulates through out the secondary winding and produce flux (Φ_2) which lags behind (Φ_1) by an angle (α).
- Hence torque produced in the Al. disc due to interaction of two fluxes (Φ_1 & Φ_2):

$$\Rightarrow T \propto \Phi_1 \Phi_2 \sin \alpha$$

- This is an important feature in this type of relay i.e. the operation can be control by opening or closing of secondary winding circuit.
- If secondary side winding is open no torque is produced.

Date: 08/10/2019

3. Induction Cup Structures -

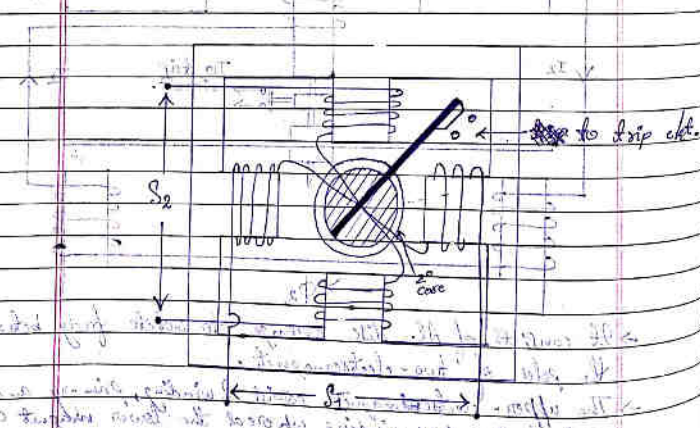

- It is the same as that of induction type motor except that the motor iron is stationary, only the rotor conductor portion being free to rotate. The moving element is a hollow cylinder which turns on its axis.
- The rotating field produced by 2 pairs of coils wound on 4-poles.
- This rotating field induces a current in the cup to necessary driving torque and hence the torque produced due to interaction of two flux Φ_1 & Φ_2 i.e.

$$T \propto \Phi_1 \Phi_2 \sin \alpha$$

- where; (α) is the phase angle between flux Φ_1 & Φ_2 .
- A pair of spring attached to the spindle to prevent continuous rotation of tripping contact.


USES:- It is very efficient torque producer so this type of relay has very high speed of operation about 0.1 sec.

* Relay timing:- According to the time of operation i.e. the time when the actuating element is energized to the instant when the relay contacts are closed, the relays are of several types;

- ① Instantaneous Relay:- An IR is one in which no intentional time delay is provided.
 - In this type of relay the contacts are closed immediately after the current in the relay coil exceeds the minimum calibrated value.
 - For this is a short time interval between the instant of pick-up and closing of relay contact.
 - The operating time of this type of relay expressed in cycles i.e. $1/50$ cycle = 0.02 sec.

②. Inverse time relay :-

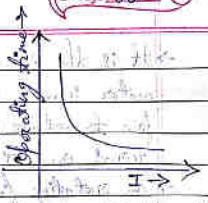→ In this type of relay the operating time is inversely proportional to magnitude of actuating quantity.
 → In this type of relay at value of current less than pick-up value the relay doesn't operate & at higher value the time operation of relay decreases steadily with increase in current.



③. Definite time lag relay :- In this type of relay there is a definite time gap between the instant of pick-up and closing of relay contacts.
 → This particular time setting is independent of amount of current through relay coil.

* I.M.P. TERMS :- Pick-up Current →

It is the min^m current in the relay coil at which the relay starts to operate. At normal operating condⁿ, the current in the relay coil is less than pick-up value.

→ Current Setting →

It is required to adjust pick-up current at any required value that is known as Current Setting. This can be achieved by using lappings on the relay operating coil. This relay operating coil provides with plug bridge which permits to alter the no. of turns on relay coil.



Peak-up Current = Rated Secondary Current of the C.T x Current Setting

Date 23/03/2019


Plug Setting Multiplier (PSM) → It is defined as the ratio of fault current in relay coil to the pick-up current.

PSM = $\frac{\text{Fault Current in relay coil}}{\text{Pick-up Current}}$

or: $\text{PSM} = \frac{\text{Fault Current in relay coil}}{\text{Rated Secondary Current of the C.T x Current Setting}}$

Time Setting Multiplier (TSM) → A relay generally provided with adjustment to the time operation, this adjustment of time is known as time setting multiplier (TSM).

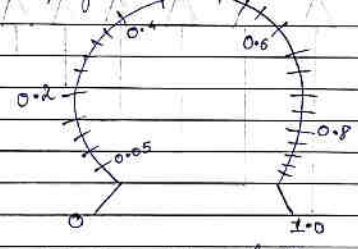The time setting dial is calibrated from 0 to 1 and each step of 0.05 sec.



* Functional Relays :- Most of the relay in the power system are of electro-magnetic attraction type or electro-magnetic induction type but the relays are generally classified according to the function to be performed known as functional relays.



→ If the relay used for protection against over current known as over current relay or if the relay use for protection of transmission line at various distance are known as distance relays.

→ Hence functional relays are several types.



- (i) Induction type over current relay.
- (ii) Induction type reverse power relay.
- (iii) Distance Relay.
- (iv) Differential relay.
- (v) Transfer Scheme.

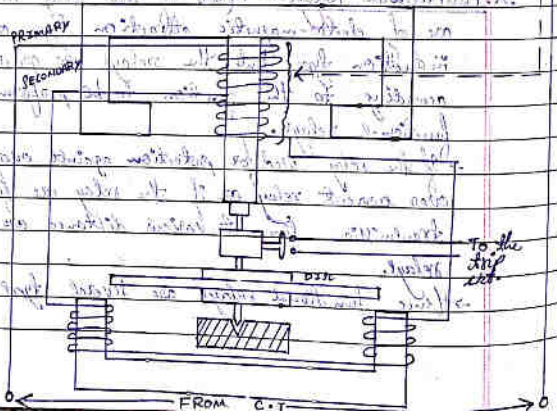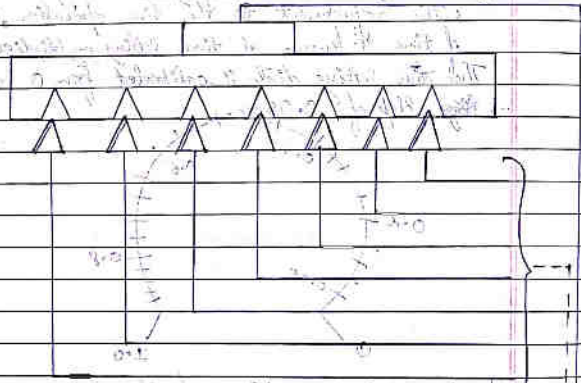(i) Induction type Over Current Relay (NON-DIRECTIONAL RELAY):



→ This type of relay works on Induction principle and initiates when current exceeds pre-determined value.

Construction

- It is a typical non-directional over current relay having consists of 2 electro-magnet the upper electro-magnet had a primary & a secondary winding and the primary winding is connected to secondary of a C.T. which is mounted in the line to be protected.
- The metallic Al. disc pivoted at the centre of the 2 magnets.
- The tappets are connected to a plug setting bridge which have several tapped at equal interval.
- The secondary winding of the relay which is at lower magnet activated by induction principle.
- The controlling torque provided to the spring by a spiral spring.
- The spindle carries the pair of contacts which rotates through a pre-set angle which can be adjusted between 0° to 360°. And this adjustment adjust the time setting.

Operation


→ The driving torque on Al. disc is set-up due to induction principle, the driving torque is opposed by the restraining torque provided by the spring under normal operating condition. Hence under normal operating condition restraining torque is greater than driving torque and Al. disc is stationary. However, the current in the line to be protected exceed pre-determined value then driving torque is greater than restraining torque and hence Al. disc is starts rotating through a pre-set angle and the trip contacts operate the CB.

Notes - This relay are used on ac ckt only and can operate for fault current in either direction.

Date 12/03/2019 Imp
 (ii) Induction type directional power relay -

→ This type of relay operates when power in the circuit flowing in a specific direction.
 → This type of relay is so design that it obtained the operating torque by interaction of magnetic field derived from both voltage & current source of the circuit to be protected.

CONSTRUCTION :-

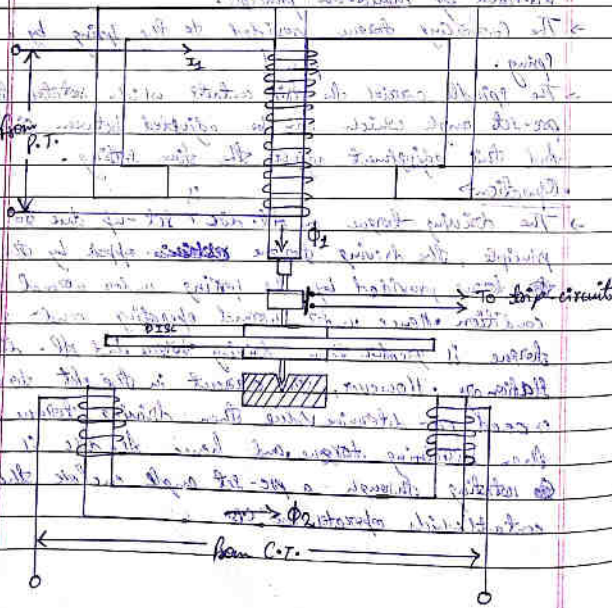

→ The typical diagram of a induction type directional power relay consists of an Al. disc which is free to rotate in between 2 electro-magnets (laminated silicon steel).

→ The upper electro-magnet carries the winding at the central limb excited by potential ϕ (P.T.).

→ The lower electro-magnet has separate winding (Current Coil) connected to the secondary of (C.T.) in the line to be protected.

→ The current coil provided with several tappings for peak-up current adjustment.

→ The spindle of the disc carries a moving contact which bridges the 2 contact when disc has rotated a θ angle.

→ By adjusting the moving angle we adjust the operating time of the relay.

$$T = \frac{\theta}{\omega}$$

OPERATION :-

→ The flux (Φ_1) due to potential coil lags nearly 90° behind the supply voltage (V).

→ The flux (Φ_2) due to current coil is phase with ckt current / line current (I).


→ Due to interaction of flux (Φ_1 & Φ_2) driving torque produce in the Al. disc.

$$T \propto \Phi_1 \Phi_2 \sin \alpha$$

$$\therefore \Phi_1 \propto I_1 \propto V$$

$$\text{and } \Phi_2 \propto I_2 \propto I$$

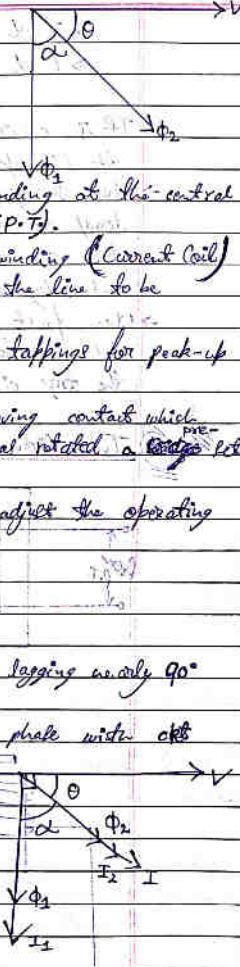
$$\Rightarrow T \propto V I \sin \alpha$$




$\Rightarrow T \propto VI \sin(\phi - \theta)$
 $\Rightarrow T \propto VI \cos \phi$ & Power in the Circuit

- It is clear that driving torque produce in the disc depends upon direction of power flow in the circuit.
- When the power flow is in the normal direction (source to load) the driving torque & restraining torque help each other to turn away the moving contact from fixed contact and relay is inoperative.
- When fault occurs the driving torque is large enough and rotate the disc in the reverse direction and close the trip circuit and cause the operation of CB.

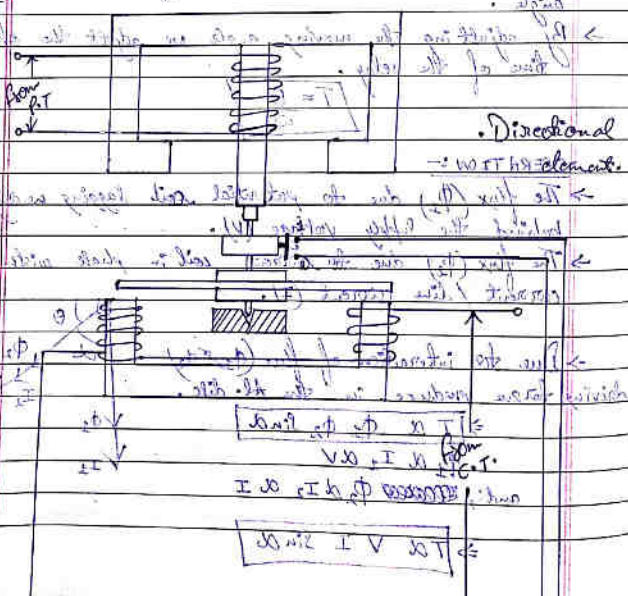IMP (ii) Induction type directional overcurrent relay :-



Non-Directional element.

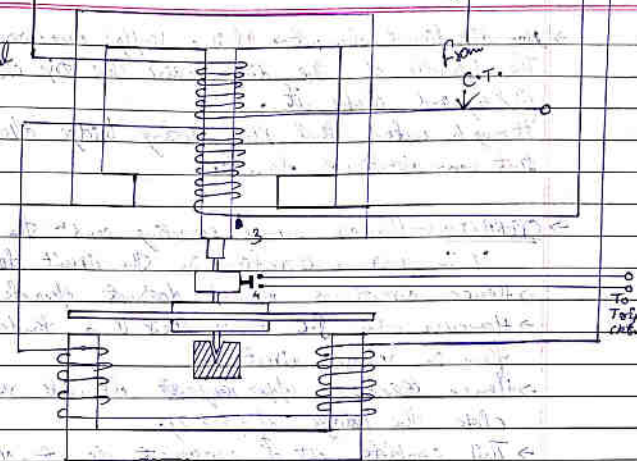

→ This type of relay is suitable directional protective relay under f.c. condition. When f.c. occurs the system voltage fall to a low value and may be insufficient torque develop in the relay to cause its operation.


→ This difficulty overcome in directional overcurrent relay.

CONSTRUCTION:-

→ It consists of 2 elements directional or well as non-directional element.

→ Directional element :- It operates when the power flows in specific direction. It consists of a potential coil excited by P.T. and current coil energized by C.T.

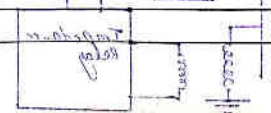
The trip contact (T.S.C) are connected in series with secondary of non-directional element so non-directional element cannot operate until the directional element operate.



- Non-directional element → It is a simple over current element. The spindle of the disc carries the strip ckt contacts (B&4) and closes it. It may be noted that plug setting bridge also provided in that non-directional element.
- OPERATIONS - Under normal operating condⁿ the power flow is in normal direction in the circuit to be protected. → Hence directional element doesnot operate. → However when S.C occurs there is a tendency of power flow in reverse direction. → Hence ~~directional~~ upper contact element rotates and close the bridge of (1&2). → This complete ckt of overcurrent element. Now the non directional "electro-magnet" activate and rotate the spindle such that the (B&4) ~~strip~~ contacts closed which activate the strip ckt.

Distance or Impedance Relay

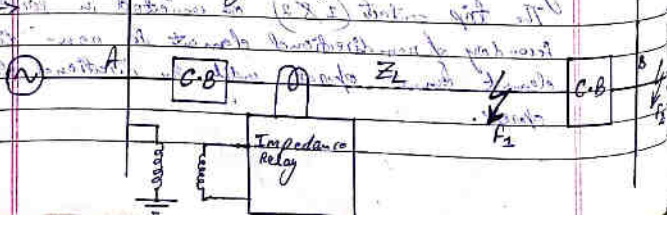- The operation of relay discussed earlier depends upon the current ~~and~~ power in the protected circuit.
- Before this the operation of relay is governed by ratio of applied voltage to current in the protected circuit.
- So an impedance relay the force produced by current element is affected by voltage element.



- The basic operation of impedance relay shown in the diagram. The impedance relay has 2 elements i.e. voltage element & current element.
- The Voltage element excited by potential X^v (P.T) whereas the current element is excited by current X^i (C.T).
- The line (A to B) is the protected zone.
- ~~The relay~~ relay is so design that it closes the ~~strip~~ contacts (relay contacts) when protected region impedance falls below pre-determined value (Z_L).

Let (V) is the normal transmission voltage.
(I) is the normal current flowing in the T.L.


$$Z_L = \frac{V}{I}$$

where; Z_L → transmission line impedance in protected zone.

- Now; Suppose fault occurs at point (F₂) in the protected zone. the impedance (Z_{L2}) = $\frac{V}{I}$ between the points where relay installed is \leq less than normal value of (Z_L). Hence relay shows operation.
- $Z_{L2} < Z_L$ ($Z_L = \frac{V}{I}$)
- and; when fault occurs outside the protected zone (F₂) then ~~the~~ (Z_L) value is remain constant as ($\frac{V}{I}$) value doesn't affected the C.T. & P.T. coil of protected zone. Hence relay is in operate.
- $Z_{L2} > Z_L$ ($Z_L = \frac{V}{I}$)

* Types of distance relay :-

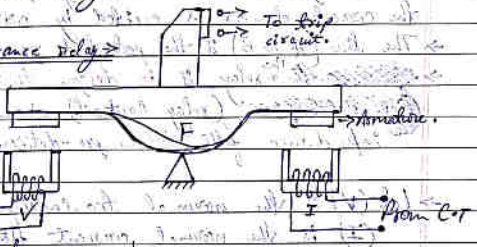- (1) Definite distance relay.
- (2) Time distance relay.
- (3) Definite distance relay.



CONSTRUCTION It consists of pivoted beam (P) and 2 electro-magnets energized respectively by current & voltage in the protected circuit.

→ The armature of 2 electro-magnet mechanically coupled to the beam (in both sides) of opposite arm.

→ The relay is so design that the torque produce by the 2 electro-magnet is in opposite direction.

Operations

- Under normal operating condition the pull due to voltage element is greater than that of current element therefore the relay contacts are open.
- However, when fault occurs in the protected zone the applied voltage to the relay decrease whereas current increase (i.e. fault).
- Therefore the pull of current element is greater than voltage element.
- Therefore the beam to tilt in a direction close to trip contact.
- As we know that, at I.C condition pull of current element is greater than pull of voltage element. So I.C can arise.


force in the
 $[K_1 V^2 < K_2 I^2]$ i.e. the pull of current element is proportional to (I^2) and force produced in the voltage element is proportional to (V^2) .

$$\Rightarrow \frac{V}{I} < \sqrt{\frac{K_2}{K_1}}$$

$$\Rightarrow Z < \sqrt{\frac{K_2}{K_1}}$$

where; K_1 & K_2 are two constant which are depends upon ampere turns of 2 electro-magnet.

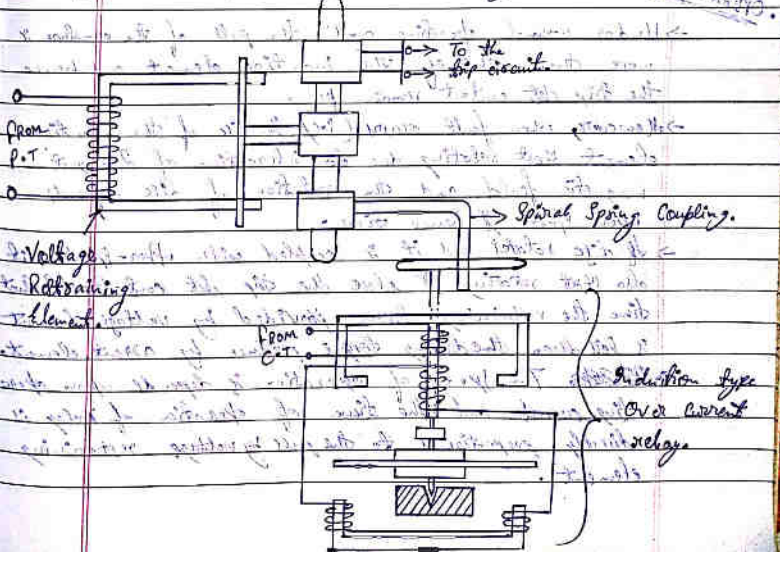~~Distance Protection Relays~~
 (1) Time distance impedance relay



INTRODUCTION


- The time distance impedance relay is one which adjust its operating time acc. to the distance of the relay from fault point.
- So operating time (T) directly proportional to $\left(\frac{V}{I}\right)^2 \left[\frac{T \propto V}{I}\right]$ or, $\left[\frac{T \propto Z}{I}\right]$ or, [T & distance].

CONSTRUCTION

- It consists of a current driven induction element similar to double-winding type induction overcurrent relay.
- The spindle carrying the disc of this element is connected by means of a spiral spring.
- The lower spindle is coupled with upper spindle which carries the trip contacts.
- The trip circuit bridge contact normally open and by voltage restraining element if it is excited from a P.T.

OPERATION

- Under normal operating cond. the pull of the armature is more than that of the induction element and hence the trip circuit contact remain open.
- However, when fault occurs (i.e.) the disc of the induction element start rotating due to interaction of 2 magnetic field and the rotation of disc depends upon speed & hence time.
- If disc rotates and it is coupled with upper spindle, it also start rotating & close the trip circuit contact. At that time the restraining device provided by voltage element is let down the driving torque produce by current element.
- The speed of operation is depends upon operating current and the time of operation of relay is directly proportional to the pull by voltage restraining element.

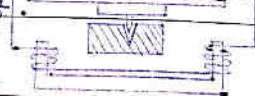

→ Therefore the time of operation depends upon both voltage & current.
$$T \propto \frac{V}{I} \propto Z$$

$$Z = (\text{impedance of certain distance upto point of fault}).$$


Date: 14/03/2019

Differential Relay


- Most of the relay which are discussed work on excess of current.
- This relays are less sensitive because they cannot make distinction between heavy load condition & minor-fault condition.
- So a differential relay is one that operated when the phase difference of 2 or more similar electrical quantities exceed a pre-determined value.
- So there are 2 types of differential relays, i.e. Current differential relay & voltage differential relay.

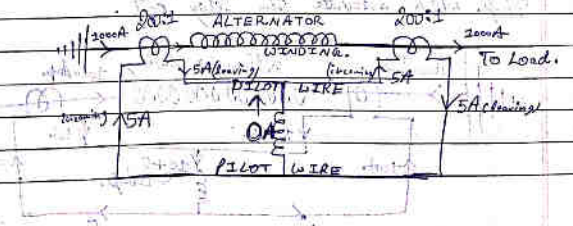(i) Current Differential Relay → It is one which compare the current entering a section of the SF with the current leaving the section.


- Under normal operating condition the 2 currents are equal but at time of fault occur this condition is no longer stable.
- This difference of current flow through the relay coil, which cause operating or pick-up of relay.



- The above diagram shows an overcurrent relay to operate as differential relay. A pair of identical C.T. are fitted on either side of the protected section (alternator winding).
- The secondary side of the C.T. are connected in series in such a way that they carry induced current in the same direction.
- Hence, in normal operating condⁿ no current flow through relay coil.
- Let the current 1000 Amp. out from alternator winding, the current in the 2 secondary C.T. are equal, their current will circulate between the C.T.'s and no current will flow through differential relay.
- Let a fault condition of alternator winding, if some current ground

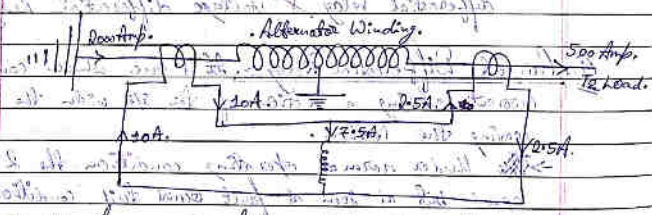

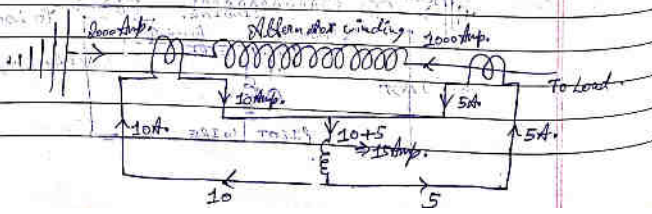
500amp. flow out of one side while the larger current 1000amp. enter the other side; hence the difference of C.T.'s current flow through relay coil is: $10 - 2.5 = 7.5$ Amp. which activate the relay coil.



→ If current flow to the fault from both side then the C.T. secondary's are drawn current 20amp. & 5amp. which flows through relay operating coil.

- Disadvantages- The Pilot wire's cause slightly difference both the current at the 2 end of the line to be protected; if the relay is very sensitive then it will operate even under no fault condition.
- The capacitance may be seen both pair of pilot wire cause in correct operation of the relay when large current is flowing.
- Accurate matching of C.T.'s cannot be achieved due to impedance of the pilot wire.

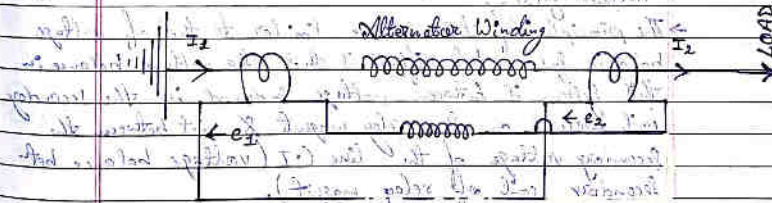Date 15/03/2019 * Voltage Balance Differential Relay *



- In this scheme of protection, two similar currents are connected at either end of the elements to be protected by means of pilot wires.
- The secondary of C.T.'s are connected in series with relay in such a way that under normal operating condition, their induced emf are in opposition hence no resultant emf.

- Under healthy condition ($I_1 = I_2$) & ($C_1 = C_2$) hence no resultant current flow through the relay coil.
- When fault occurs in the protected zone the current in the 2 primaries of the C.T(s) will differ from each other ($I_1 \neq I_2$).
- Hence secondary voltages no longer balanced to each other, which cause flowing of current through relay coil & trip the circuit.

* Disadvantages -


- A multipoint protection is required to achieve balance between C.T pairs.
- The system is suitable for protection of cable of relatively short length because longer length cable shows capacitance drop across the line.

* Translay Scheme - It is the modified form of voltage balance system.

The principle of this scheme similar to that of voltage balance system but different is that the voltage balance in this system is between voltage induced in the secondary coil winding on the relay magnet & not between the secondary voltage of the line C.T (voltage balance between secondary coil of relay magnet).

It consists of two identical double-winding induction type relay fitted in either side of the feeder to be protected.

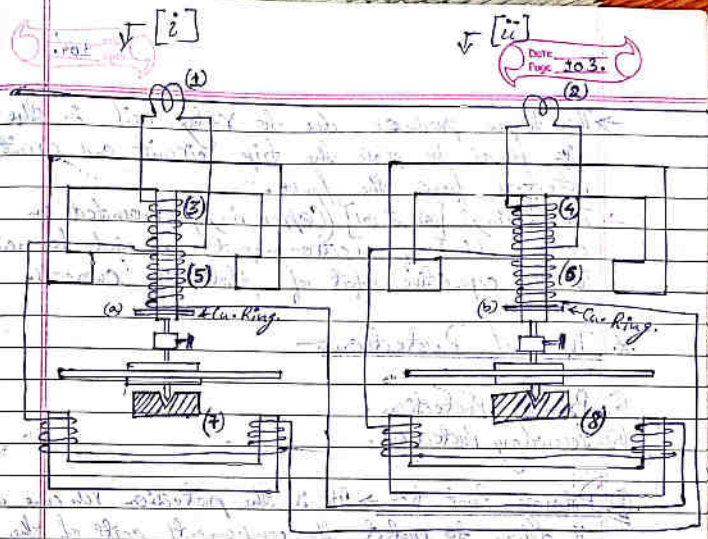The primary ckt. of the relays are supplied through a pair of C.T's where at the secondary winding of 2 relays connected in series by pilot wire in such a way that the voltage induced in the former opposes to one another.



* Operation - Under normal operating condition 2 ends of the protected feeder is same & the primary winding of the relay carry the same current and hence equal voltage induced in the relay coils (3,4).

Date: 10/02/2024

The coil 3 & 4 induced equal emf in the secondary winding (5,6,7,8) coil.

→ All this windings are so connected that the induced emf are series opposition to each other. Hence no resultant emf and no resultant current in the pilot wire which cause no torque in the disc.


→ On occurrence of fault inside the protected zone, unequal voltage will be induced in the secondary winding of the relay hence current circulate in the pilot wire.

→ The force produce due to relay coil in the sh. disc tends to close the trip circuit and circuit protected from the fault.

→ The 2 rings (a) & (b) (Copper rings) mounted on central limb of electro-magnets are used to neutralise the capacitive effect of pilot wire circuits.

* Types of Protection:-

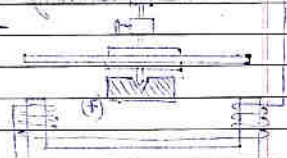- (a) Primary Protection.
- (b) Secondary Protection.



(i) Primary Protection → It is the protection scheme which is design to protect the component parts of the power system (alternator, X_r, feeder).

→ Each line has an overcurrent relay that protect the line. If a fault occurs in any line it will be cleared by relay & C.B. This forms the primary or main protection. It serves as 1st line of defence.

→ The service record of primary protection 90% of all operation being correct.

(ii) Back-up Protection → It is the 2nd line defence in case of failure of primary protection.

→ It is design to operate with sufficient time delay so that primary relaying will be given enough time to function if it is able to.

→ It is also over-current relay having time delay of nearly about 0.6 second.

* Protection of Alternator & X_r:-

→ The power system consists of several elements like alternator, X_r, Station Bus-Bars, transmission line and other equipments.

→ This equipments are desirable and necessary to protect from several and variety of faults.

→ The most severe fault occur in the X_r & alternators due to S.C. So we use several protection techniques for above equipments.

Protection of Alternator:-

→ Alternators are 3φ ac generating equipments. So they are different imp. faults may occur on an alternator that are:

- (i) Failure of prime mover.
- (ii) Failure of fields.
- (iii) Overcurrent.
- (iv) Over speed.
- (v) Over voltage.
- (vi) Unbalance loading.
- (vii) Stator winding faults.

(i) Failure of Prime Mover

When input to the alternator or prime-mover ~~some~~ fails, the alternator runs as synchronous motor and draws some current from supply system. This condition is known as inverted running.

In case of turbo-alternator sets failure of steam supply may cause inverted running, so steam supply is gradually restored, the alternator with pick-up load without disturbing the system.

If the steam failure is likely to be prolonged, the machine can be safely isolated by control room attendant.

In case of hydro-electric power plant protection against inverted running is achieved by providing mechanical devices on the water wheel.

If the water flow drops to a insufficient rate to maintain, the electrical output, the alternator is disconnected from the system.

(ii) Failure of Field - The chances of field failure in an alternator is very rare. If it does occur, no immediate damage will be caused by permitting the alternator to run without a field for a short period.

If the fault is continue for a long time, the control room attendant advise to disconnect faulty alternator manually from the system bus-bar. So no automatic protection provided to this type of fault.


(iii) Over Current - It occurs mainly due to partial break-down of winding insulation or due to overload on the supply system. The alternator now a days so design that, they have very high value of internal impedance (synchronous impedance),

so that they will stand against complete short ckt and there terminals for sufficient time without serious overheating. If over load occurs the alternator dis connected manually. In this type of alternator protection in case of a power-plant cause interfering of continuity of supply.

(iv) Over Speed - The chief cause of over-speed is the sudden loss of all or major part of the load on the alternator. So the modern alternators are usually provided with centrifugal mechanical devices mounted on the same (driving) shaft to trip the main valve of the prime mover and avoid dangerous over speed occur.

(v) Over Voltage - The over voltage in an alternator occurs when speed of the prime mover increases or due to sudden loss of the alternator load. So the field excitation system of alternator is so design that over voltage condition at normal running speed cannot be occur.

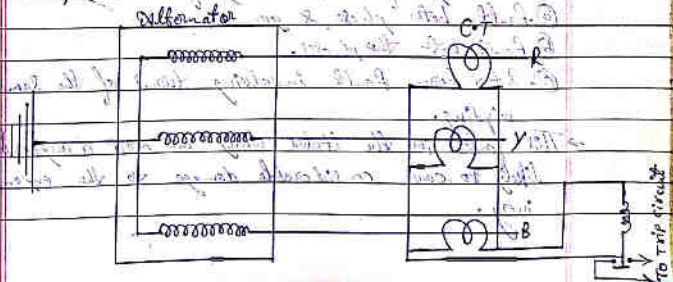(vi) Unbalanced Loadings - It means that there are different phase current in the all three phases. The unbalanced loading arises from faults to earth or faults between phases on the circuit external to the alternator.



→ For avoid unbalance loading in an alternator this protection scheme is use. In this scheme there are 3 line C.T's are mounted on each phase and the secondary of this C.T's are connected in parallel.

→ A relay is connected across the $\sqrt{3}$ secondary in parallel.

→ Under normal operating condition, equal current flow through the different phases of alternator.

→ Hence algebraic sum of currents of each phase is equal to zero. Hence no current flow through the neutral wire.

→ Hence, there is no current flow through C.T secondary and relay coil and relay is inoperated.

→ However if unbalance occurs the current induced in the secondary will be different. Hence resultant current flows across the C.T secondary and relay coil, and relay starts operate and trip the C.B. and disconnected the load from alternator.

→ The above faults are (i) to (v) are external faults to the alternator.

(vi) Stator Winding faults (Internal faults):


→ The stator winding faults mainly due to the insulation failure of the stator winding.

→ The main types of stator winding faults are:

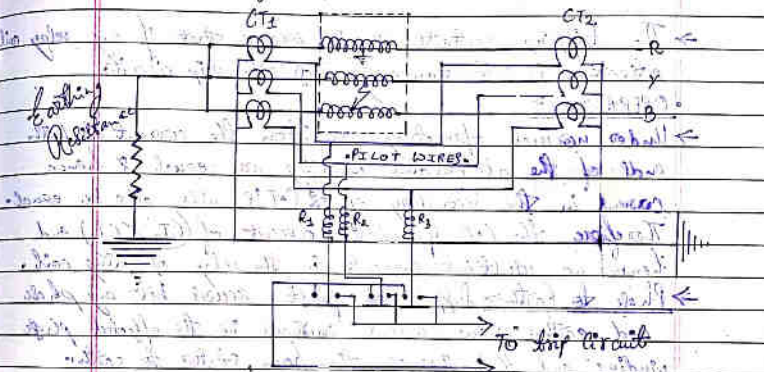- (a) Fault between phase & ground.
- (b) Fault between the phases.
- (c) Inter turn fault involving turns of the same phase winding.

→ This faults in the stator windings are most dangerous and likely to cause considerable damage to the expensive machine.

→ Therefore, automatic protection scheme is absolutely necessary for protection of alternator against such faults, differential method of protection is used (Merz-Price scheme).



MERZ-PRICE SCHEME (above figure)
(Merz-Price Protection Scheme / Differential method of protection)

INTRODUCTION
 → This is the most common type of protection of stator winding fault employed circulating current principle.

CONSTRUCTION
 → The arrangement shows 2 identical C.T pair (C.T-1 & C.T-2) which are placed on either side of the each phase winding (stator).

→ The secondary of each set of C.T are connected in star, the neutral points of corresponding terminals of the 2 star groups are being connected together by means of 4 pilot wires.

→ Therefore, an independent path for the current circulation is provided for each pair of C.T corresponding to pilot wire (D).

→ The Relay coils are connected in star, neutral point being connected to the C.T. common neutral and the other ends are to each of the other 3-pilot wires.

→ The tripping contacts are so arranged that if any relay coil activate, it instantaneously stops the trip circuit.

OPERATION →

→ Under normal operating condition the current at both ends of the alternator winding are equal & hence current in the secondary of 2 C.T.'s will also be equal. Therefore the C.T. secondary current of (C.T. X C.T.) and hence no resultant current in the relay operating coil.

→ Phase to earth → Suppose fault occurs between any phase and earth. Now current in the affected phase winding and flows through the frame, station to earth.

→ Hence the current in the secondary of 2 C.T.'s are unequal (empty current ≠ living current).

→ So the difference of 2 unequal current of 2 C.T.'s are flow through affected phase relay coil cause tripping of C.T.

→ If fault occurs between any 2 phases (P.C.) - Hence current in the affected phases on both sides of alternator are unequal, corresponding C.T. secondary current also unequal cause circulating current in the pilot wires and flow through protective relay coil, which the trip contact of the C.B.

→ It may be noted that the relay circuit is so arranged that if it energised (relay coil) cause opening of the C.B. connected to the alternator B.W. Bus and opening of the field circuit of the alternator.

* Protection of transformers - X^r are static device which are enclosed and generally well-merged. So chance of fault occurring are very rare.

→ If fault occurs then X^r is quickly disconnected from the supply so automatic protection systems are design for protection of X^r.

→ For small distribution X^r are connected to the supply through series fuses instead of C.B. However, for power X^r probability of fault is high so automatic protection systems are necessary.

→ Common X^r faults are: Open circuit fault; Over-heating fault (over-load); winding short circuit (intentional faults); phase to earth fault; phase to phase fault.

→ An open ckt in case of a 3φ X^r may cause undesirable heating so relay protection is not provided against open-ckt. i.e. ~~accidental~~ the X^r is simply disconnected on occurrence of open-ckt fault.


→ The over heating of the X^r usually caused by detained over-load or short-ckt or occasionally failure of cooling system. So relay protection is provided with thermal over-rides, and sound alarm & fan.

→ In case of winding short-circuit the X^r simply disconnected quickly by automatic relay protection. If otherwise it may cause explosion.

* Protection of X^r :- For protection of power X^r more precise circulating scheme is highly necessary. besides that scheme other protective equipments are used for X^r.

- (i) Buchholz's Relay
- (ii) Earth-fault Relay
- (iii) Over-current Relay
- (iv) Differential System (Merz-Price)

Buchholz Relay

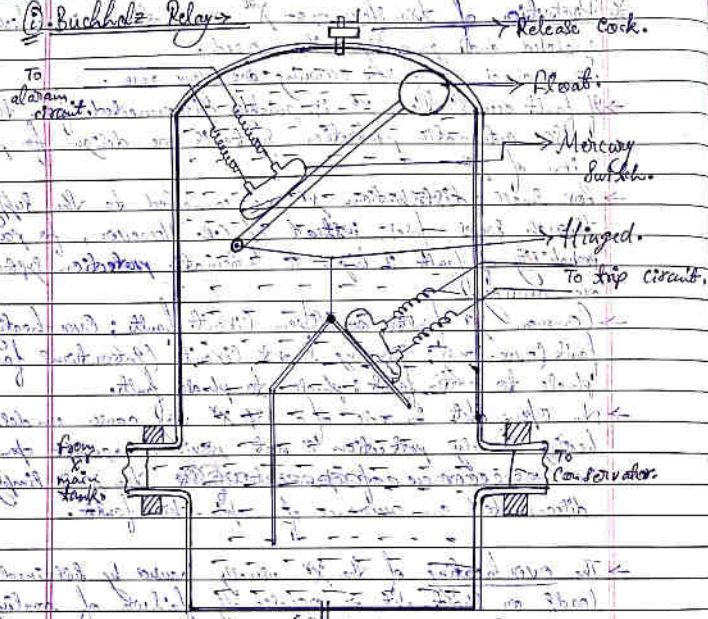

→ It is a gas actuated relay installed in oil emerged XL for protection against all kinds of faults.

→ This relay use to give an alarm during incipient fault (slow developing fault) and disconnect the XL during severe fault.

→ It is install in the pipe between conservator & main tank.

→ The Buchholz relay are generally used for XL protection above 750 KVA.

Construction

→ It is a dome shaped vessel type having 2 elements: upper & lower element; the upper element consists of mercury switch attach to a float.

→ The lower element consists of a hinged type flap attach to a mercury switch placed in the direct pipe between conservator & main tank.

Operation

→ In case of a incipient fault heat is produced in the oil and decompose the oil of the main tank, so 70% due to decomposition of H_2 it is produced which is a light gas and tend to go top of the chamber.

→ Now the gas surrounded the float and produced pressure which cause tilt of mercury switch and close the alarm ckt contact.

→ If a minor fault occur (plate to plate (or) plate to earth fault) then enormous amount of heat is generated and oil start rising towards main tank to conservator tank and tilt the flap of well of mercury switch which close the trip ckt contact and C.B disconnected the XL.

Advantages & Disadvantages


Advantages

- It is the simplest form of XL protection.
- It is able to detect smaller incipient fault.

Disadvantages

- This is only used for oil emerged type XL.
- It only detect fault below oil level in the XL, so separate protection is needed for connecting cables.

(ii) Earth fault (or) Leakage Protection

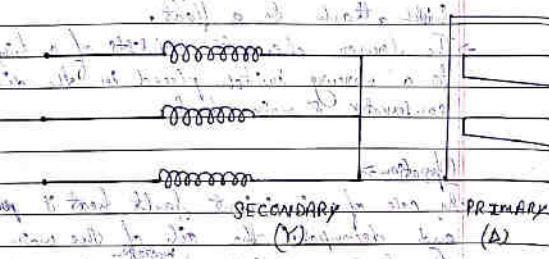


(Figure)

INTRODUCTION

- The earth-fault indicates partial break-down of insulating low-voltage, insulating material.
- The resulting leakage current is considerably less than that of SC current.
- This type of fault continues for a long time and cause considerable damage before it ultimately develops SC and removed for the system.
- So in this condition earth fault relay is profitable and disconnect the line when fault initiated.
- It is a over-current relay having low setting (PSM).

CONSTRUCTION

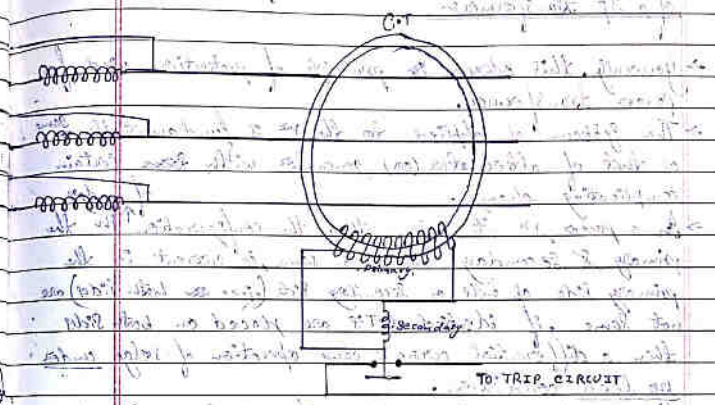- The 3φ leads of the line and of power are taken through core of the C.T. which carry a single secondary winding.
- The operating coil of the relay is connected to dual secondary winding.
- The relay operating coil carries pair of stripping contacts.



OPERATION

- Under normal operating condition the vector sum of 3φ primary wind current are equal to zero.
- Hence no resultant current in the core & flux produced in the core of the C.T.
- $I_1 + I_2 + I_3 = 0$
- At time of fault occurs both earth & wind due to insulation failure the vector sum of 3φ current is no longer zero.
- Hence resultant current set-up a flux in the core of the C.T. and induced emf in the secondary windg. of C.T. which energized relay operating coil and trip the C.B. to open.


Δ	Δ	Y	Y	1
Y	Y	Δ	Δ	2
Y	Δ	Δ	Y	3
Δ	Y	Y	Δ	4

* Mho-Price Protection Scheme (or) Differential protection scheme of a 3 ϕ transformer

- Generally, this scheme is principle of protection used for power transformer.
- The system as applied to the $\Delta-\Delta$ is fundamentally same as that of alternator (or) generator with some certain complicating change.
- In a power $\Delta-\Delta$ it is seen that the configuration of windings in the primary & secondary are not same, so current in the primary side of coil or secondary side (i.e. on both sides) are not same, if identical C.T's are placed on both sides then a differential current cause operation of relay under no load condition.
- This can be avoid by mounting different turn ratio C.T's both on primary & secondary side of the power $\Delta-\Delta$.
- There is usually phase difference betⁿ primary & secondary currents in case of a 3 ϕ transformer even if C.T's are different and proper turn ratio and cause differential current flow through relay coil during normal operating conditions. So, this phase difference of current avoided by appropriate connection of C.T's on both side of the $\Delta-\Delta$. Hence different connections of C.T's are employed for current match-up on both sides.

Sl. No.	Power Transformer's		C.T's	
	Primary	Secondary	Primary	Secondary
1.	Y	Y	Δ	Δ
2.	Δ	Δ	Y	Y
3.	Y	Δ	Δ	Y
4.	Δ	Y	Y	Δ

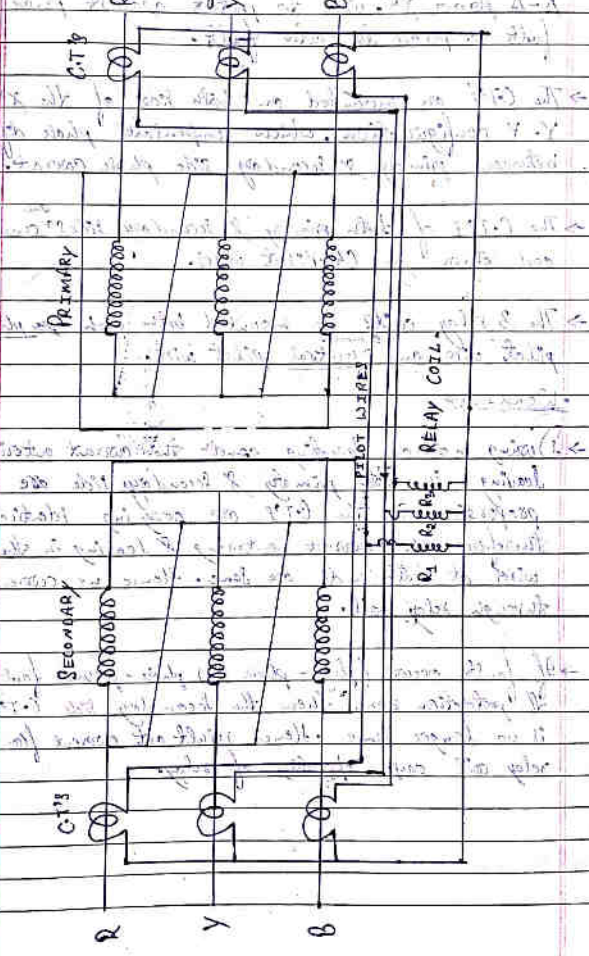* Circulating Current Scheme / Differential Scheme / Mho-Price Scheme of a $\Delta-\Delta$ $\Delta-\Delta$




CONSTRUCTION →

Protection

- The diagram shows Mosez-Price scheme / Circulating-current scheme / Differential-protection scheme of a 3φ Δ-Δ power x^m, used to protect against phase-phase fault or phase-to-earth fault.
- The C.T's are provided on both side of the x^m are of Y-Y configuration, which compensates phase difference between primary & secondary side phase currents.
- The C.T's of both primary & secondary sides are connected to each other by 04-pilot wires.
- The 3 relay coils are mounted both ends ~~per phase~~ ^{common} of pilot wire and neutral pilot wire.

WORKING →

- During normal operating condⁿ the current entering & leaving in both primary & secondary side are same proportion; so the C.T's are carrying identical current; therefore the current entering & leaving in the pilot wire at both ends are same. Hence no current flow through relay coil.
- If fault occurs (phase-phase or phase-ground fault) inside the protection zone then the secondary side C.T's current is no longer same. Hence result net current flow through relay coil causing operating of relay.

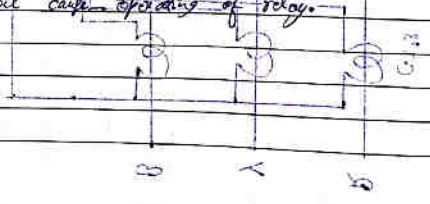

Protection against Over-voltage (Voltage Surges)

- A sudden rise of voltage for a short period (from normal value) in the power system is known as over voltage/voltage surge or, transient voltage.
- * Causes of Over-voltage - There are 2 cause i.e.
 - ① internal cause.
 - ② external cause.
- ① Internal Cause / Reason - Internal reasons are as follows:
 - Switching surge.
 - Insulation failure.
 - Arcing ground.
 - Resonance.


② External Cause - The internal cause are avoided by suitable design of power system equipment.

- Lightning → An electric discharge between cloud & earth, between clouds or between and charge centres of the same cloud is known as lightning.
- lightning is huge spark between clouds & earth or neighbouring clouds due to breakdown of dielectric strength of the air.
- The most accepted theory for explain how cloud acquired charge is that; during uprush of warm moist air from the earth, the friction between the air & tiny particles of water caused the building-up of charges.
- When drops of water are form the larger drop became (+vely) charged & the smaller charge drops became (-vely) charged.

- When the droplets of water are accumulated they ~~flow~~ form cloud and hence clouds may posses +vely or -vely charge.
- The charge of the clouds may be so large that it cause discharge between earth or other clouds seen as a lightning.
- Due to lightning the air suddenly heats up and cooling it to expand. ~~due~~ so the surrounding air pushes the expanded air back and which cooling wave motion of the air recognised as a thunder.

Mechanism of lightning Discharges

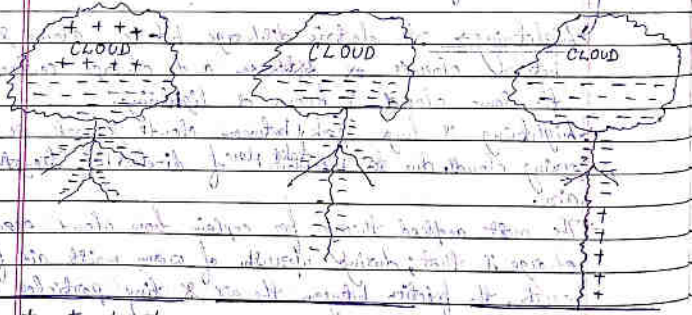- When charge cloud passes through the earth it ~~induce~~ induced equal and opposite charge.
- The charge acquired by the cloud increases the potential gradient and if it is sufficient $[15kV/cm]$ to $[30kV/cm]$ than the surrounding air get breakdown and lightning stroke starts



(i) As soon as the air near the cloud get breaks they charge streamer known as Pilot/Leader streamer starts from cloud towards earth and if still potential gradient is maintained in the tip of the streamer then it complete the journey towards earth otherwise incomplete.

(ii) In some cases the leader streamer ~~may~~ continue its journey towards earth and comes in contact with earth or some object. Hence during the path several points of luminance which looks like stepped ^{leaders} and each step about 50m distance from each other.

(iii) If path of the streamer leader is so ionised that complete breakdown of air insulation, leader streamer reaches the earth and a return streamer shoots up from the earth towards the cloud in the same path. This action can be compared with a closing of a switch between (+ve) & (-ve) terminal which causes sudden spark and we called as high stroke lightning/heavy lightning.

Once it starts complete break-down of air occurs which follows path of heavy lightning.

→ The time required for travelling the charge towards earth is about 0.0005 sec. to 0.5 sec.


→ 87% of all lightning stroke results from (-vely) charge clouds only 13% originated from (+vely) charge clouds.

→ It has been estimated that through out the world there are 100 lightning strokes occur per second.

→ One lightning discharge may have current in the range of 10kAmp to 90kAmp.

→ There are 2 types of lightning stroke; Direct stroke and indirect stroke.

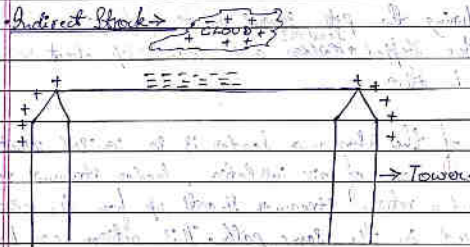Direct Stroke → In this type of stroke the lightning discharge is directly from the cloud to the subject equipment (tree, overhead lines, towers) and the overvoltage occurs across insulator which cause flash over.



→ This type of stroke results electro-statically induced charge on the conductor due to presence of charge cloud.
 → If truly charge cloud above the conductor then due to electro static force the (+ve) charge start gather below charge cloud & the (+ve) charge can leak through earth via insulator when the charge cloud diffused now the (+ve) charge can not flow to the earth over the insulator and travel along the line in both direction looking like travelling wave.

- * Protection against lightning → Due to lightning over voltage occurs near equipments and may damage these expensive equipments. In order to avoid lightning stroke most commonly used devices are:
- Lightning screen.
 - Over-head ground wires.
 - Lightning arrester.

Earthing screen → The power station or grid sub-station generally having expensive equipment so in order to protect against lightning stroke earthing screen is provided. It consists of a network of Cu-conductor mounted all over the electrical equipment in the sub-station and this network properly connected to earth at least two points through low impedance which provides low resistance path to the lightning stroke.

Over-head ground wire → The most effective method of providing protection against lightning stroke in over-head transmission line is over-head ground wire.


The over-head ground wire are placed above the line conductor or top of the tower at such a position that practically all lightning stroke are intercepted by them.

→ When direct lightning stroke occur at transmission line heavy current, 10 KAmp. to 90 KAmp. flow from ground wire to ground through tower & footing resistance such that the flash over voltage (voltage between cross-arm & conductor near insulator) is less high as compare to voltage between ground wire to ground.

→ For proper discharge the footing resistance should be kept low value and doesn't allow discharge through line conductor.

Lightning arrester → Lightning arrester is a surge diverter or a protective device which conducts the high voltage surge on the power system to the ground.

Principle → $\frac{V}{R} < I$

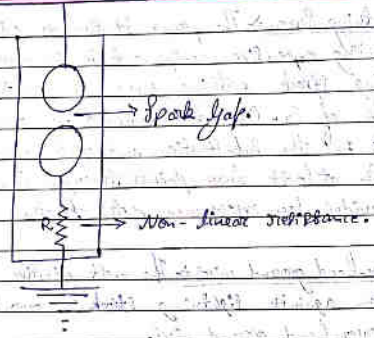

Principle


- The lightning arrester consists of 2 conductors having a gap series with non-linear resistance. The gap is so adjusted that the normal system voltage doesn't produce any arc.
- The property of non-linear resistance is that the resistance decreases if the voltage increases and vice versa.
- So under normal operating condition LA remains OFF-circuit and no current flows to the earth.
- On occurrence of the lightning stroke the air between the gap becomes ionized due to high electro-static field and a arc is seen across the gap and the surge voltage discharges to the earth through non-linear low resistance.

* Types of LA's

① Rod gap arrester - The rod gap arrester is very simple construction which consists of two 1.5 square rod which are bent right angle with a gap between them. One rod is connected to the line of the distribution and the other is connected to the earth.

→ The distance between gap & insulator must not be less than 2/3rd of the gap length so that the arc that reaches the insulator and damage it.

$P > \frac{1}{3} U_0$

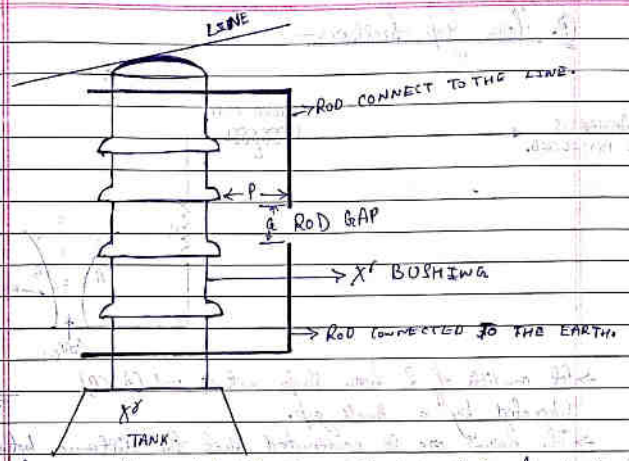

- Generally the gap length is so adjusted that the breakdown should occur at 80% of spark-over voltage in order to avoid cascading of very steep (steep) wave front across the insulator.
- Generally this type of arrester found across the bushing of the X'.
- Under normal operating condition the gap remains non-conducting, on the occurrence of high voltage surge the gap becomes conducting and large current conducted towards earth.

Limitation

- After surge voltage over the arc is maintained by the normal system voltage and S.C. of system may occur.
- The rod may melt or get damaged due to excessive heat produced by the arc.
- The climatic condition affect the performance of the arrester.
- The polarity of the surge also affects the performance of the arrester; due to this limitation this type of arrester is used for back-up protection.


Date 12/10/2019

R.S. Hoist pole

Date Page 126

② Horn gap arresters-

To APPARATUS TO BE PROTECTED.

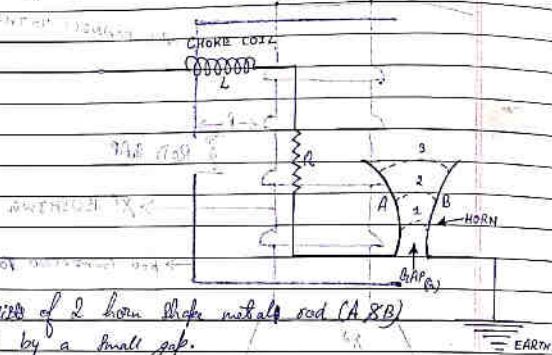

- It consists of 2 horn shape metal rod (A & B) separated by a small gap.
- The horns are so constructed that the distance between them gradually is greater towards top.
- This 2 horns are mounted on porcelain insulator.
- One end of the ~~line~~ horn is connected to the line through a resistor (R) & choke coil (L) whereas the other end of the horn is effectively grounded.
- The resistor (R) limit the flow of current to a small value whereas the choke coil (L) offer small reactance at normal power frequency but high reactance at transient frequency.
- The gap between the horns is so adjusted that the normal 90 voltage doesn't produce any spark or insufficient to produce arc.

Operation-

- Under normal operating condition the gap is non-conducting hence no arc produced across the gap.
- On the occurrence of over voltage, the air of the gap become ionised due to high electrostatic force and cause initiation of arc. The arc moves progressively into position (1, 2 & 3).

Date Page 127

- At some position of the arc (3-position) the gap is too long that ~~rather~~ the arc fails to maintain with that surge voltage and it become extinguished and excess charge moves to the ground.
- Advantages → The arc is self clearing, hence this type of arrester doesn't cause short circuiting of the system after clearing of voltage surge or fault.
- Series resistance help to limit flow of current to a small value and inductance (L) help to limit transient frequency.
- Disadvantages →
- The bridging of gap by some external agency (birds) can render the device useless.
- The setting of gap likely to be change due to corrosion or pitting (rusting).
- The time of operation is comparatively long about 3 seconds.