

Class Notes

PE&PLC (Theory)

Introduction to
Programmable Logic Controllers
(PLC'S)

Industrial Control Systems

Fall 2006

Aslis Dask

Lecturer

Electrical Engg

The Need for PLCs :-

- ⇒ Hardwired panels were very time consuming to wire, debug and change.
- ⇒ GM identified the following requirements for computer controllers to replace hardwired panels.
 - Solid-state not mechanical
 - Easy to modify input and output devices
 - Easily programmed and maintained by plant electricians
 - Be able to function in an industrial environment

The first Programmable Logic Controllers (PLCs)

- ⇒ Introduced in the late 1960's
- ⇒ Developed to offer the same functionality as the existing relay logic systems.
- ⇒ Programmable, reconfigurable and reliable
 - Could withstand a harsh industrial environment
 - They had no hard drive, they had battery backup
 - Could start in seconds
 - Used ladder logic for programming

Programmable Logic Controller :-


- ⇒ A programmable logic controller (PLC) is a specialized computer used to control machines and process.
- ⇒ It uses a programmable memory to store instructions and specific functions that include on/off control, timing, sequencing, arithmetic, and data handling.

Advantages of PLC Control System

- ⇒ Flexible
- ⇒ Faster response time
- ⇒ Less and simpler wiring
- ⇒ Solid-state - no moving parts
- ⇒ Modular design - easy to repair and expand
- ⇒ Handles much more complicated systems
- ⇒ Sophisticated instruction sets available
- ⇒ Allows for diagnostics "easy to troubleshoot"
- ⇒ Less expensive

Advantages of a PLC Control System

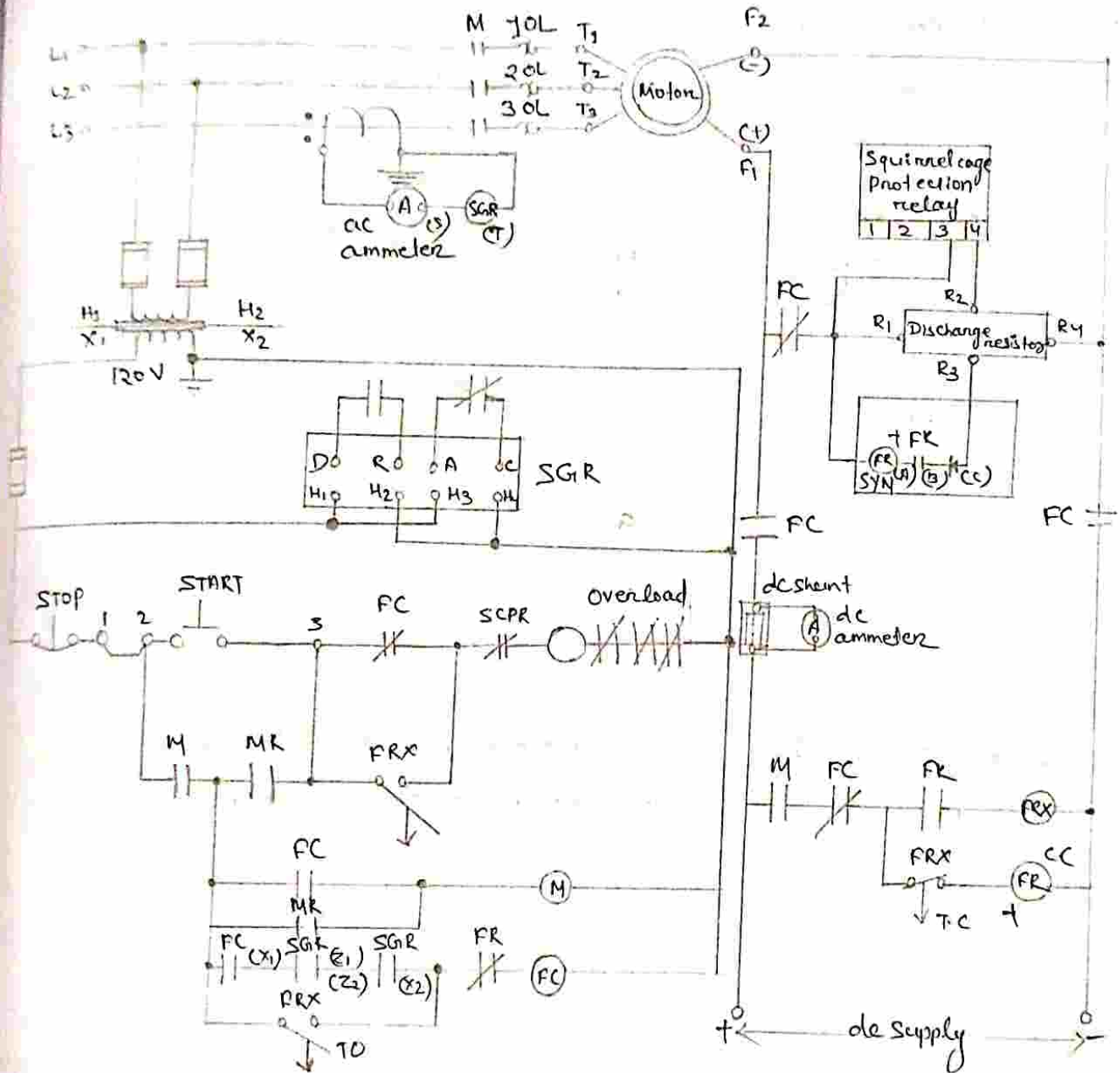Eliminates much of the hard wiring that was associated with conventional relay control circuits.




The program takes the place of much of the external wiring that would be required for control of a process.

Advantages of a PLC Control system

Increased Reliability

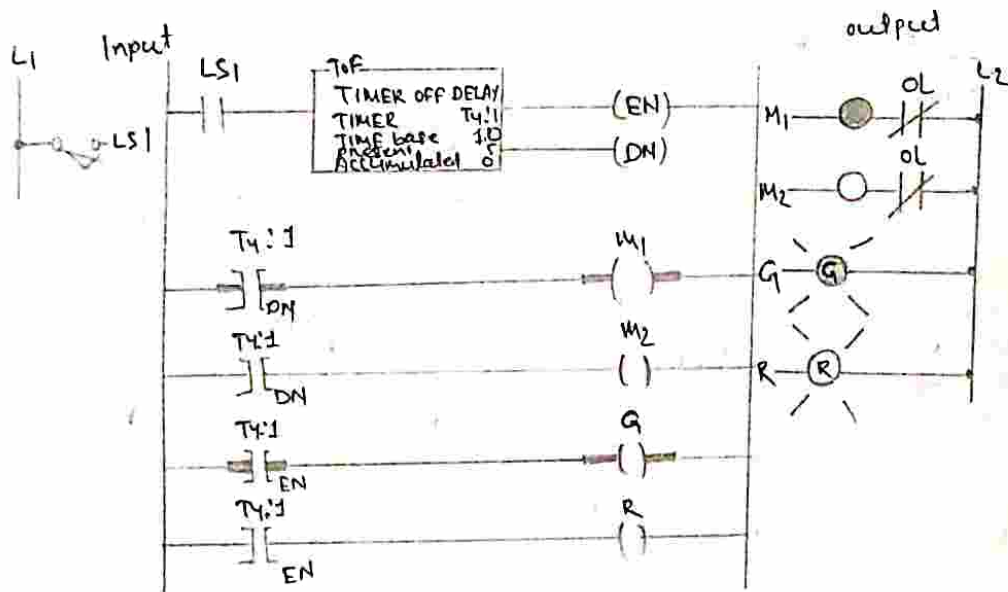Once a program has been written and tested it can be downloaded to other PLCs.




Since all the logic is contained in the PLC's memory, there is no chance of making a logic wiring error.

Conversely...

Advantages of a PLC Control system

More flexibility:

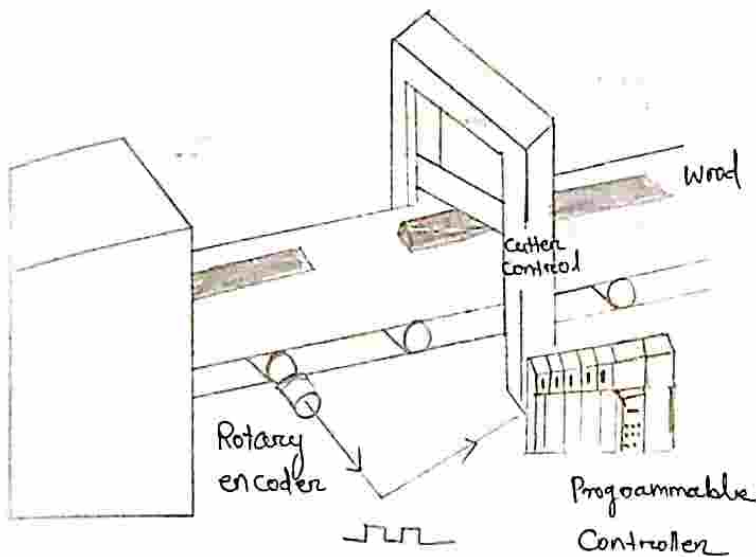Original equipment manufacturers (OEMs) can provide system updates for a process by simply sending out a new program.




It is easier to create and change a program in a PLC than to wire and rewire a circuit. End-users can modify the program in the field.

Advantages of a PLC Control system

Lower Costs:

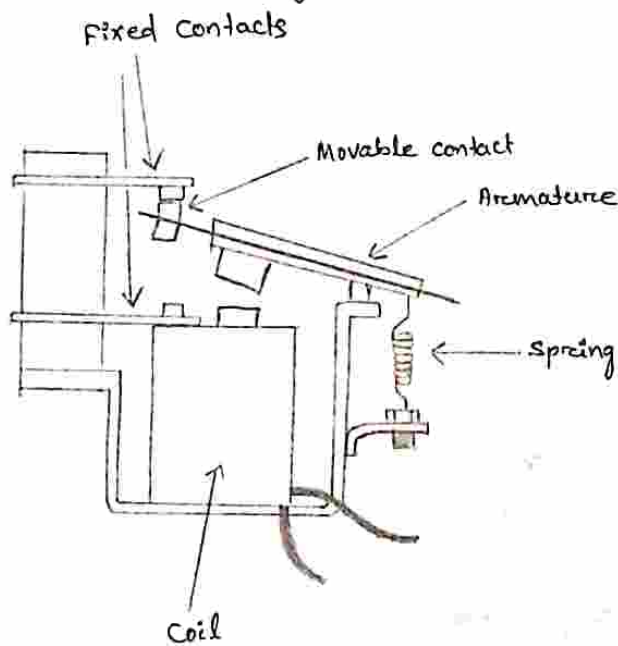Originally PLCs were designed to replace relay control logic. The cost saving using PLCs have been so significant that relay control is becoming obsolete, except for power applications.




Generally, if an application requires more than about 6 control relays, it will usually be less expensive to install a PLC.

Advantages of a PLC Control System

Communications Capability:

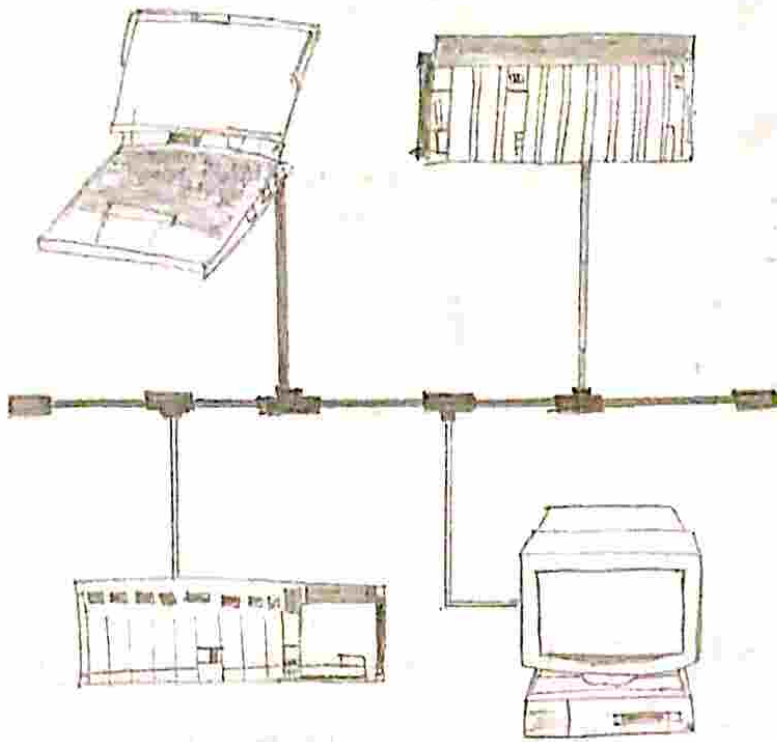A PLC can communicate with other Controller or Computer equipment.




They can be networked to perform such functions as:
Supervisory control, data gathering, monitoring devices and
Process parameters, and downloading and uploading of programs.

Advantages of a PLC Control System

Faster Response Time:

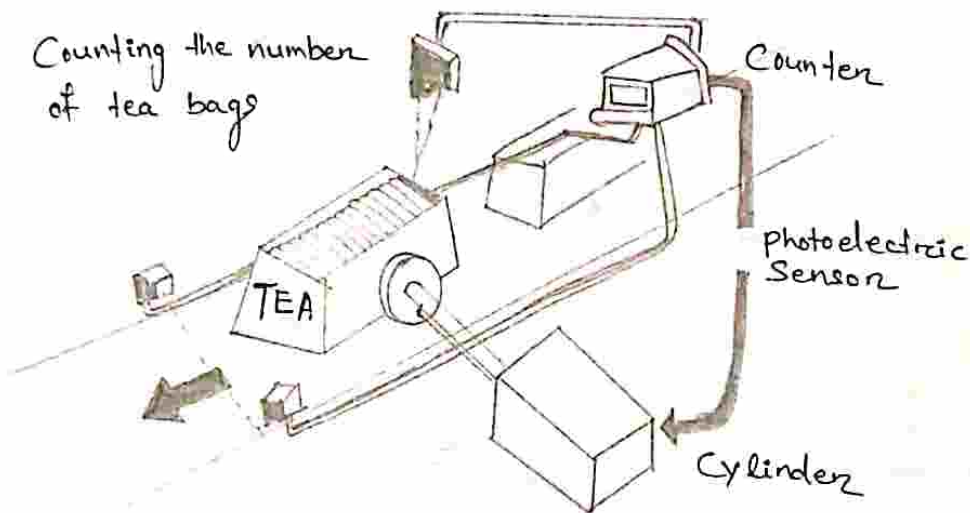PLCs operate in real-time which means that an event taking place in the field will result in an operation or output taking place.




Machines that process thousands of items per second and objects that spend only a fraction of a second in front of a sensor require the PLC's quick response capability.

Advantages of a PLC Control System


Easier To Troubleshoot:

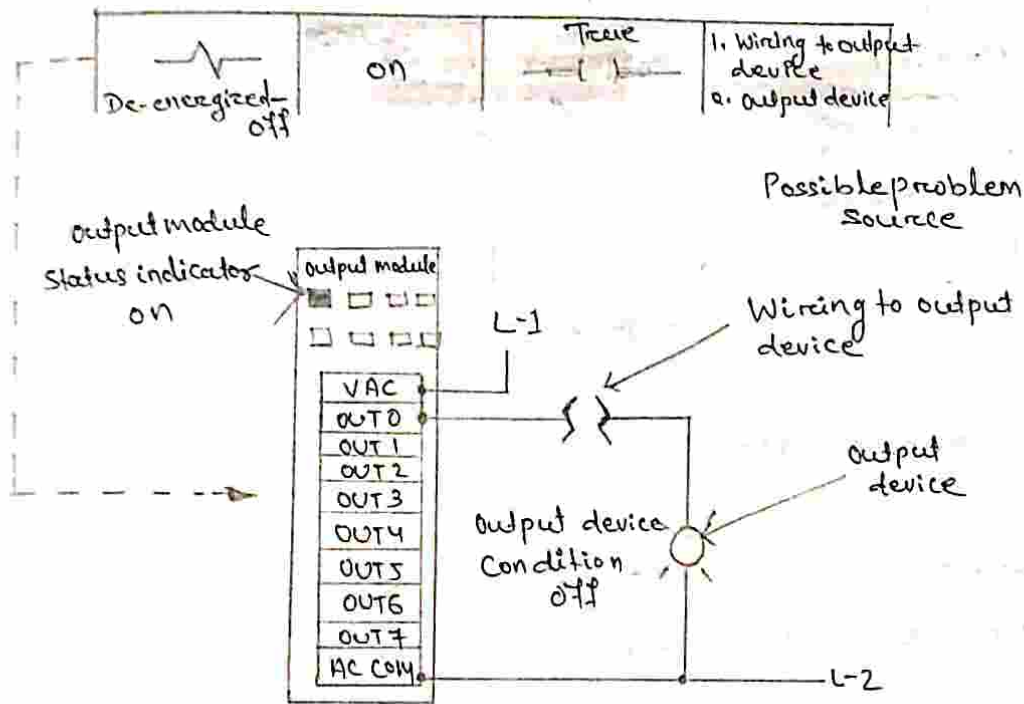PLCs have resident diagnostic and override functions allowing users to easily trace and correct software and hardware problems.




The Control program can be watched in real-time as it executes to find and fix problems.

PLC Architecture

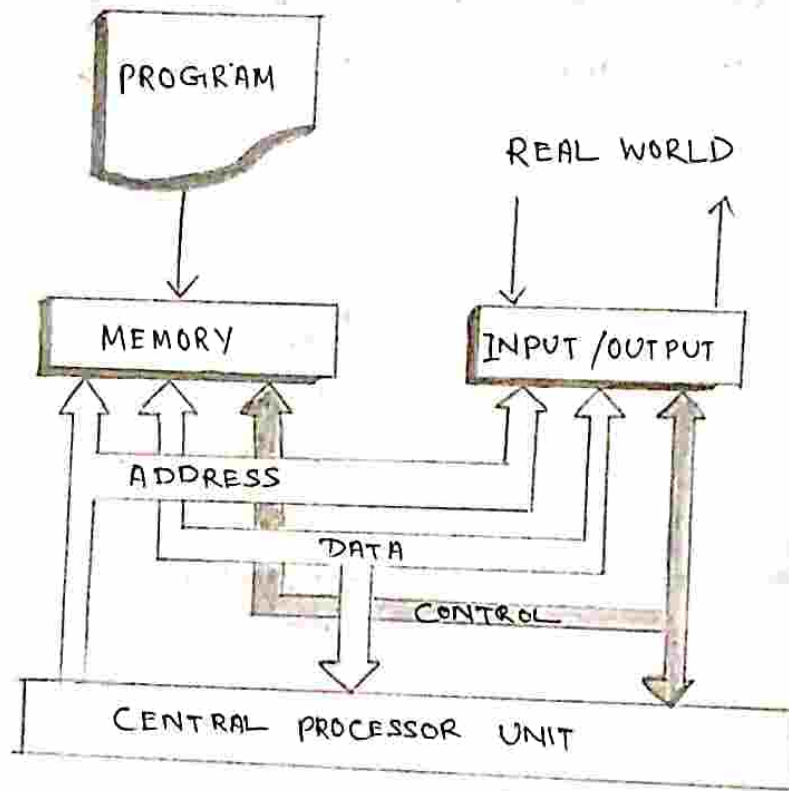

The structure of a PLC is based on the same principles as those employed in computer architecture.

PLC SYSTEM

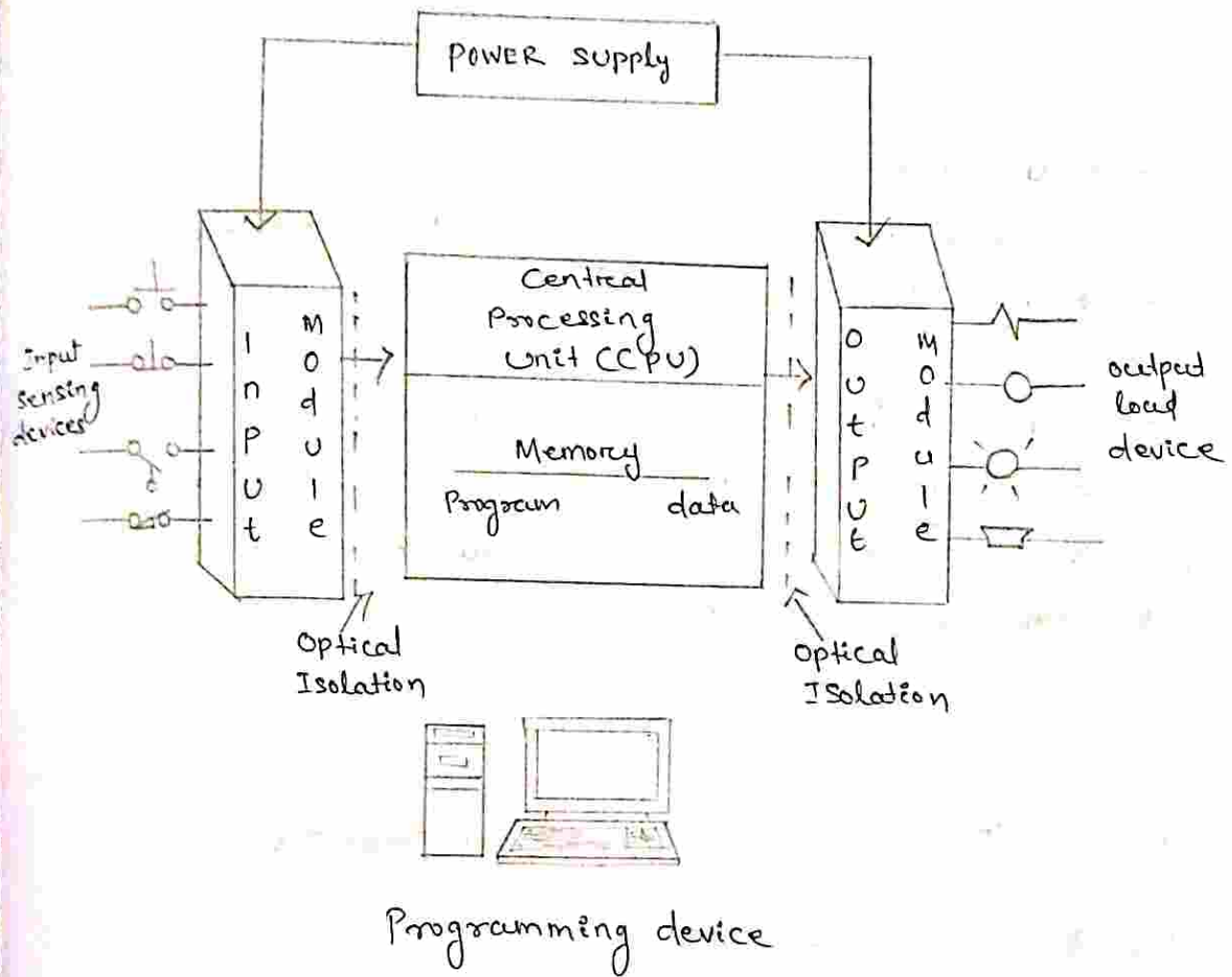

PLC Architecture

⇒ An open architecture design allows the system to be connected easily to devices and programs made by other manufacturers.

⇒ A closed architecture or proprietary system, is one whose design makes it more difficult to connect devices and programs made by other manufacturers.

NOTE: When working with PLC systems that are proprietary in nature you must be sure that any generic hardware or software you use is compatible with your particular PLC.

I/O Configuration


Fixed I/O

⇒ Is typical of small PLCs

⇒ Comes in one package, with no separate removable units.


⇒ The processor and I/O are packaged together.

⇒ Lower in cost - but lacks flexibility.

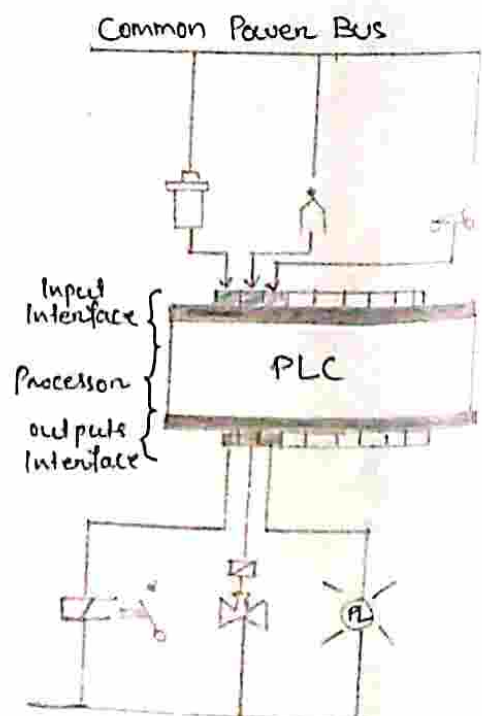

I/O Configuration

Modular I/O

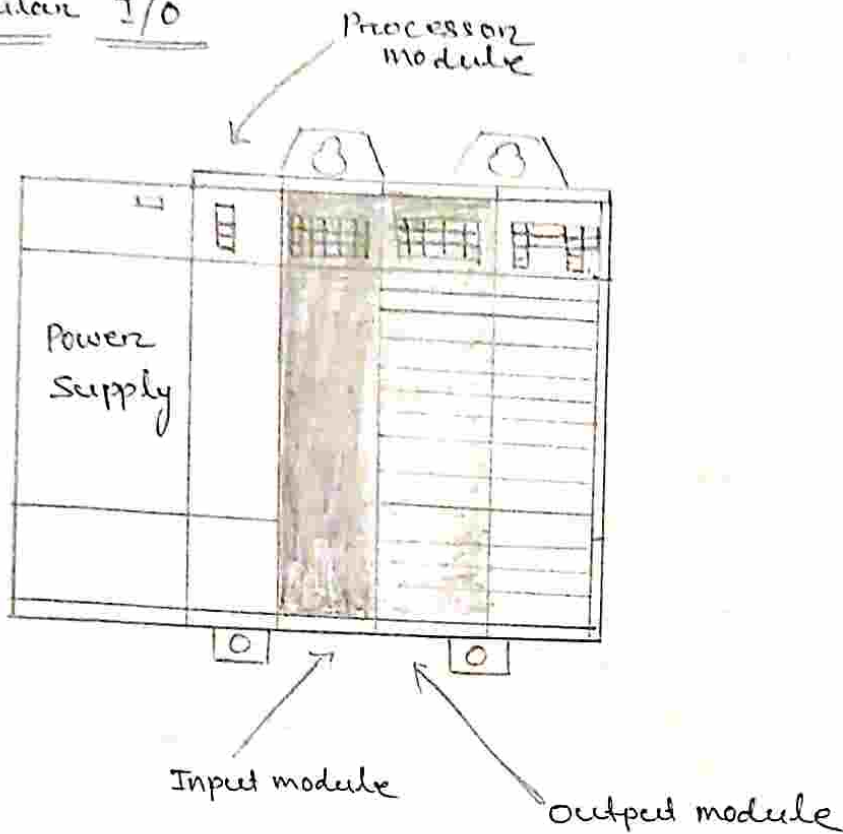


⇒ Is divided by compartments into which separate modules can be plugged.

⇒ This feature greatly increases your options and the unit's flexibility. You can choose from all the modules available and mix them in any way you desire.


I/O configurations

Modular I/O

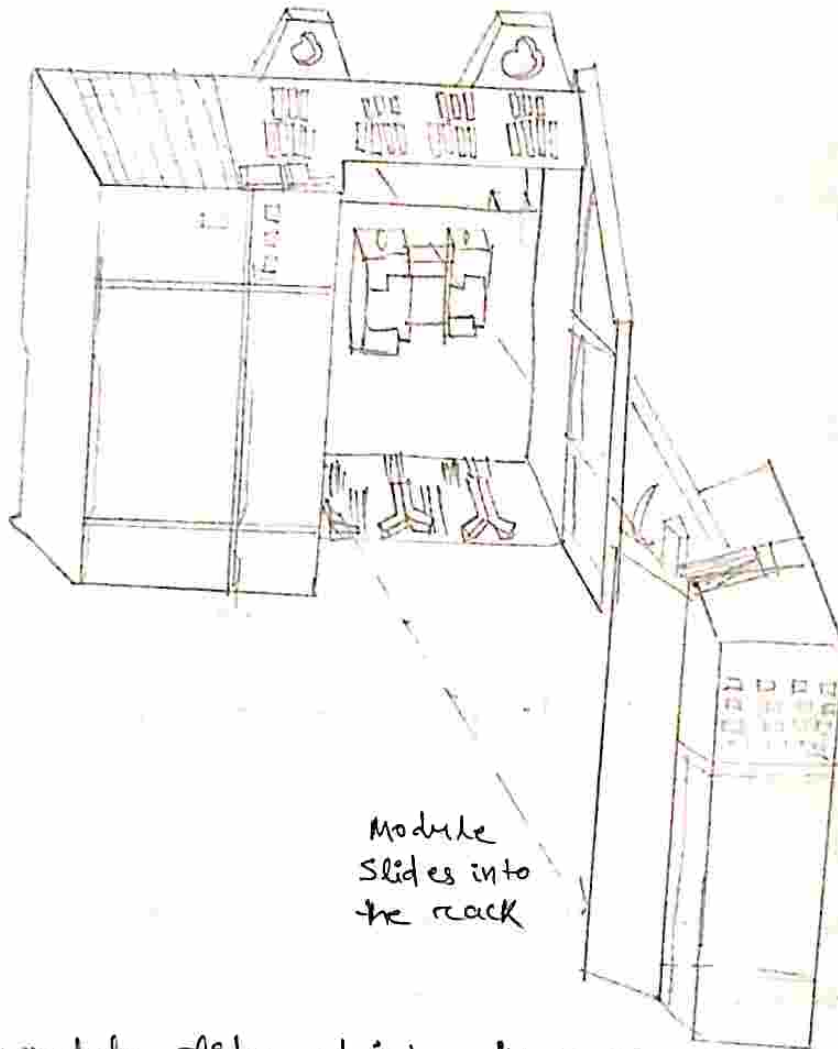


When a module slides into the rack, it makes an electrical connection with a series of contacts - called the backplane. The backplane is located at the rear of the rack.

Power supply

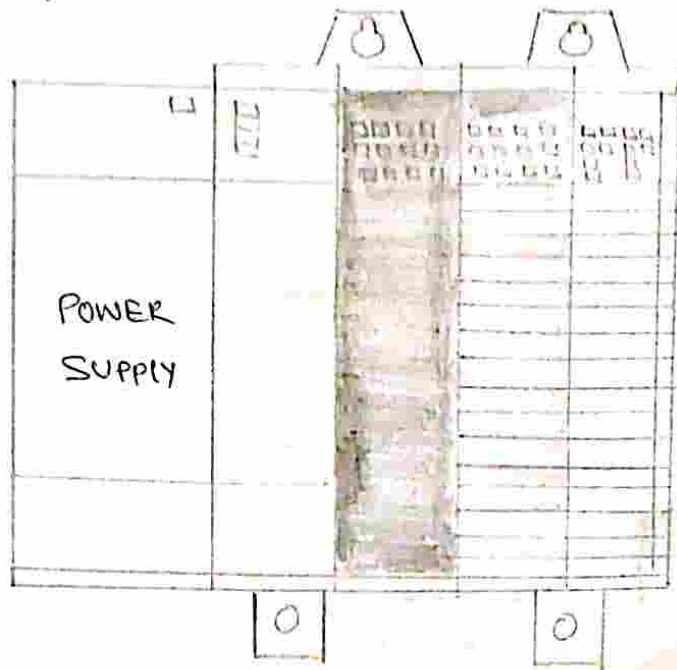

- ⇒ Supplies DC power to other modules that plug into the rack.
- ⇒ In large PLC systems, this power supply does not normally supply power to the field devices.
- ⇒ In small and micro PLC systems, the power supply is also used to power field devices.

Processor (CPU)

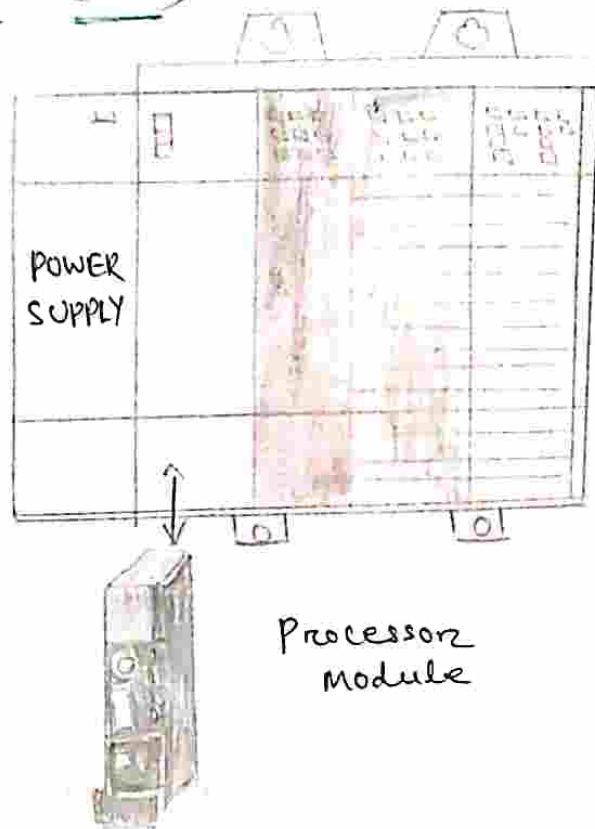


⇒ Is the "brain" of the PLC.

⇒ Consists of a microprocessor for implementing the logic, and controlling the communications among the modules.

⇒ Designed so the desired circuit can be entered in relay ladder logic form.

⇒ The processor accepts input data from various sensing devices, executes the stored user program, and sends appropriate output commands to control devices.

I/o Section

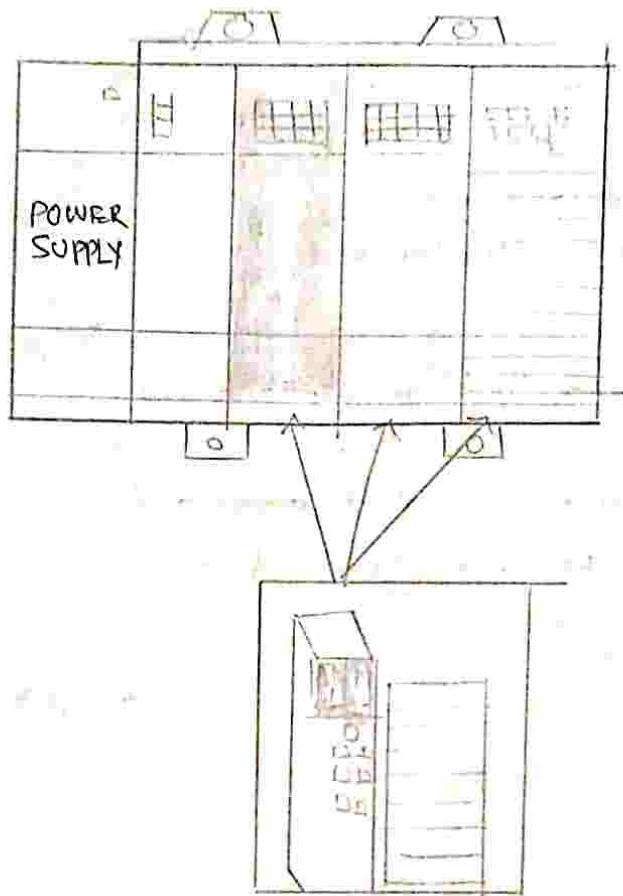

Consists of :

-> Input modules


-> Output modules.

I/O Section

Input Module

→ Forms the interface by which input field devices are connected to the controller.

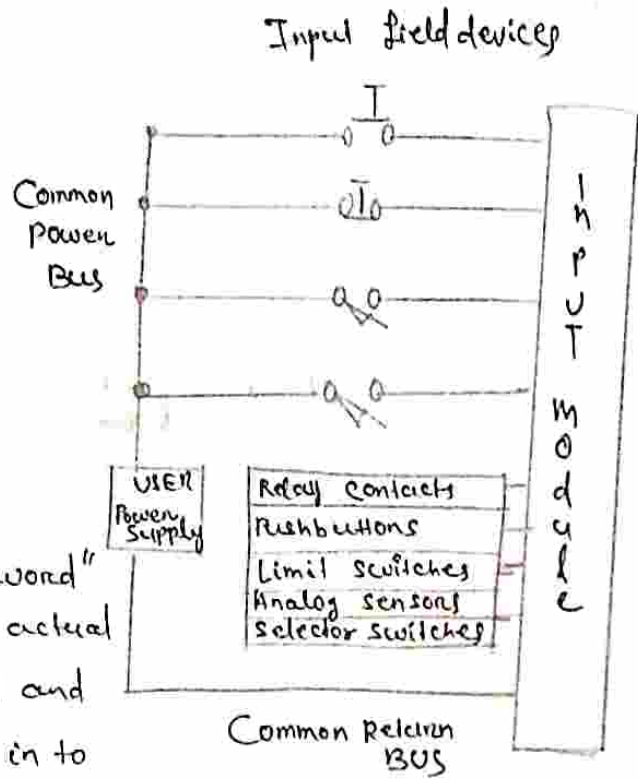→ The terms "field" and "real world" are used to distinguish actual external devices that exist and must be physically wired in to the system.




Output field devices


Output Module

→ Forms the interface by which output field devices are connected to the controller.

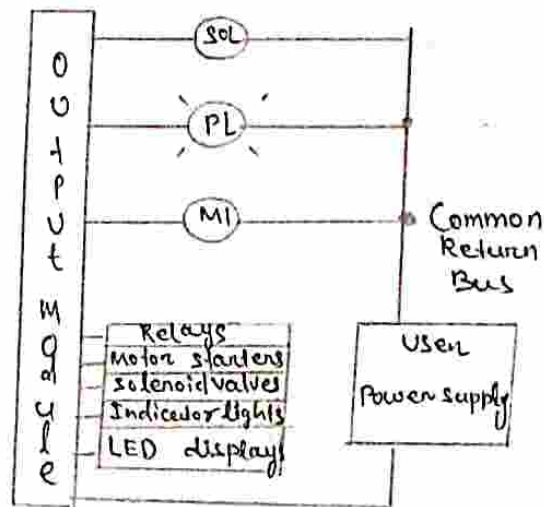→ PLCs employ an optical isolator which uses light to electrically isolate the internal components from the input and output terminals.




Programming Device

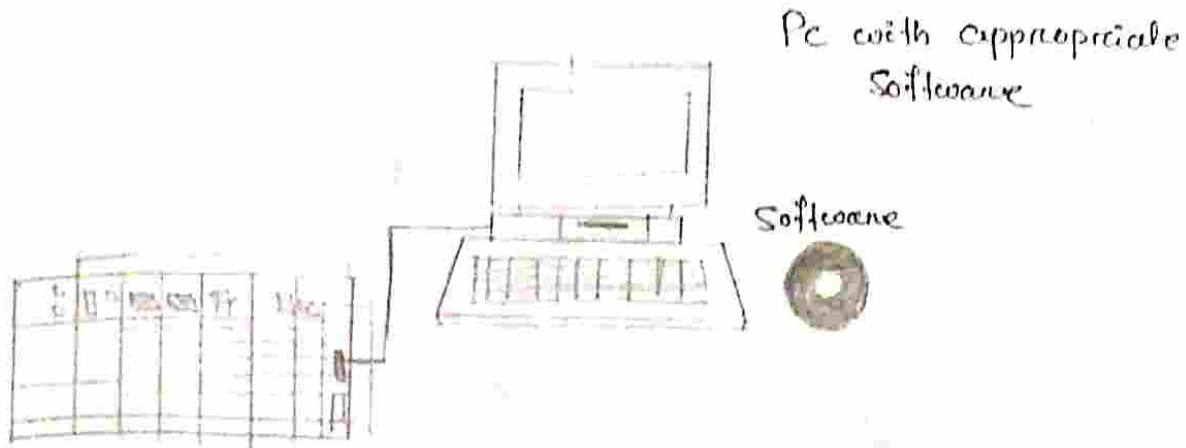

- ⇒ A personal Computer (PC) is the most commonly used Programming device.
- ⇒ The software allows users to create, edit, document, store and troubleshoot programs.
- ⇒ The personal computer communicates with the PLC processor via a serial or parallel data communications link.

Programming Device

Hand-held unit
with display

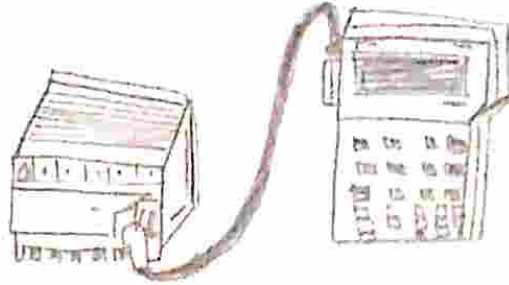


⇒ Hand-held programming devices are something used to program small PLCs.

→ They are compact, inexpensive, and easy to use, but are not able to display as much logic on screen as a computer monitor.

⇒ Hand-held units are often used on the factory floor for troubleshooting, modifying programs and transferring programs to multiple machines.

PLC Mixer process Control problem

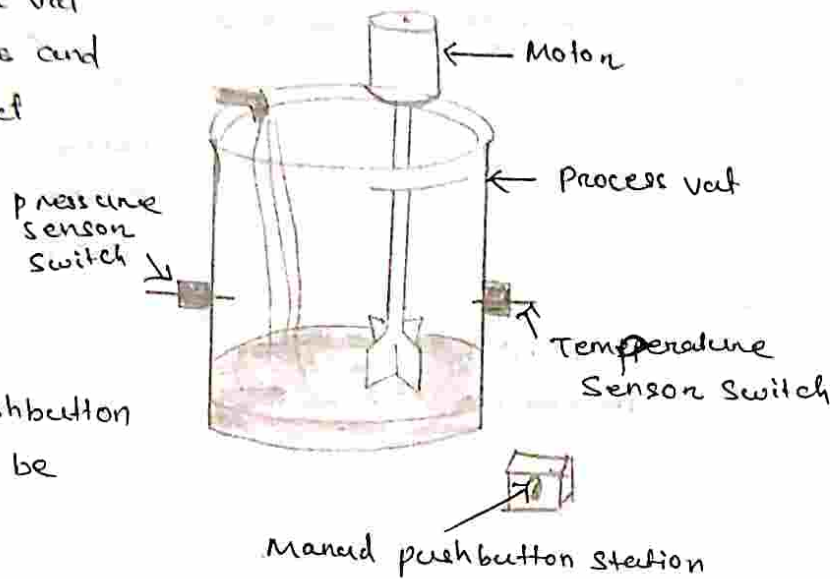
Mixer motor to automatically stir the liquid in the vat when the temperature and pressure reach preset values.



Alternate manual pushbutton control of the motor to be provided

The temperature and pressure sensor switches close their respective contacts when conditions reach their preset values.


Process Control Relay Ladder Diagram

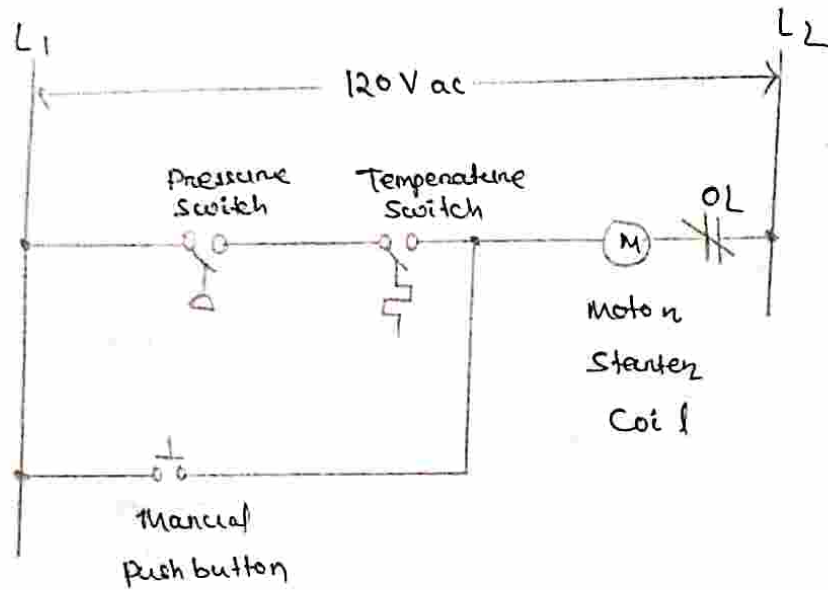

Motor Starter coil is energized when both the pressure and temperature switches are closed or when the manual pushbutton is pressed.


PLC Input Module Connections

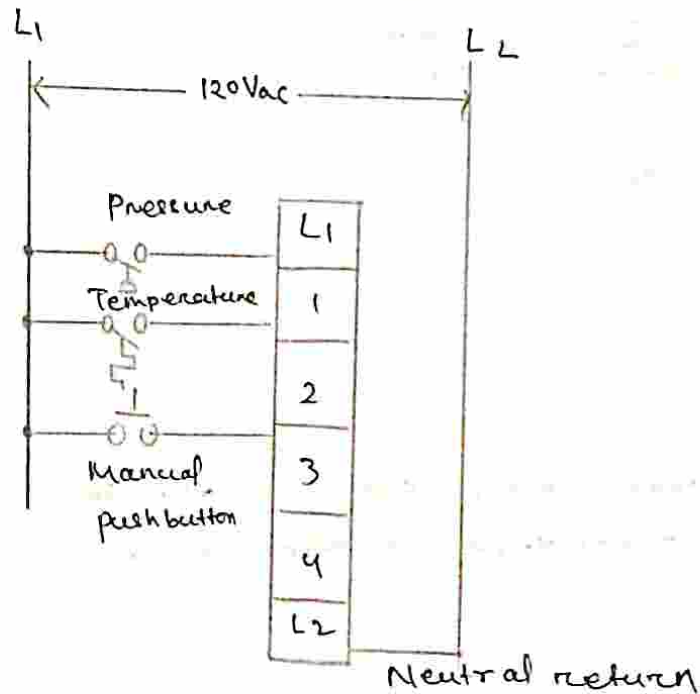- The same input field devices are used
- These devices are wired to the input module according to the manufacturer's labeling scheme.




PLC output Module Connections

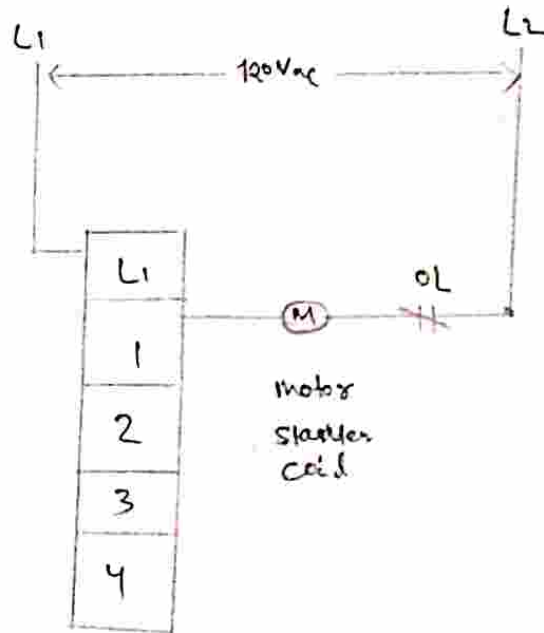
Same output field device is used and wired to the output module.



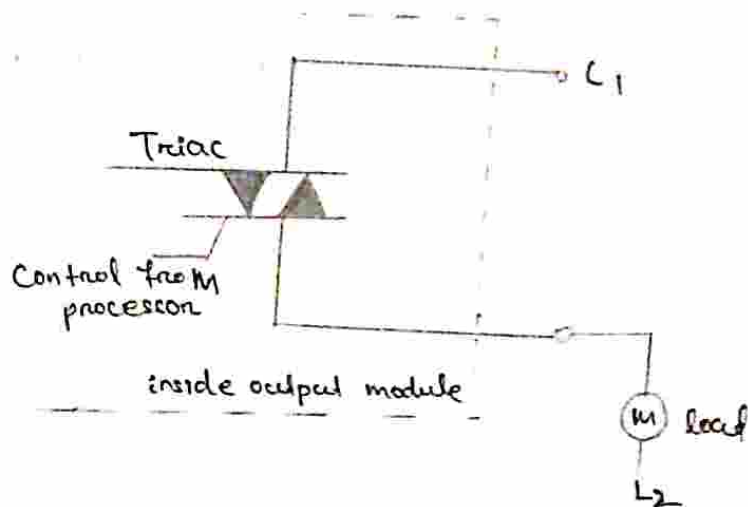
Triac switches motor ON and OFF in accordance with the control signal from the processor.



PLC Ladder Logic program

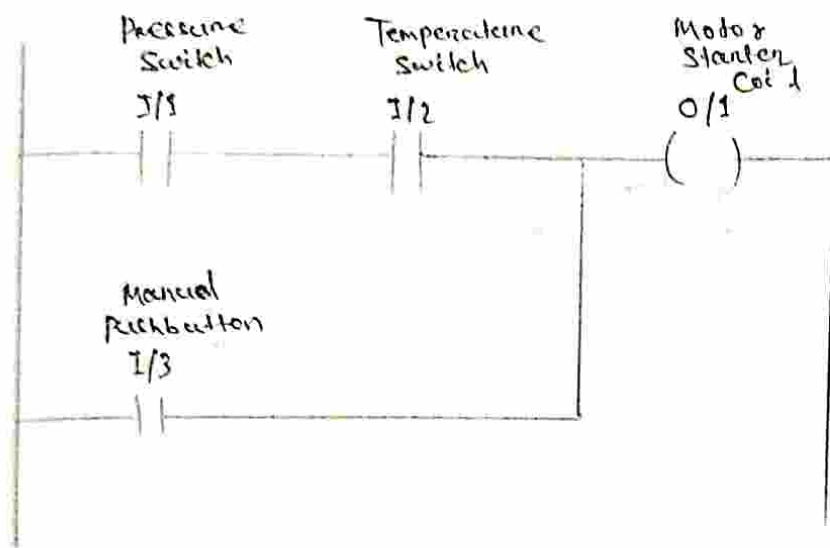

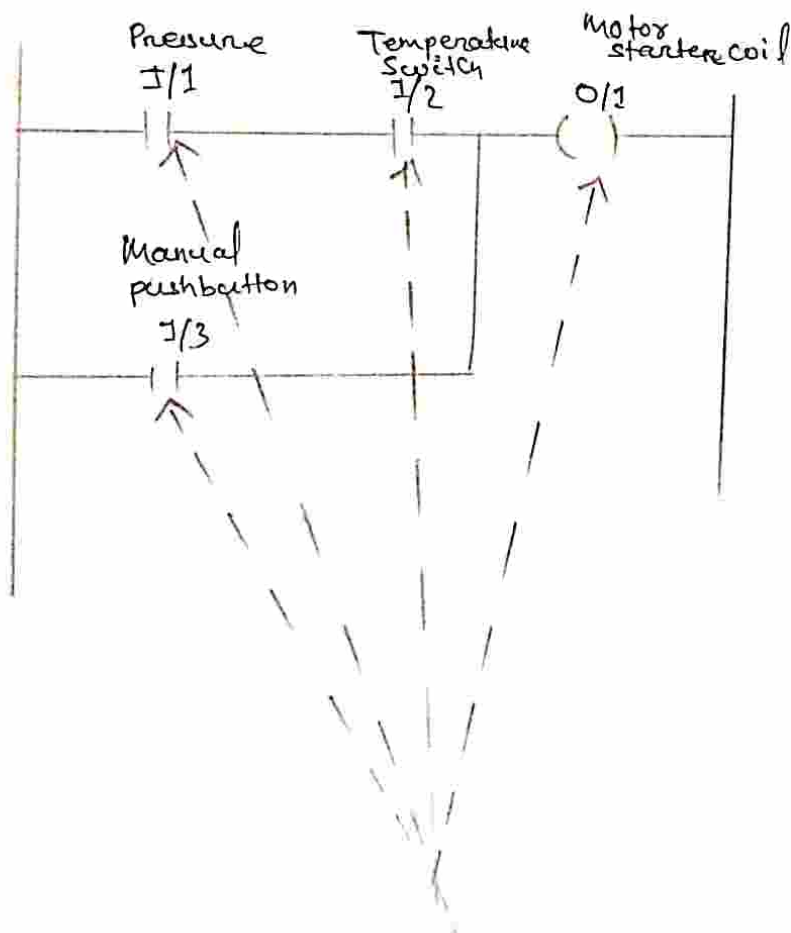
⇒ The format used is similar to that of the hard-wired relay circuit.




The symbols represent instructions

PLC Ladder Logic program

The numbers represent addresses

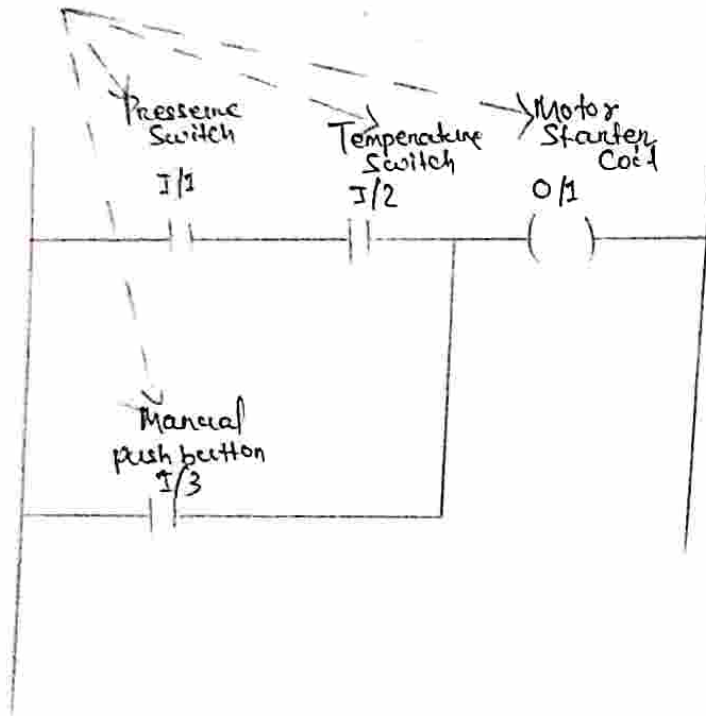


PLC Ladder Logic program

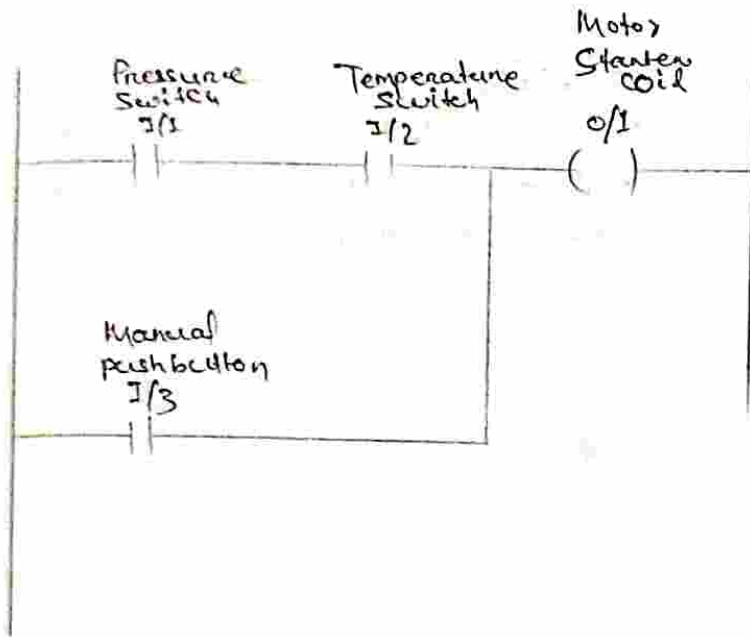

⇒ I/O address format will differ, depending on the PLC manufacturer. You give each input and output device an address. This lets the PLC know where they are physically connected.

Entering And Running The PLC Program

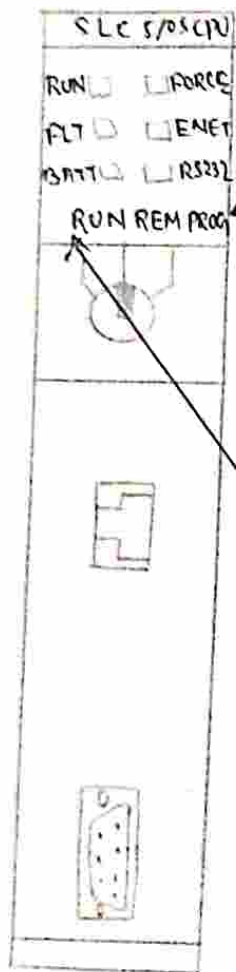


To enter the program into the PLC, the processor in the PROGRAM mode and enter the instructions one-by-one using the programming device.

To operate the program, the controller is placed in the RUN mode or operating cycle.


PLC Operating Cycle

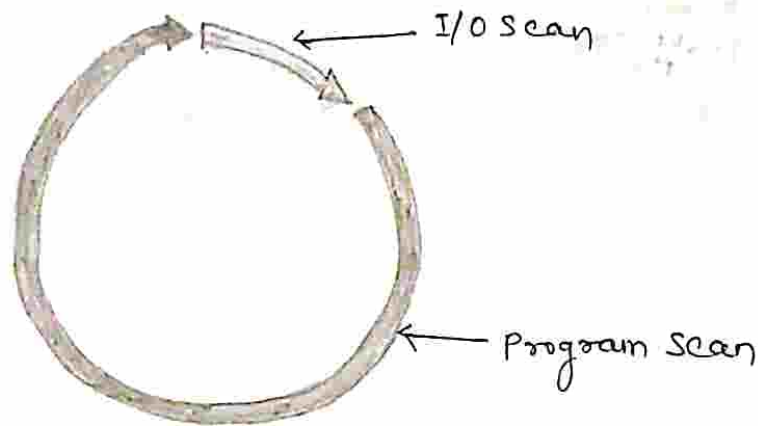During each operating cycle, the controller examines the status of input devices, executes the user program, and changes outputs accordingly.



The completion of one cycle of this sequence is called a scan. The scan time, the time required for one full cycle, provides a measure of the speed of response of the PLC.

PLC Operating Cycle

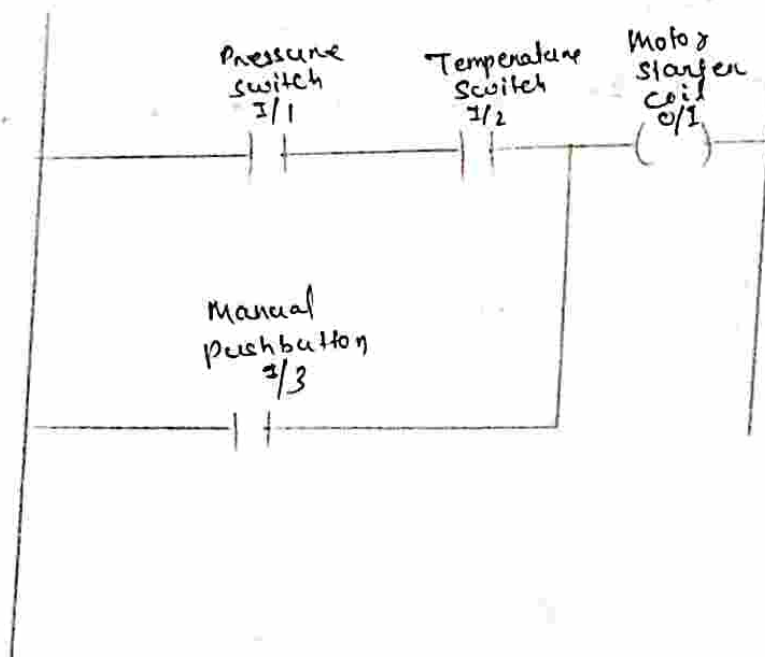


Each $-||-$

can be thought of as a set of normally open contacts

The $(-)$


can be considered to represent a coil that when energized, will close a set of contacts.

PLC operating cycle

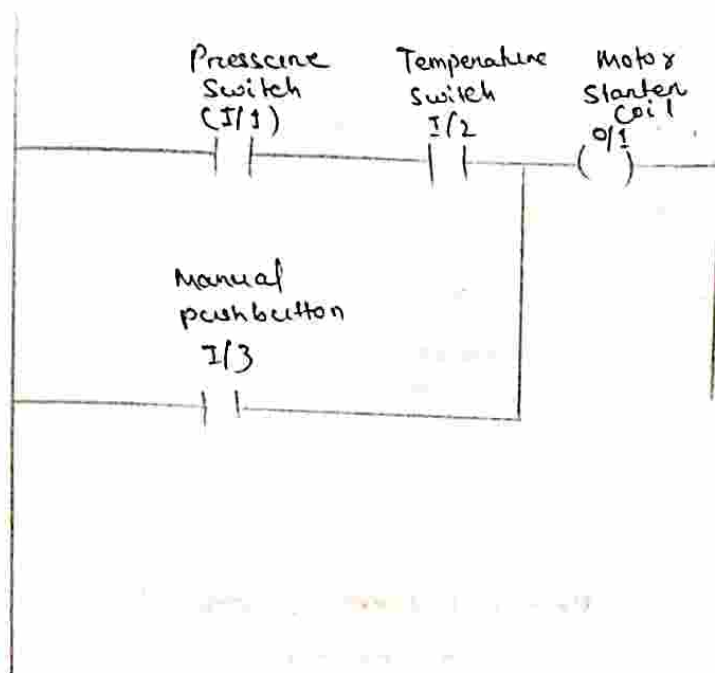

Coil O/1 is energized when contacts I/1 and I/2 are closed or when contact I/3 is closed. Either of these conditions provides a continuous path from left to right across the rung that includes the coil.

Modifying A PLC Program

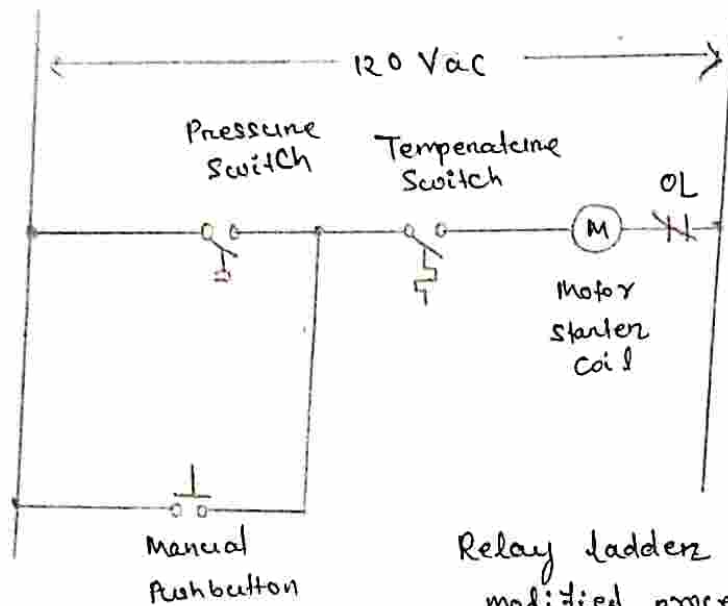


Relay ladder diagram for modified process.

The change requires that the manual pushbutton control should be permitted to operate at any pressure but not unless the specified temperature setting has been reached.

If a relay system were used, it would require some rewiring of the system, as shown, to achieve the desired change.

Modifying A PLC program

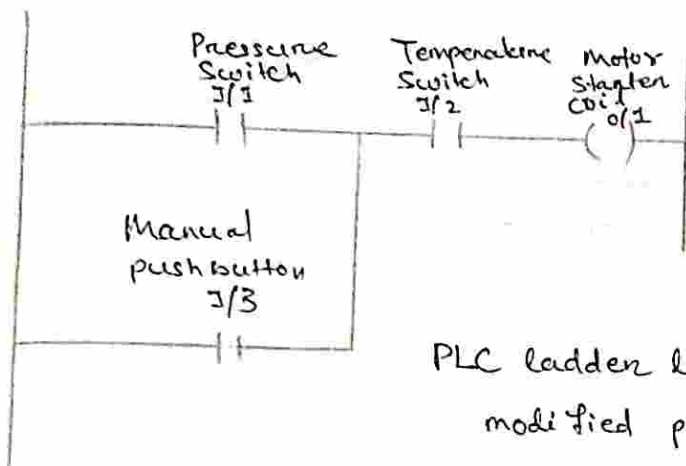


PLC ladder logic diagram for modified process

If a PLC is used, no rewiring is necessary!


The inputs and outputs are still the same.

All that is required is to change the PLC program.

PLCs versus personal Computers

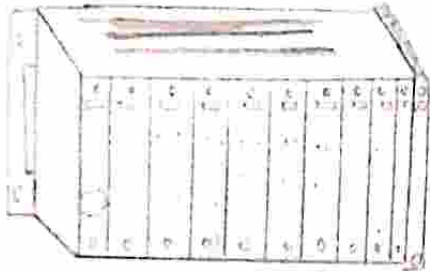

Same basic
architecture

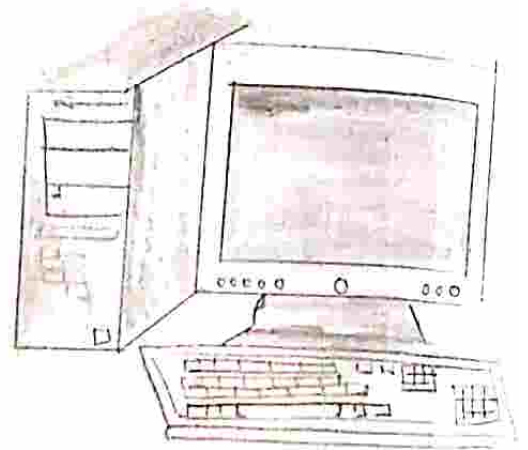

PLC

- ⇒ Operates in the industrial environment.
- ⇒ Is programmed in relay ladder logic.
- Has no keyboard, CD drive, monitor or disk drive.
- Has communications ports, and terminals for input and output devices.


PC

- ⇒ Capable of executing several programs simultaneously, in any order.
- ⇒ Some manufacturers have software and interface cards available so that a PC can do the work of a PLC.

PC Based Control Systems


Advantages

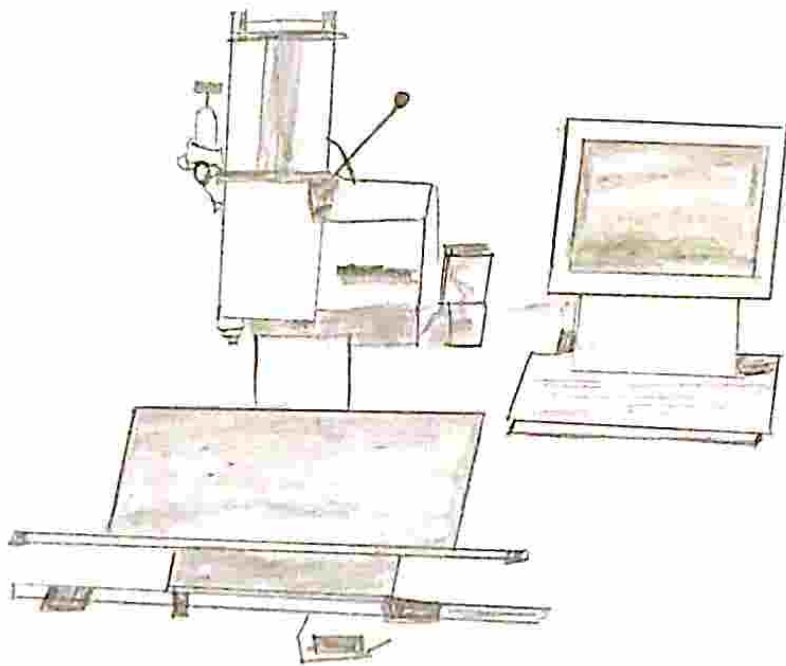- ⇒ Lower initial cost
- ⇒ Less proprietary hardware and software required
- ⇒ Straight forward data exchange with other systems
- ⇒ Speedy information processing
-) Easy customization



PLC Instruction Set

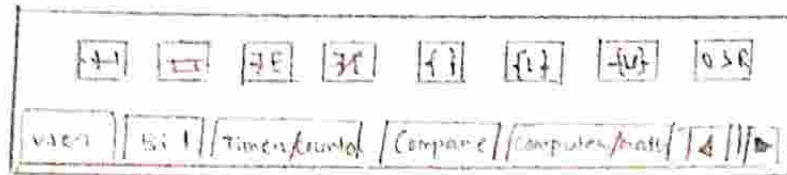The instruction set for a particular PLC type lists the different types of instructions supported.



An instruction is a command that will cause a PLC to perform a certain predetermined operation.

Typical PLC Instructions

XIC (Examine ON) Examine a bit for an ON condition

XIO (Examine OFF) Examine a bit for an OFF condition

OPE (Output Energize) Turn ON a bit (non retentive)

OTL (Output Latch) Latch a bit (retentive)

OTU (Output Unlatch) Unlatch a bit (retentive)

TOF (Timer off-Delay) Turn an output ON or OFF after its rung has been OFF a preset time interval.

TON (Timer on-Delay) Turn an output ON or OFF after its rung has been ON for a preset time interval.

CTD (Count Down) Use a software counter to count down from a specified value.

CTU (Count Up) Use a software counter to count up to a specified value.

Power Electronics

In power electronics there is two words:-

- (i) Power
- (ii) Electronics

Power:


Here power refers to electrical power which is get general transmitted and distributed, which in the form of high power high voltage and high current.

Electronics

Electronics deals smooth-performans of function by controlling different signals or electronics engineering deals generation, transmissions distribution of datas at low power, low voltage and low current.

So by combining two words power electronics, which defined as the application of electronics principle for the control and conversion of electric power in high power, high voltage and high current level.

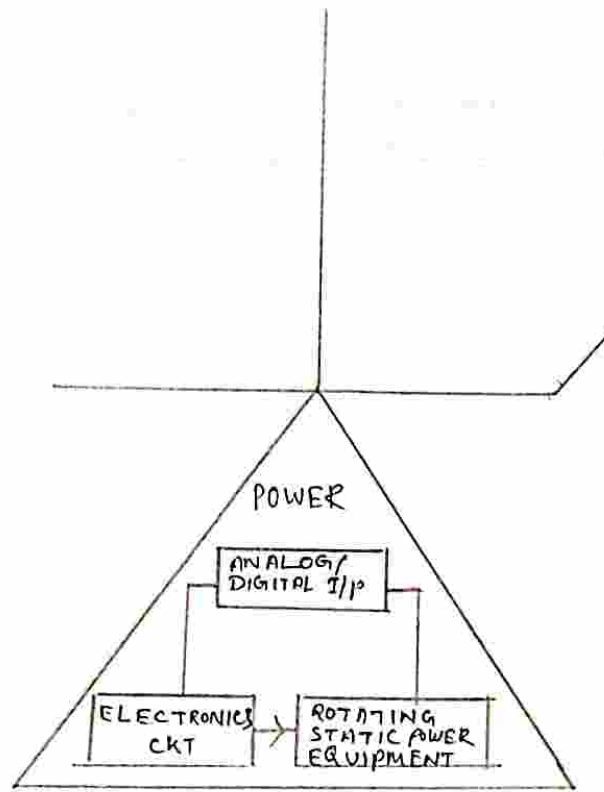Hence the function of power etc. Control the process during generation transmission and distribution of high power.






[BLOCK DIAGRAM OF POWER ELECTRONICS]

Application of Power Electronics:

Power electronics devices are used:-



① As a Control Rectifier: -

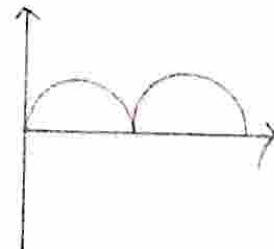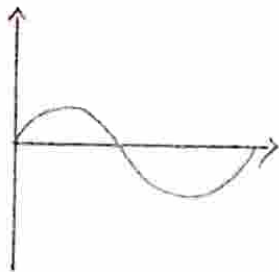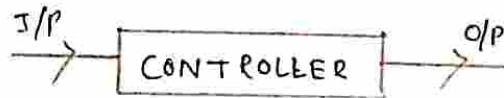It converts fixed high value of A.C voltage to variable value of d.c voltage.






② INVERTERS:

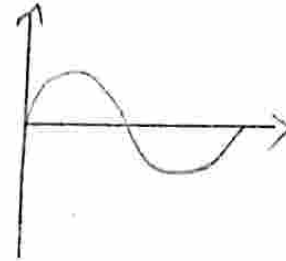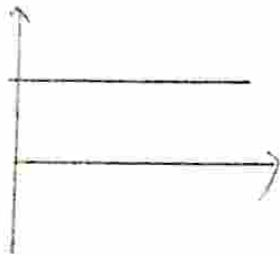It converts fixed high value of D.C voltage to variable AC voltage which have variable frequency.






③ CHOPPERS

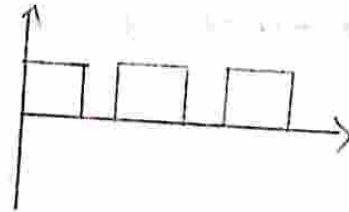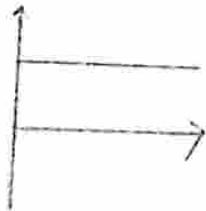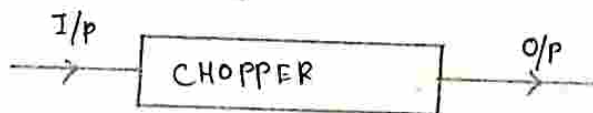It converts fixed d.c voltage to variable d.c voltage






④ A.C VOLTAGE CONTROLLER :- (A.C Regulator)

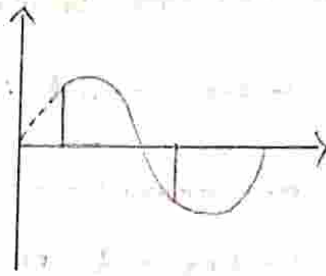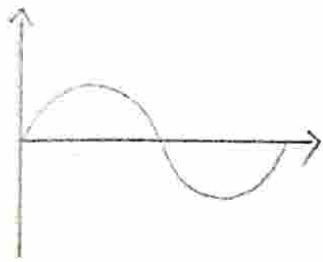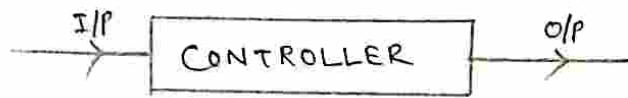It converts fixed value of A.C voltage to variable voltage of A.C voltage.



⑤ CYCLO CONVERTERS :-

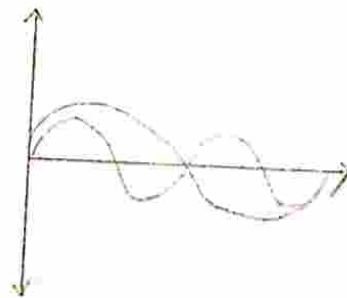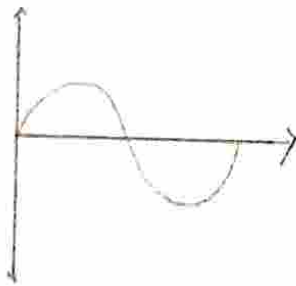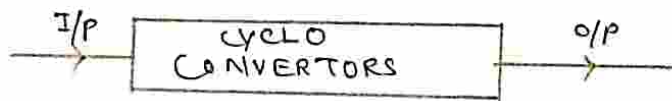It converts fixed frequency A.C to variable voltage, variable frequency of A.C o/p voltage.



Besides this power electronics devices the P. Elec. also used for :-

- (i) Battery charging system.
- (ii) Speed control of d.c motor
- (iii) HVDC transmission system
- (iv) Electric device control interaction.
- (v) Ups (Un-interruptable power system)
- (vi) Induction heating and ARC furnace
- (vii) Welding power supply

Power Electronics Devices :-

THYRISTOR :-

- ⇒ As diode is an electronics semi-conductor electronics switching devices.
- ⇒ Similarly Thyristor is the semiconductor power electronics switching family.
- ⇒ In thyristor family there are more than one power electronics devices or components.
- ⇒ The name "THYRISTOR" is derive from the words THYR + ISTOR.
- ⇒ "THYR" Comes from Thyatron tube & "ISTOR" comes from Transistor.
- ⇒ The Thyatron tube has function to control the rectifier which is used as high power electronic switch which is filled with gas.
- ⇒ And the function of Transistor is to amplify the weak signal.
- ⇒ By combining both the words. Thyristor which is a solid device like transistor and it's characteristic is same as Thyatron Tube.

⇒ In Thyristor family there are more family members like:-



- 1- SCR (Silicon Control Rectifier)
- 2- DIAC (Bi-directional Diode Thyristor)
- 3- TRIAC (Bi-directional Triode Thyristor)
- 4- GTO (Gate Turn off SCR)

SCR

⇒ It stands for Silicon Control Rectifier.

→ SCR is most widely used power semiconductor device about 99%.

Construction of SCR

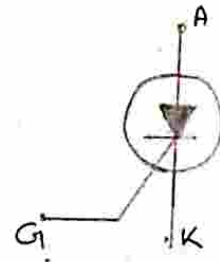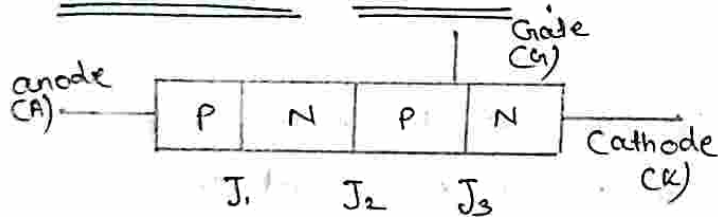

⇒ SCR has 4 layers & 3 junction devices.

The material which is used for formation p-type & n-type layer is silicon.

So by alternating combining (cascoding) p-type & n-type material SCR is formed which have 3 terminals i.e

Anode (A), Cathode (K) & Gate (G)

Anode

Anode is a out side terminal of p-region.

Cathode


Cathode is a out side terminal of N-region.

Gate

A terminal welded to p-type layer nearest to cathode + CK is known as Gate terminal.

V-I CHARACTERISTICS OF SCR :-

CKT Diagram

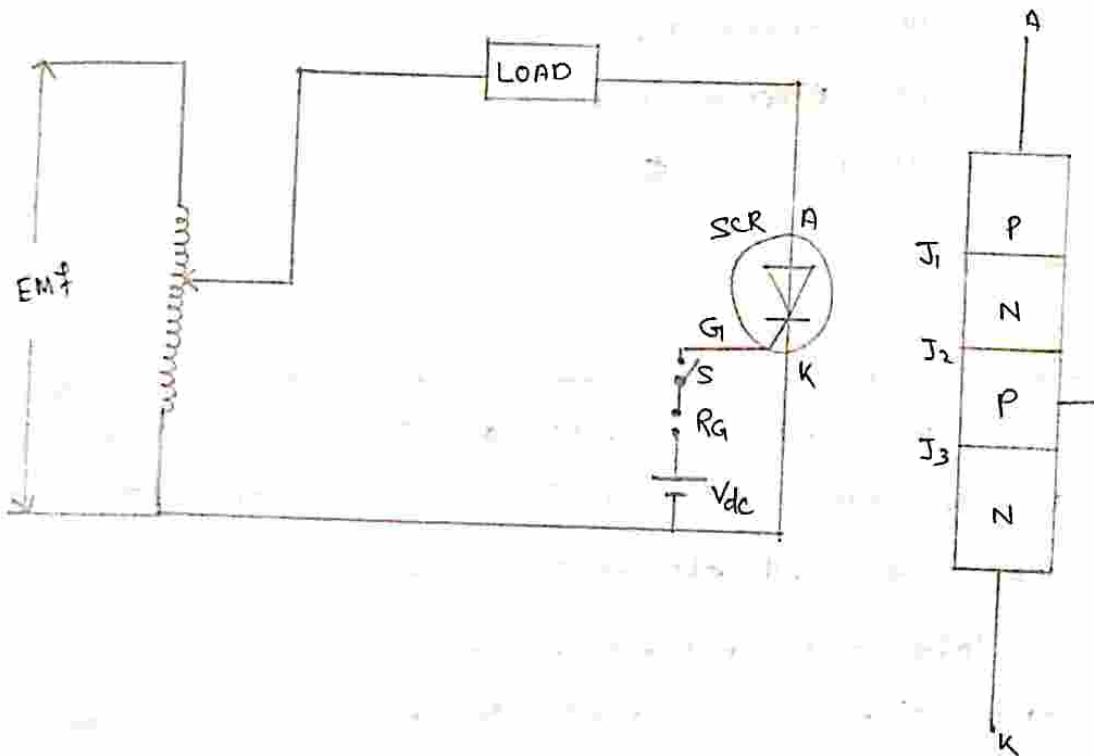

⇒ As SCR is a 4 layer 3 junction device and there is 3 terminals i.e. ANODE, CATHODE & GATE.

⇒ Among 3 junction generally J_1 & J_3 are forward biased where as J_2 is reverse biased.

⇒ In the above ckt a SCR is connected to fed power from source to load.

⇒ When SCR conductor (ON state) then power transfer source to load.

⇒ According to the supply feed to load there are 3 mode of operation i.e. (A) Forward Blocking mode
(B) Reverse Blocking mode
(C) Forward Conduction mode

FORWARD BLOCKING MODE :-

When Anode is +ve w.r.t cathode & Gate ckt is open then the SCR is said to be F/W biased. At that time recombination takes place at J_1 & J_3 layer and F/W biased where as at J_2 junction the amount of holes and electrons get reduced hence no recombination take place and get reverse biased.

As no current flow from anode to cathode (J_2 is reverse biased) so the mode of operation is known as F/W Blocking mode.

If $V_{R/W}$ voltage increases (Anode to cathode voltage) then the reverse junction is will have Avalanche break down (force recombination of e.s & holes)

→ When the R/W voltage applied a "Avalanche break down" take place at J_2 junction then the voltage is known as R/W Break over voltage (V_{BO}).

⇒ In R/W Blocking mode the SCR is treated as open switch (OFF state).

$E > V_{BO}$ (ON)
$E < V_{BO}$ (OFF)

Reverse Blocking Mode :

- (i) When cathode is +ve w.r.t Anode and Gate ckt is open the SCR is reverse biased.
- (ii) At that time J_1 & J_3 are reverse biased where as J_2 junction is R/W biased.
- (iii) So there is no current flow from Anode to cathode.
- (iv) The reverse blocking mode is known as off state and the characteristic is same the diode.
- (v) If reverse voltage increases (Cathode to Anode) then avalanche break down take place at a critical voltage known as Reverse Breakdown voltage (V_{BR})

F/W CONDUCTION MODE :-

In the F/W blocking mode the Anode is +ve where as the Cathode is -ve and as J_1 & J_3 are F/W biased but J_2 is reverse biased so it is in blocking mode.

To bring the SCR from blocking mode to conduction mode by exceeding F/W Anode to cathode voltage (break over voltage) or by applying a gate pulse between gate and cathode.

Now the SCR is ON state and behaves like a switch & the voltage drop having 1-2 volt across to it, which is negligible.

Once SCR conduct by F/W current J_2 Junction no longer reversed biased exist.

As no Gate current is required for device to remain in ON state.

LATCHING CURRENT (I_L) :-

The minimum value of Anode current required to turn ON the SCR even after the Gate pulse is remove and the SCR is remain in ON state.

HOLDING CURRENT (I_H) :-

It is the minimum value of Anode current below which Thyristor is turn OFF. Generally Latching current is greater than holding current ($I_L > I_H$).

Which is two to three times of I_H .

*) Latching current is useful for keeping the SCR in ON state where as Holding current is use for keeping the SCR.

Difference betⁿ:

DIODE

- (i) Diode is 2 layer one junction device.
- (ii) It is bring only reverse blocking mode.
- (iii) It is a uncontrol switch.
- (iv) Voltage drop across diode is 0.3 - 0.7 volt.
- (v) Fig:

SCR

- (i) SCR is 4 layer 3 junction device.
- (ii) It is bring both F/W + reverse blocking mode.
- (iii) It is a control switch.
- (iv) Voltage drop across SCR is 1-2 volt.
- (v) Fig:

Difference betⁿ:


TRANSISTOR

- (i) It has 3 layer 2 junction
- (ii) In transistor emitter - base is F/W biased and base collector is reverse biased.
- (iii) It is not a latching ckt.
- (iv) Switching frequency is high as compare to SCR.
- (v) Fig:-

SCR

- (i) It has 4 layer 3 junction.
- (ii) In SCR J_1 and J_3 are F/W biased and J_2 is reverse biased.
- (iii) It is a Latching ckt.
- (iv) Switching frequency is low as compare to Transistor.
- (v) Fig:

V-I CHARACTERISTIC OF SCR

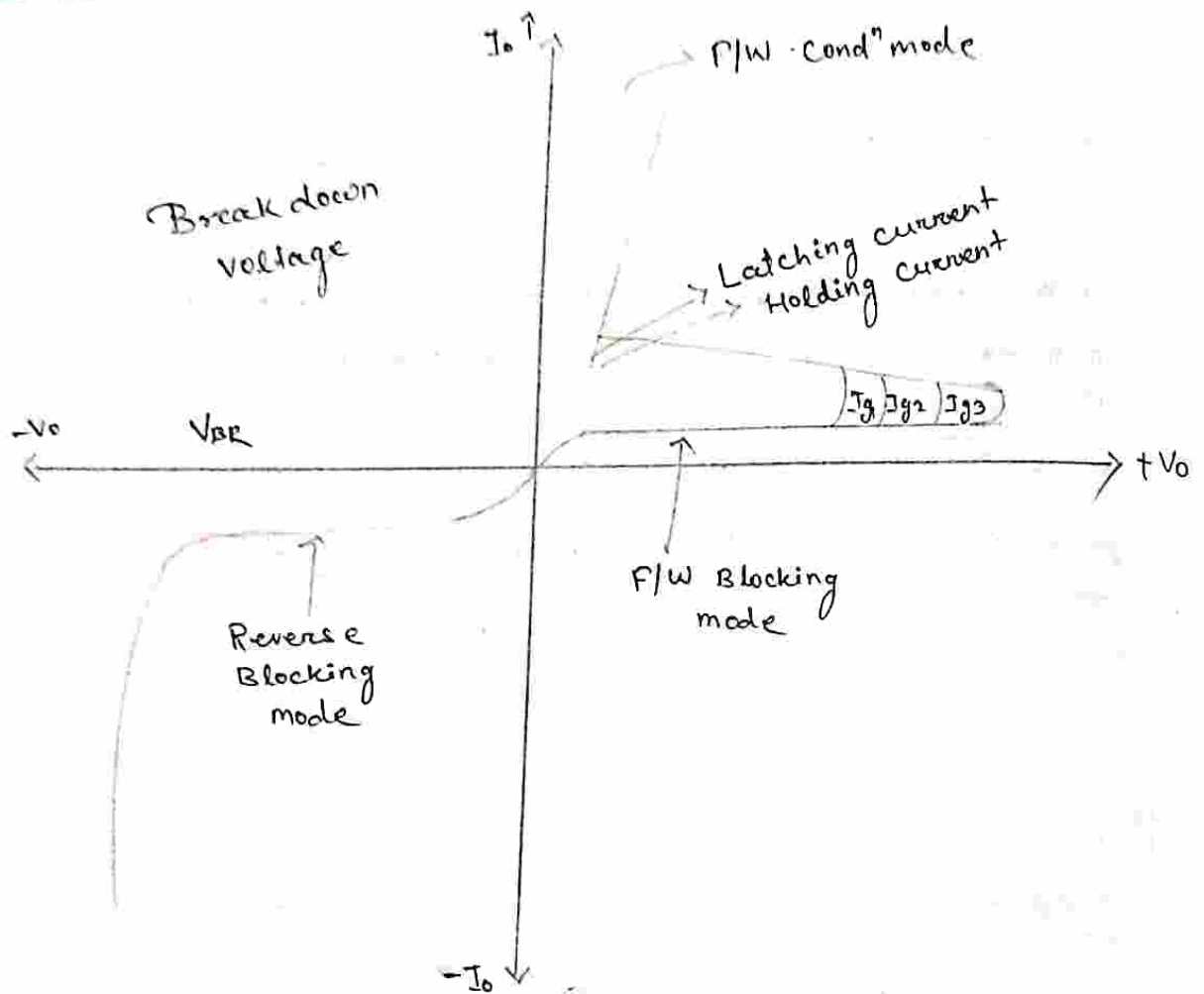

⇒ For bringing the SCR from forward blocking mode to conduction mode if greater the F/W voltage (+ve lesser will be required for pulse current and vice-versa (if lesser the F/W voltage greater gate current required to turn on)

$$I_{g1} < I_{g2} < I_{g3}$$

Turn - ON method of SCR :

There are five methods for turning ON the SCR:

(i) Increasing the F/W voltage


(ii) Gate turn ON method

(iii) $\frac{dV}{dt}$ turn ON method

(iv) Light turn ON method

(v) Thermal turn ON method

(i) Increasing the F/W voltage :

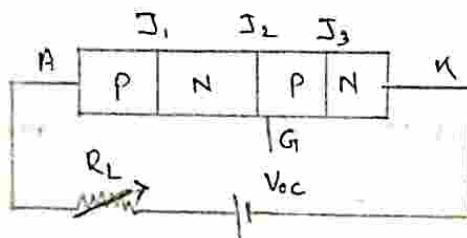


⇒ When SCR is F/W biased J_1 + J_3 acts as a close switch where as J_2 acts as open switch since it is reverse biased.

⇒ When the forward voltage increase beyond the break over voltage.

$V_0 > V_{BO}$ Then J_2 breakdown & through current start flowing between anode to cathode.

⇒ This method is not generally used because required voltage is large.

GATE TURN ON METHOD :-

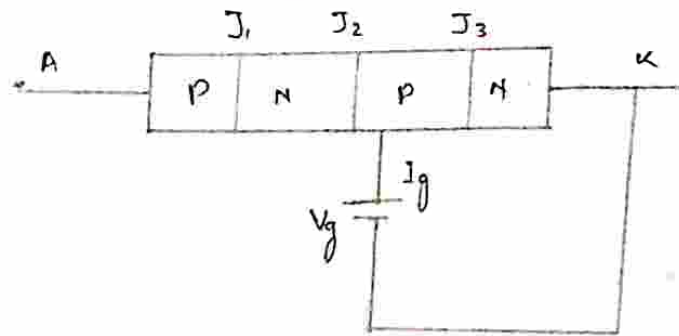

During f/w blocking mode J_1 & J_3 are f/w biased and J_2 is reverse biased.


To bring the J_2 to f/w biased we applied a +ve gate pulse between Gate and cathode.

If Gate current is high then low f/w voltage is required to turn ON the SCR.

When Gate pulse is applied to p-layer it generate large amount of holes which brings the ' J_2 ' junction to f/w bias.


⇒ (iii)

$\frac{dV}{dt}$ TURN ON METHOD :-

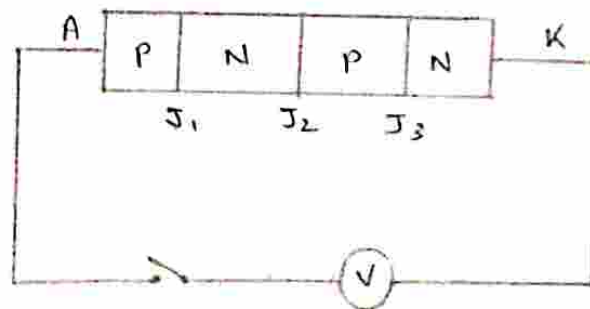

- (i) When anode is made +ve w.r.t cathode junction J_1 and J_3 are F/W biased and J_2 junction is reverse biased.
- (ii) The depletion layer around the junction J_2 acts as di-electric but J_1 and J_3 are acts as good conductor so SCR entirely act as a capacitor.
- (iii) When switch is suddenly closed the $\frac{dv}{dt}$ is very very high.
- (iv) As a result large charging current ($i_c = C_{j_2} \frac{dv}{dt}$) flow through SCR can breaks the J_2 junction and SCR conducts from anode to cathode.
- (v) This method is not generally used as high charging current may damage the SCR.

(iv) Light Turn ON Method :-

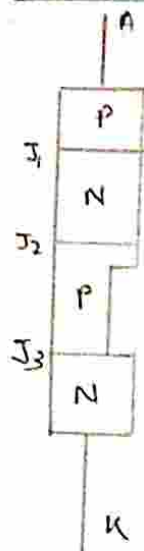

(i) Here the energy required for breaking co-valent bond is given by light source.

(ii) This can be achieved by a special wavelength of light (λ)

(iii) When light falls it breaks co-valent bond & emits electron which generates electron-holes pair and trigger the SCR by breaking J_2 junction.


(iv) This type of SCR are known as LA-SCR (Light Activated):

✓ Thermal Turn ON method :-

(i) In this method the energy required for breaking the co-valent bond is obtained by heat energy.


(ii) The area around J_2 is heated by external thermal source and J_2 junction break and current start flowing from anode to cathode.

Two-TRANSISTOR ANALOGY OF SCR :-

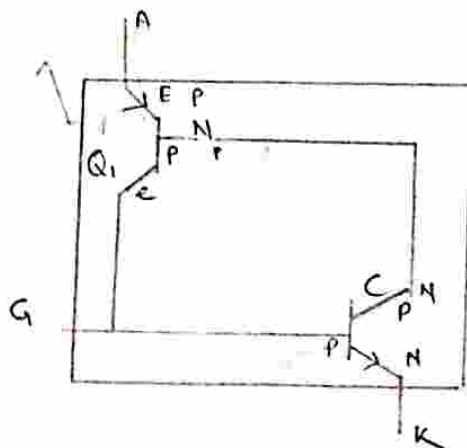

- (i) The latching ckt of SCR can be understood by 2 transistor analogy of SCR.
- (ii) Here the SCR is broken into 2 transistor (PNP + NPN)
- (iii) When gate is +ve w.r.t cathode the NPN transistor (Q₂) starts conducts.
- (iv) As a result this provide a base current to PNP transistor and turn on.
- (v) The o/p of PNP is the i/p of NPN since collector of Q₁ is connected to base of Q₂.
- (vi) Even after gate voltage is remove the transistor continue to conduct since they are connected back to back.
- (vii) Both the transistor able to con conductor the SCR acts as close switch conduct anode to cathode upto it is not turn off forcefully or naturally.

Derivation of two transistor Analogy!

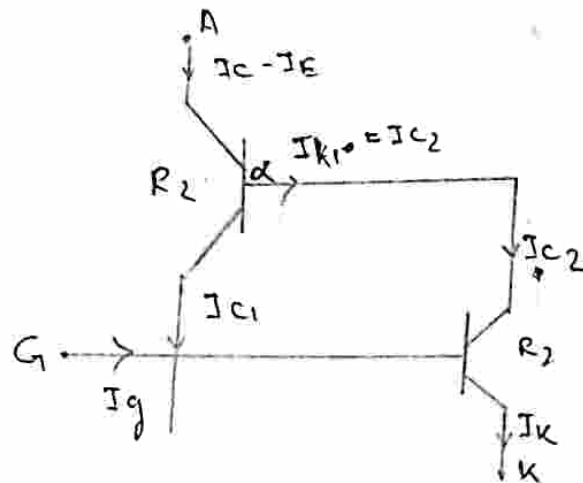

$$I_c = \alpha I_E + I_{CBO}$$

$$I_k = I_a + I_g$$

α = Common base current gain

I_{CBO} = Common base leakage current of collector base junction.

For R_1

$$I_{c1} = \alpha_1 I_{E1} + I_{CBO1} = \alpha_1 I_a + I_{CBO1} \dots \dots \dots \textcircled{1}$$

For R_2

$$I_{c2} = \alpha_2 I_{E2} + I_{CBO2} = \alpha_2 I_k + I_{CBO2} \dots \dots \dots \textcircled{2}$$

Putting I_k value in eqⁿ $\textcircled{2}$

$$I_{c2} = \alpha_2 I_k + I_{CBO2}$$

$$\Rightarrow \alpha_2 (I_a + I_k) + I_{CBO2} \dots \dots \dots \textcircled{3}$$

The sum of two collector current given by eqⁿ ① and eqⁿ ③ is equal to external circuit current I_a entering

$$I_a = I_{c1} + I_{c2}$$

$$= \alpha_1 I_a + I_c B_{01} + \alpha_2 (I_a + I_g) + I_c B_{02}$$

$$= \alpha_1 I_a + I_c B_{01} + \alpha_2 I_a + \alpha_2 I_g + I_c B_{02}$$

$$= \alpha_1 I_a + \alpha_2 I_a + I_c B_{01} + \alpha_2 I_g + I_c B_{02}$$

$$= I_a (\alpha_1 + \alpha_2) + \alpha_2 I_g + I_c B_{01} + I_c B_{02}$$


$$= I_a - I_a (\alpha_1 + \alpha_2) = \alpha_2 I_g + I_c B_{01} + I_c B_{02}$$

$$\Rightarrow I_a \{ 1 - (\alpha_1 + \alpha_2) \}$$

$$= \alpha_2 I_g + I_c B_{01} + I_c B_{02}$$

$$\Rightarrow \boxed{I_a = \frac{\alpha_2 I_g + I_c B_{01} + I_c B_{02}}{1 - (\alpha_1 + \alpha_2)}}$$

Gate characteristics of SCR :-

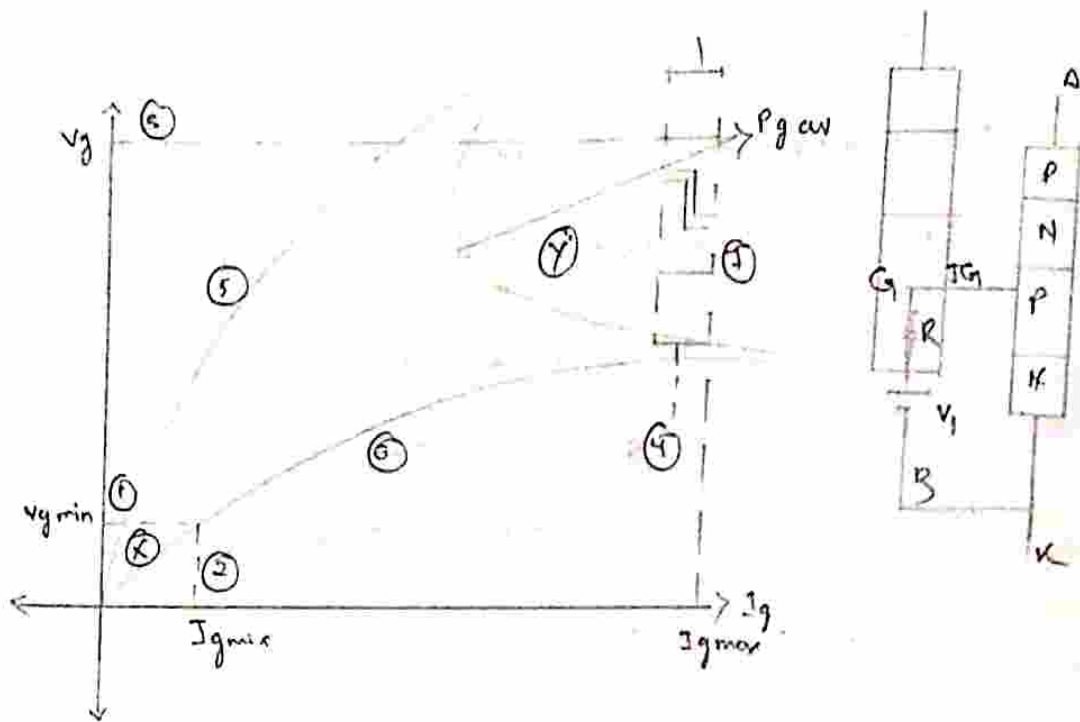

Gate is nothing but a PN junction.

Here we found the characteristic Gate voltage & Gate Current ($V_g \sim I_g$) seen across a f/w biased SCR.

According to doping level there are 02 no. of graph is obtained between $V_g \sim I_g$

The curve - (5) represent $V_g \sim I_g$ graph when doping level is low curve - (6) represent that of when doping level is high.

The CKT for triggering SCR through gate is design according to the doping level.

- (v) Curve - (1) is represent the low curve voltage value must be applied across gate to turn on the SCR.
- (vi) Curve - (3) represent highest possible voltage that can be applied to Gate ckt safely.
- (viii) Curve - (2) & Curve (4) is represent min^m & max^m value of gate curve required to turn ON the SCR.
- (ix) The max^m limit should be not excided in order to avoid Permanent damage of junction.
- (x) Curve - (7) indicates average power that can be discipitade by the devices.
- (xi) The area enclosed by Curve (5), (6), (4) represent safe operating area (SOA) for the SCR.
- (xii) So when we designed gate ckt for triggering SCR, the operating point should be lies is sag.
- (xiii) If the operating point lies in the cross (X) area then can't turn on the SCR.

(xiv) If operating point lies in the (v) region it is not safe for device operating.

P_{gav} = Average Gate power dissipation

V_{gmax} = Max^m permissible Gate voltage

I_{gmax} = Max^m permissible Gate current

V_{gmin} = Min^m Gate voltage required trigger on SCR.


I_{gmin} = Min^m Gate current required trigger on SCR.

TURN OFF METHOD OF SCR :-

⇒ To turn off the SCR we brought it from F/W conduction mode to F/W blocking mode or Reverse blocking mode for turn off.

⇒ It is also known as commutation of SCR.

⇒ Different types of turn off process :-

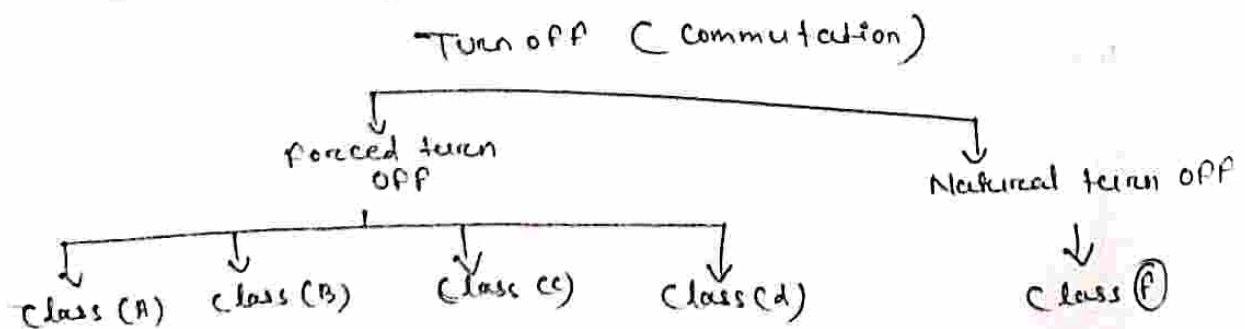


Natural Turn off :

- When SCR is connected to an AC source, the current goes through its natural zero at the end of every half cycle & reverse voltage acts automatically across SCR. Therefore SCR turn off.
- This is known as Natural turn off
- As no special ckt is required for turn off the SCR.
- The line commutated rectifier inverter used natural commutation or turn off for turn off the SCR.
- It is also known as class-A type commutation Turn off or line commutation.

Forced Turn off :

- In case of dc ckt there is no natural current zero & we have to turn off the SCR by designing special commutated ckt.
- In this process forcefully the current has to reduced to zero & the SCR is forcefully commutated.
- The components like Resistance, Inductance & Capacitance are used to achieved forced commutation so these are known as commutating components.
- There are five types of forced commutation process.

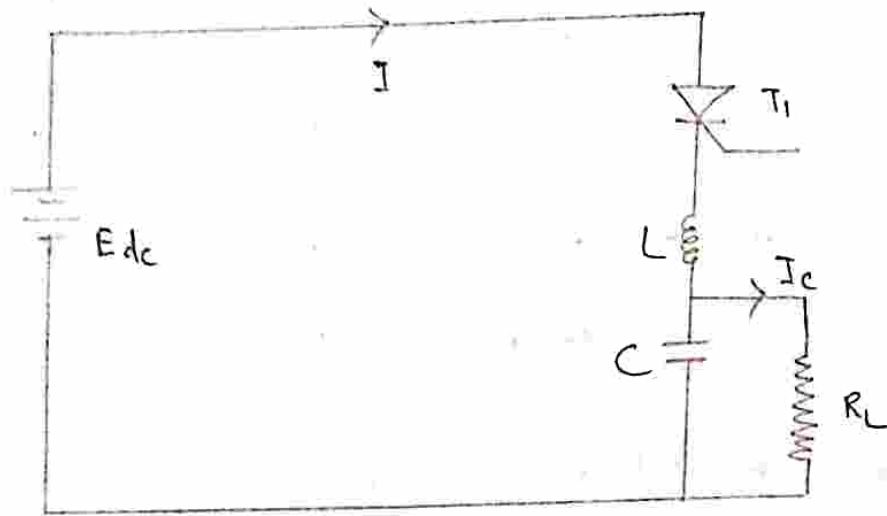Class - A { Resonant commutation / Load - Commutation }



Ckt description :-

- ⇒ The ckt diagram for class A type commutation is shown in the fig.
- In this case thyristor T_1 is connected series with $L+C$ and the load resistance R_L connected either series or parallel with capacitor.
- ⇒ During initial condⁿ the upper plate is -ve & lower plate is +ve.
- The SCR is trigger at $t=0$ by applying Gate pulse.
- At initially $I=0$ and the capacitor in fully discharge condⁿ.


→ After turning ON the SCR, I starts flowing through $T_1 + L_1$ and oscillation with I which help for charging of the capacitor & I_c start flowing -ve to +ve plate & charge of capacitor.

→ At that time I_L circulate through R_L .


→ After charging the capacitor a voltage $2E_{dc}$ build up across it & the upper plate +ve & lower plate -ve.

Now the capacitor starts discharging through R_L .

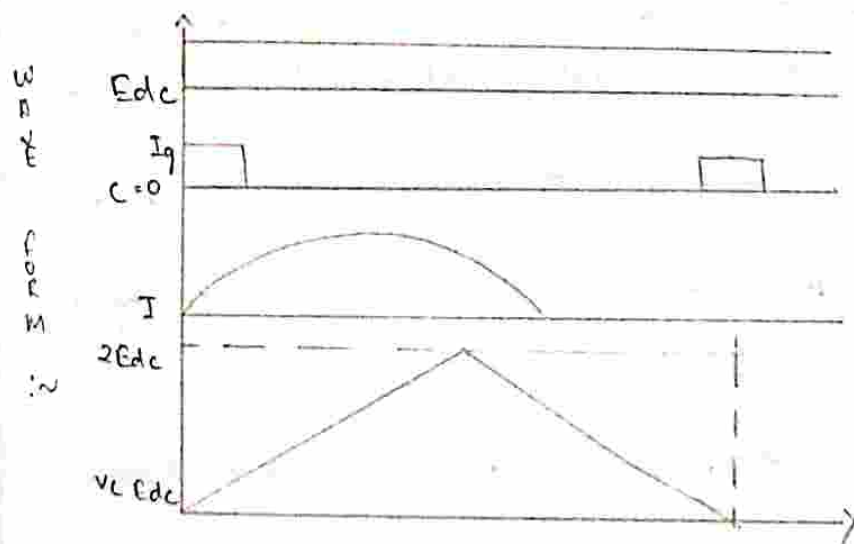When the current I less than I_c then the SCR automatically turn OFF As I_c forced turn OFF the SCR.



Class - B (Self Commutation)

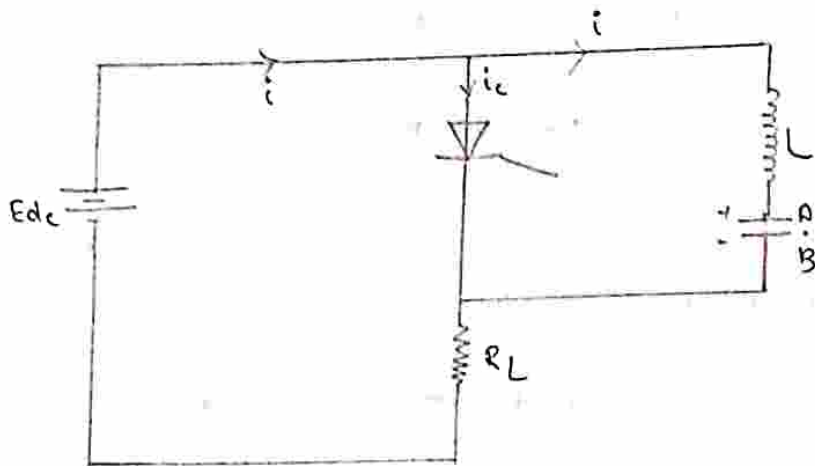

Ckt description :-

- (i) In class-B Commutation L & C are connected parallel with Thyristor & it constitute a R, L, C resonating ckt with load resistance R_L .
- (ii) The thyristor T_1 is series with R_L across switch E_{dc} is applied.
- (iii) When d.c supply is given it constitute R, L, C ckt as γ is in OFF condⁿ.
- (iv) The capacitor get fully charged with plate +ve & plate -B -ve
- (v) SCR is trigger by given Gate pulse.
- (vi) There are 02 current passes i.e. the load current ' i ' flow through $+E_{dc} \rightarrow T_1 \rightarrow R_L \rightarrow -E_{dc}$ and another is i.e. resonating current (discharging current) flow through $A \rightarrow C \rightarrow T_1 \rightarrow B$

(vii) After discharging the voltage across capacitor gets reversed (A \rightarrow -ve & B \rightarrow +ve) as a result the load current comes towards capacitor as a reverse voltage acts across capacitor.


(viii) Now current through T_1 i.e

$$i_L = I - I_C$$

(ix) when difference is reduced is zero the SCR is turn off.

(x) There is some extend the operation of class-A & class-B are same but the only difference is the load current carry by commutating component where as in class-B i.e not shock.

class - C (Complementary Commutator)

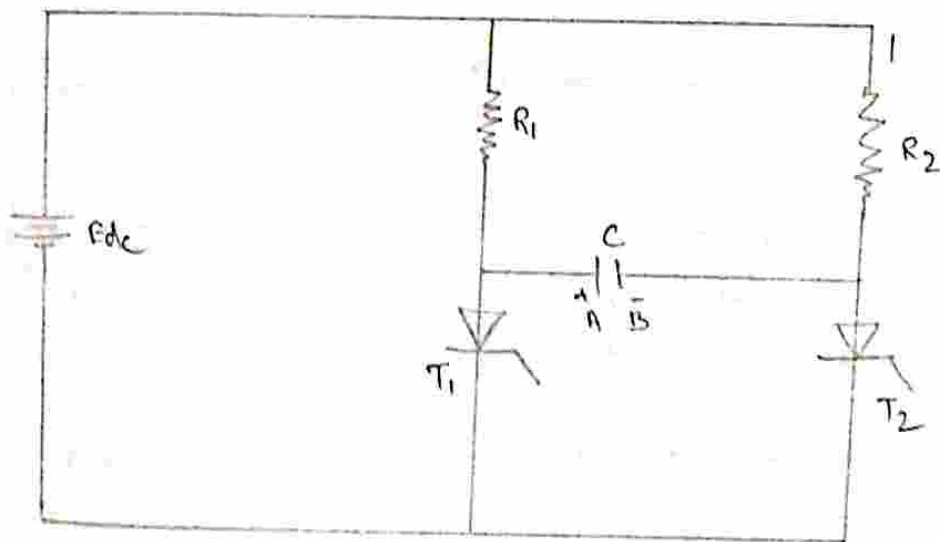


Ckt description

- (i) This is also known as complementary commutation.
- (ii) Here 2 thyristors T_1 & T_2 are connected series with R_1 & R_2 & a capacitor is connected in between the 2 branches.
- (iii) ~~Now~~ Initial capacitor point A is +ve & point B is -ve
- (iv) Now T_1 will turn on by giving gate pulse.
- (v) So there are 2 current starts flowing from source i.e. load current & charging current.
- (vi) Load current flow $+E_{dc} \rightarrow R_1 \rightarrow T_1 \rightarrow E_{dc}$ & charging current flow $+E_{dc} \rightarrow R_2 \rightarrow B \rightarrow A \rightarrow T_1 \rightarrow -E_{dc}$
- (vii) After charging the capacitor plate B +ve & plate -A-ve which reduces the charging current to zero & load current also flow through the ckt.
- (viii) At that time it is time to turn off the SCR T_1 by turning on the T_2
- (ix) As capacitor polarity is reversed (A \rightarrow -ve, B \rightarrow +ve) so it forms large current towards T_2 & current across T_1 is reduces to zero and it is turn off.
- (x) Now the current direction also reverse i.e. the charging current flows through the R_1 and charge the capacitor and the load current flow $+E_{dc} \rightarrow R_2 \rightarrow T_2 \rightarrow -E_{dc}$
charging current flow $+E_{dc} \rightarrow R_1 \rightarrow A \rightarrow B \rightarrow T_2 \rightarrow -E_{dc}$

vi) The T_2 will be turn off when is will be reduces to zero by turning on the T_1 & above cycle repeated.

Class-D (Auxiliary commutation)

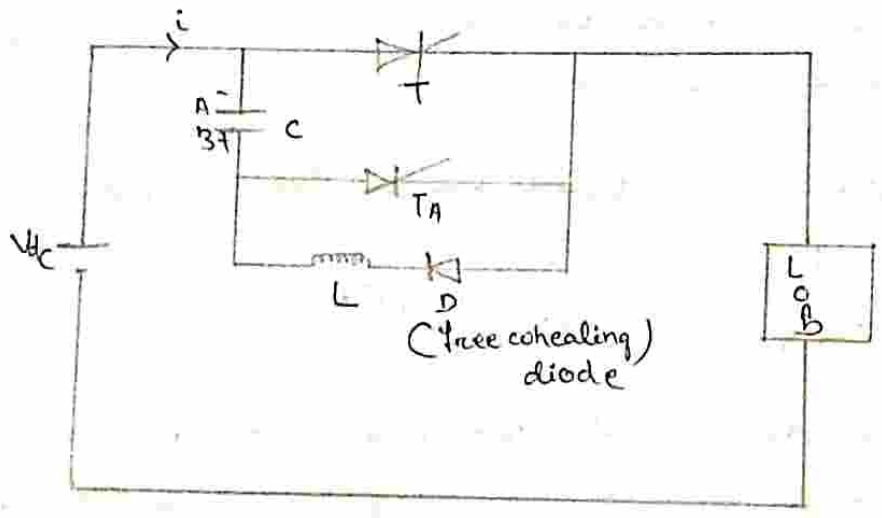

Ckt description

- i) The basic ckt shows an auxiliary thyristor & a main thyristor for ckt operation.
- ii) The auxiliary thyristor (T_A) is use forcefully commutation of main thyristor (T). So it is known as Auxiliary turn OFF / Auxiliary commutation.

iii) The SCR T_A turn on initially to free charge the capacitor plate A (+ve) & plate B (-ve).

iv) At $t=0$ thyristor 'T' turn on by giving gate pulse of the 'i' flowing
 $V_{dc}^+ \rightarrow T \rightarrow \text{load} \rightarrow V_{dc}^-$

At the mean time the capacitor start discharging through SCR (T). by circulating I_c current which is flow through i.e I_c flow
 $A^+ \rightarrow T \rightarrow D \rightarrow L \rightarrow B^-$

(vi) After freewheeling I_c current flow from capacitor i.e. the polarity get reverse i.e. A(-ve) & B(+ve)


(vii) At the mean time ($t=t_1$) T_A turn on by giving gate pulse so no. current available at SCR 'T' & it turn off forcefully known as voltage commutation.

(viii) So both charging current & load current flow through T_A the current flow path.

$$V_{ac}^+ \rightarrow A^- \rightarrow B^+ \rightarrow T_A \rightarrow \text{Load} \rightarrow V_{dc}^-$$

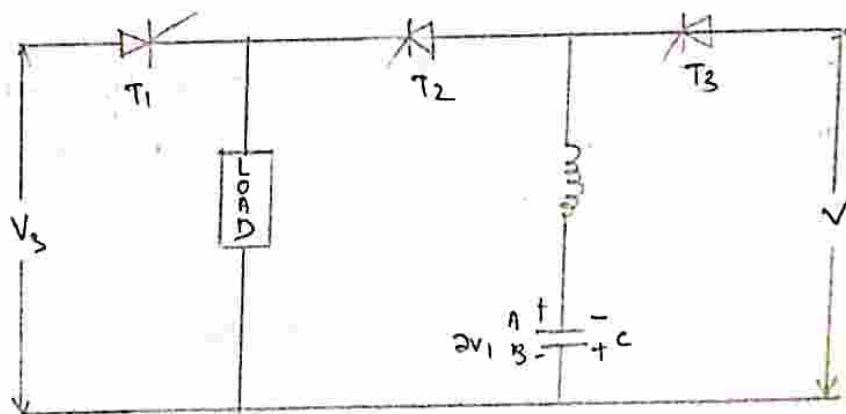(ix) After charging the capacitor the polarity get reverse A(+ve) & B(-ve) and 'T' is turn on by giving Gate pulse and above cycle repeated.

Class - E (External pulse commutation Resonant pulse Commutation)



Ckt description

- (i) Here 2 no of thyristors T_2 + T_3 are used for the turn off SCR T_1 . External voltage V_1 also used for turn off the thyristor T_1 so it is known as external pulse commutator.
- (ii) At time $t=0$ SCR T_1 + T_3 simultaneous on by giving gate pulse so a load current starts flowing through T_1 to load.
- (iii) Similarly in the mean time current I_c start flowing from V_1 to through T_3 + charge up the capacitor.
- (iv) After charging the capacitor A-plate +ve + B plate -ve + a voltage $2V_1$ develop across it.
- (v) At the is n type time T_1 turn on by giving gate pulse in T_3 automatically turn off due to voltage commutation.
- (vi) As $V_3 < 2V_1$ a large starts flowing through T_2 towards load.
- (vii) Due to this a reverse voltage acts across T_1 + it automatically turn off.

THYRISTOR PROTECTION :

→ As thyristor is 1st acting switching device which is used for converting controlling & switching purpose. Subjected to protect in different fault condⁿ.

→ there are mainly 02 fault occurs in the power system i.e

(1) over voltage

(2) over current

→ So thyristor has to protected from thus 02 fault.

Over voltage Protection :

⇒ The thyristor subjected to over voltage :-


(1) Bad commutation (Turn OFF)

(2) short ckt condition clearing by ckt breaker

(3) Transient due to switching operation

(4) Lighting stroke.

clearing of over voltage fault

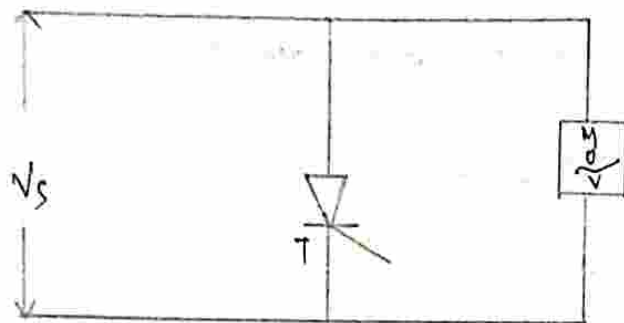

NON-LINEAR: High resistance at low voltage & low resistance at high voltage.

(i) For protection of thyristor from over voltage a non linear resistance (MOV \rightarrow metal oxide varistor) connected parallel with thyristor to be protected.

(ii) This protective device have falling resistance characteristics with increases in voltage.

* Varistor - Working


- High voltage - less resistance
- Low voltage - high resistance

(iii) At normal operating condⁿ MOV show high resistance, so load current flow through thyristor when over voltage condⁿ, occurs at that time MOV offer low resistance which produced a short out across thyristor & high voltage source discharge through the MOV & protect the SCR from over voltage.

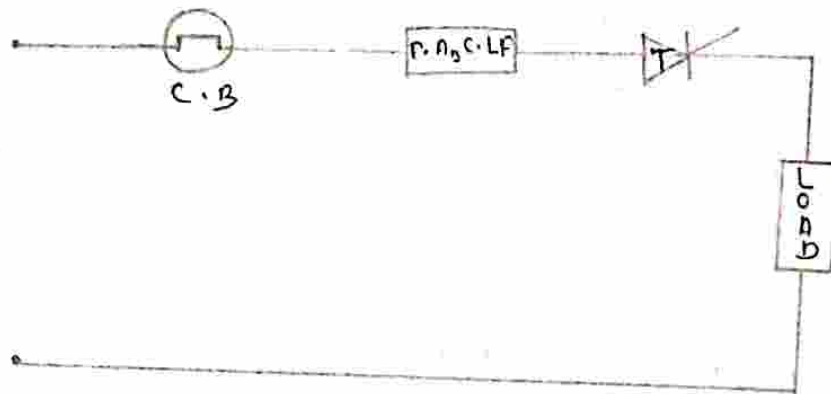(iv) Generally MOV silicon selenium thyristor diodes are used for over voltage protection.

Over Current protection :-


- ① The thyristor subjected to over current due to short ckt condⁿ of any of lines, lightning stroke.
- ② Sudden increasing of loads.
- ③ Line to ground faults.



F.A.C.L.F - First Acting Current limiting fuse.

- (i) During over current a heavy current pass through thyristor
- (ii) As the junction have some resistance ($J_1, J_2, + J_3$) it produced heat across the device due to IRt if it circulate for more time.
- (iii) The temperature with standing capacity of SCR is very small if high temp develop due to over current may damage device.
- (iv) So to protect the SCR from over current a Ckt breaker + F.A.C.L.F are connection in series with thyristor.
- (v) The CB is used to protect the thyristor against continuous over load for a long direction
- (vi) The F.A.C.L.F is used to protect the thyristor from over current for short direction.

Gate protection

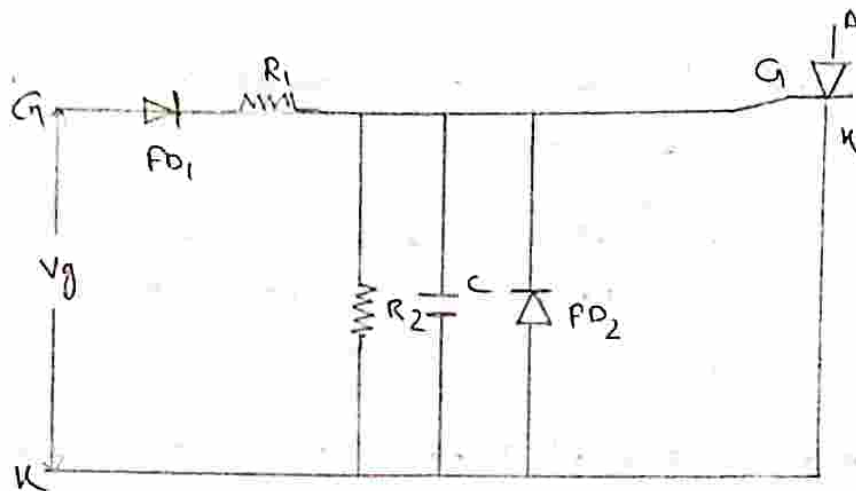

- (i) For turn on the SCR by Gate ckt method we applied Gate pulse betⁿ Gate & cathode so the necessity Gate pulse is given to Gate terminal in a control method.
- (ii) For giving Gate pulse in control manner we used different ckt elements which are connected in the above diagram.
- (iii) In the starting of the ckt a free wheeling diode is connected in series with the supply for allow only +ve pulse.
- (iv) The R_1 connected series the diode which will limiting the current in safe value.
- (v) Another resistance R_2 connected parallel with Gate & Cathode.
- (vi) For increasing the $\frac{dv}{dt}$ capability of the SCR for reducing the turn off-time. And increasing the holding & latching current.
- (vii) Capacitor 'C' removes high frequency component by connecting parallel which acts as filter ckt.
- (viii) The diode PD_2 avoids the flow of the -ve pulse from Cathode to Gate.


$\frac{di}{dt}$ protection :

- (i) A Thyristor require min^m time to spread current conduction uniformly through out the junction.
- (ii) If the rate of rise of anode current is very fast of the turn ON process a hotspot is created in the J_2 junction due to high temp.
- (iii) To avoid this creation of hotspots in the J_2 junction an inductor L_s is connected in series with SCR.

$\frac{dv}{dt}$ protection :

- (i) When anode is +ve w.r.t cathode & no Gate pulse is applied J_2 behaves like a capacitor & the total source voltage V_s appears across J_2 junction.
- (ii) Result a charging current start flowing if $\frac{dv}{dt}$ value is high the I_c value also high which is able to turn ON the SCR without giving any Gate pulse.
- (iii) This is known as mal operation of SCR which is called $\frac{dv}{dt}$ turn
- (iv) The C_s is parallel with device to prevent unwanted $\frac{dv}{dt}$ triggering & L_s also connected in series with C_s to limit the charging current.

TOTAL PROTECTION CKT OF SCR :-

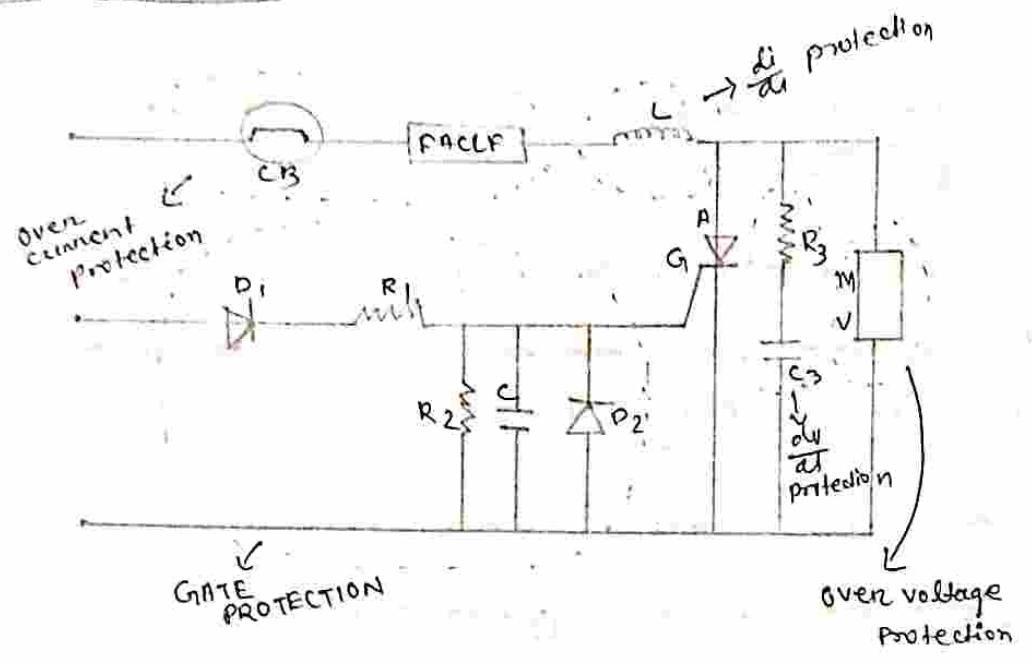


CHAPTER - 2


TRIGGERING CKT / FIRING CKT

- ⇒ To turn on the SCR by Gate triggering method we design triggering ckt.
- ⇒ During f/w blocking mode as J_2 junction is reverse biased +ve Gate pulse required to turn on the SCR by bringing it to f/w conduction mode.
- ⇒ So there are 4 types of firing ckt!-
1. Resistance or R-Triggering ckt
 2. R-C triggering ckt
 3. UJT triggering ckt
 4. Cosine low of triggering ckt


R-Triggering CKT

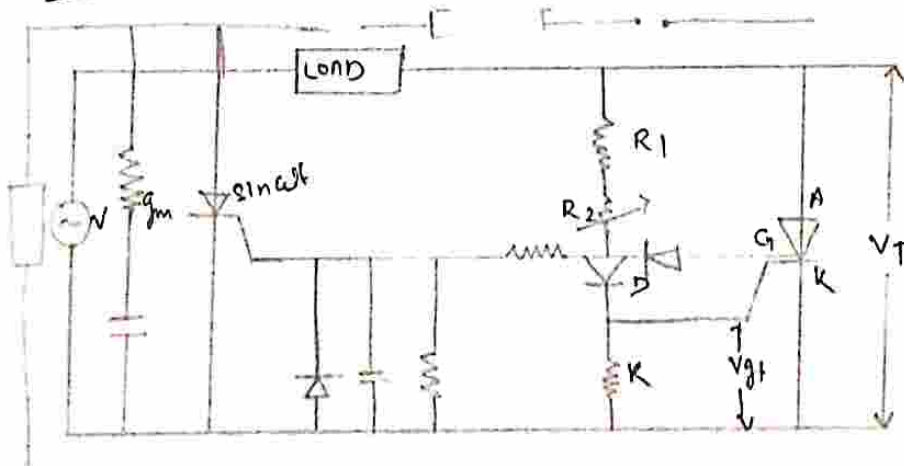

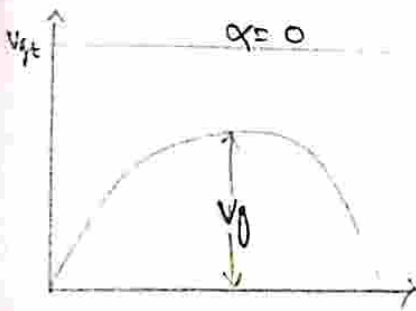- (i) The CRT shows a half control rectifier with R-triggering.
- (ii) The SCR conducts during only 1ve half cycle.
- (iii) Hence the conduction from $0-\pi$ & $2\pi-3\pi$ and show on.
- (iv) Let V_{gt} is the minimum voltage required at the gate to cathode to turn on the SCR.
- (v) The current through R can be varied by varying the resistance R_2
- (vi) If R_2 is large than the current value is small due to increase.
- (vii) So the V_g amount is small as V_{gt} is greater than V_g ($V_{gt} > V_g$) when $\alpha = 0$.
 $(\alpha = \text{firing (triggering) angle})$




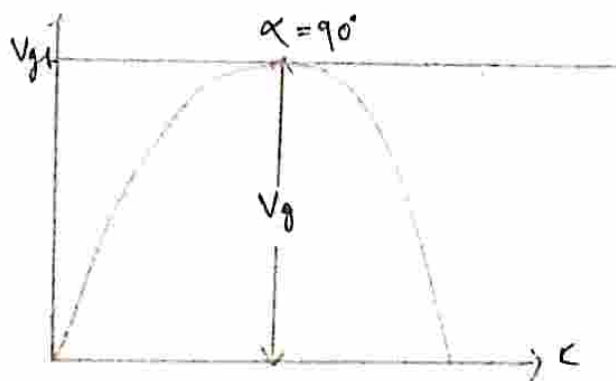- (viii) If R_2 is moderate it develop moderate amount of current flow through R and drop V_g in occurring.
- (ix) And the Condⁿ carries that $V_g = V_{gt}$ if $\alpha = 90^\circ$





(when R_2 is moderate)

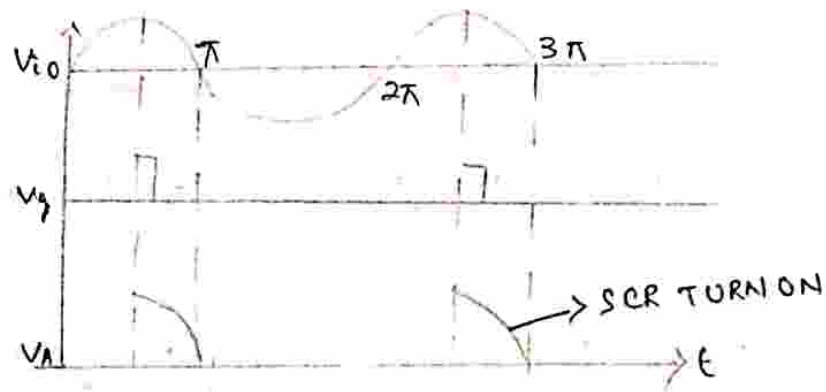(X) The voltage V_g attend the value V_{gt} at $\alpha = 90^\circ$ turn ON the SCR for a quarter cycle




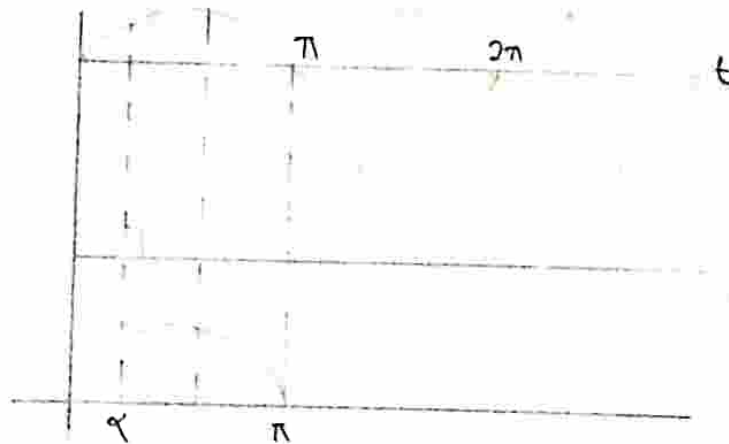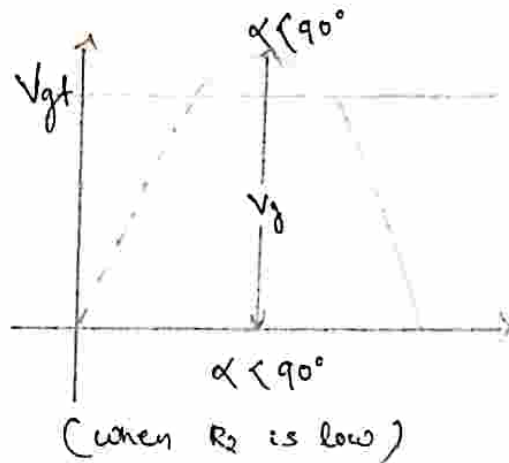(XI) When R_2 is low a heavy current starts flowing & V_g occurring at which is applied across Gate and $V_g > V_{gt}$ so SCR turns on at



⑫ In this triggering or firing ckt the α value lies betⁿ 0 to 90°
 $0 < \alpha \leq 90^\circ$

R-C Triggering ckt :-


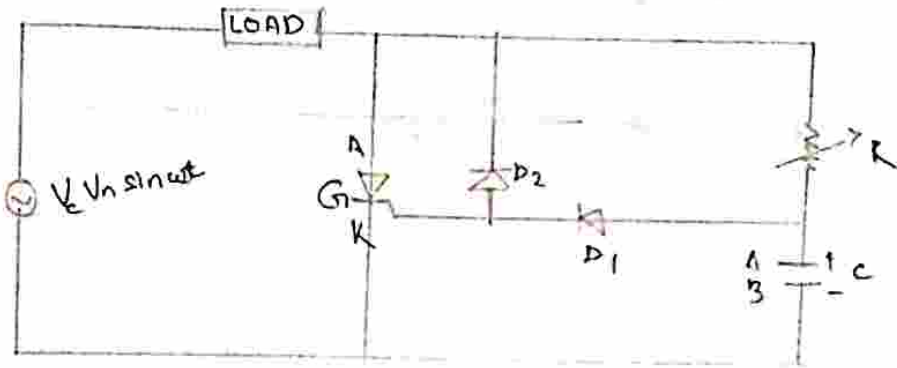


- ⑬ In this firing method the α can vary from $0-180^\circ$.
- ⑭ The above ckt consisting a series combination of a variable resistance 'R' & capacitor 'C'.
- ⑮ The capacitor 'C' connected across cathode & Gate through diode D_1 ; another diode D_2 used for charging of capacitor connected betⁿ D_1 & anode.
- ⑯ In the -ve half cycle of source capacitor charge up through D_1 & D_2 .
- ⑰ With low plate +ve & upper plate -ve.
- ⑱ At that time capacitor takes current through V resistance 'R' to raise up the voltage to V_{gt} & then V_m .
- ⑳ When capacitor attened the voltage $+V_{gt}$ then gate pulse moves through D_1 to Gate & turn ON the SCR.


(vii) This firing angle (allowing the value of V_{gt}) is depend upon the value of R .

(ix) If R is high then less amount of current is flow to charge up the capacitor and α value increases.

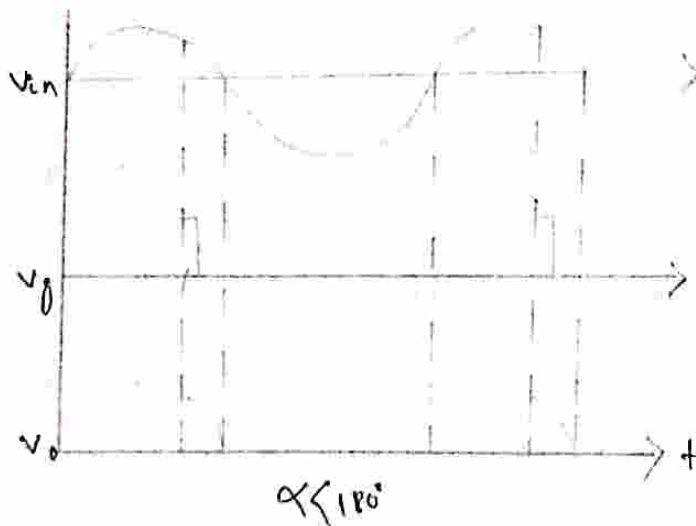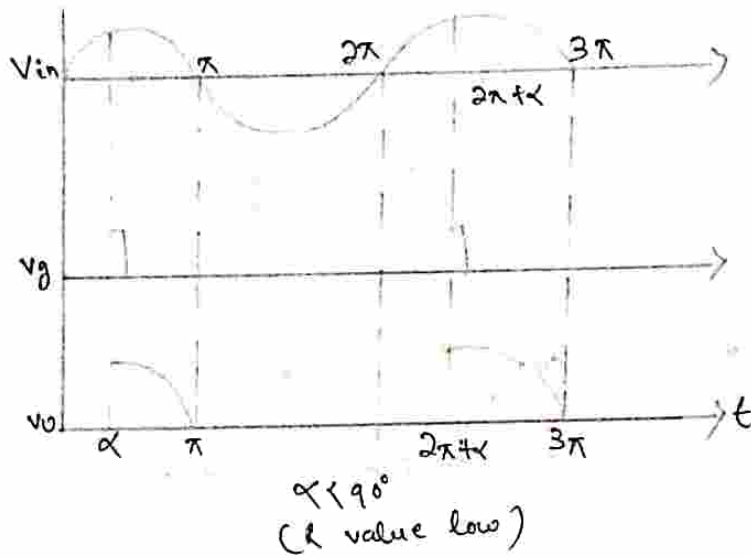(x) Where as if R is low then heavy current flow through capacitor & in less time it attend the value of V_{gt} and turn on the SCR.



PULSE TRANSFORMER TRIGGERING

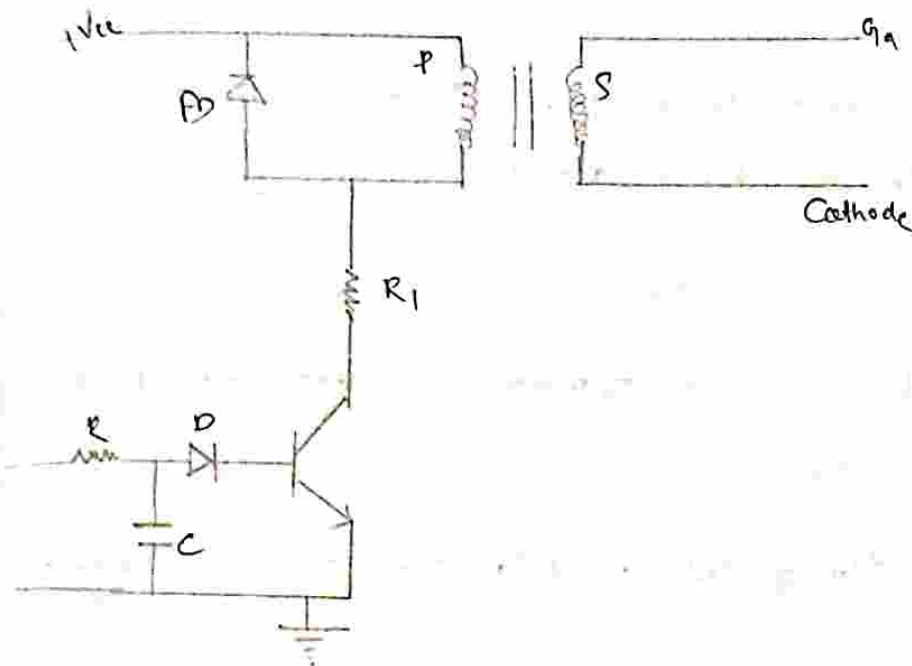

Pulse T/A :-

It is a small size T/A commonly used in thyristor triggering.

Ckt description

- ⇒ In this ckt diagram R, C + diode connected to base of transistor which is used to control the pulse o/p of pulse T/A.
- ⇒ When square wave i/p to the RC ckt it converts it into pulse.
- ⇒ Diode (D) eliminates the -ve part of the pulse.
- ⇒ When this +ve pulse applied to the base of transistor 'T' the transistor turns on & the voltage V_{cc} applied to the primary wdg.

→ there is a voltage induced across the secondary wdg.


→ And this secondary voltage used as trigger voltage of thyristor

→ when pulse is remove transistor is off. So a voltage of opposite polarity is induced across primary wdg.

Advantages

- (i) By this method a isolation between low voltage gate ckt + high voltage power ckt.
- (ii) By using one firing ckt used to turn on more than one thyristor.
- (iii) Here power drop decreases as compare to R + R-C triggering ckt.
- (iv) The layer is get reduced.

UJT Triggering ckt :

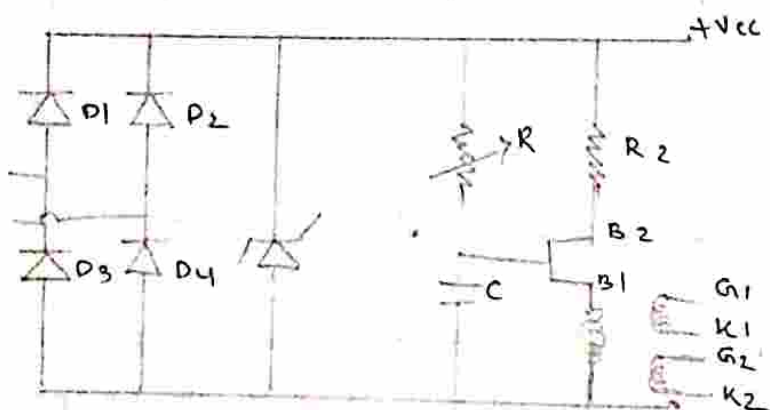

$E_{B2} + F/W$ Biased.

$E_{B1} \rightarrow R/V$ Biased.

(i) The unijunction Transistor (UJT) have 3 terminal device i.e. emitter, Base 1 & Base 2.

(ii) It consist of lightly doped N-layer as base & or heavily doped p-type base & injected inside it.

(iii) The 3 leads are welded to the 3-layer so there are or 2 junction form i.e. EB_1 & EB_2 junction.

(iv) This 2 junction are acts or resistance i.e. R_{B1} & R_{B2}

(v) The emitter leads is placed nearer to the B_2 leads so EB_2 junction is P/W biased as the B_1 leads is away from 'E' so EB_1 junction is reverse biased.

(vi) If EB_1 junction is break the conduction start through UJT.

(vii) The above CKT shows 4 diode (D_1, D_2, D_3 & D_4) acts as rectifier which convert A.C to D.C & V_{ac} applied across the UJT.

(viii) A zener diode connected across the CKT to maintain the constant voltage.

(ix) A variable resistance 'R' & a capacitor 'C' acts as R-C charging CKT used for charged the capacitor 'C'.

(x) By the variable resistance 'R' we control the firing angle ' α ' i.e. if R value is high then capacitor hence α increases and if 'R' is low & vice versa.

(xi) when the capacitor charge reaches to V_c which is actⁿ betⁿ E & B_1 result the break down of junction.

(xii) As a result current ' I_2 ' flowing through $R_1 \rightarrow B_2 \rightarrow E \rightarrow R_2$ and the pulse T/A.

(xiii) The pulse T/A shows transformation in the secondary and voltage applied to the thyristor ckt.

Phase Controlled Rectifier Converter

=> The conversion of A.C to D.C is known as Rectification.

=> For power conversion or power ckt is form A.C to D.C we used thyristor in place of diode.

=> There are 02 types of rectifier.

(1) Uncontrol Rectifier

(2) Control Rectifier.

Uncontrol Rectifier

(i) In case of uncontrol rectifier for rectification we used power diodes because the fixed value of A.C voltage converted into fixed value of D.C voltage.


(ii) It is used in case of some low power device where control of o/p voltage is not required.

(iii) It is low cost & simple ckt.

Control Rectifier

- (i) Rectifier CIR using thyristor known as control rectifier because thyristor is a control device.
- (ii) The thyristor o/p can be vary by varying the firing angle α hence o/p value of dc also vary.
- (iii) Since thyristor is a control device it is available in high current, high voltage, high power rating.
- (iv) It may be either 1ϕ or 3ϕ as i/p
- (v) It may be either semi converter or fully converter having different quadrant operation.

Classification of Converter :

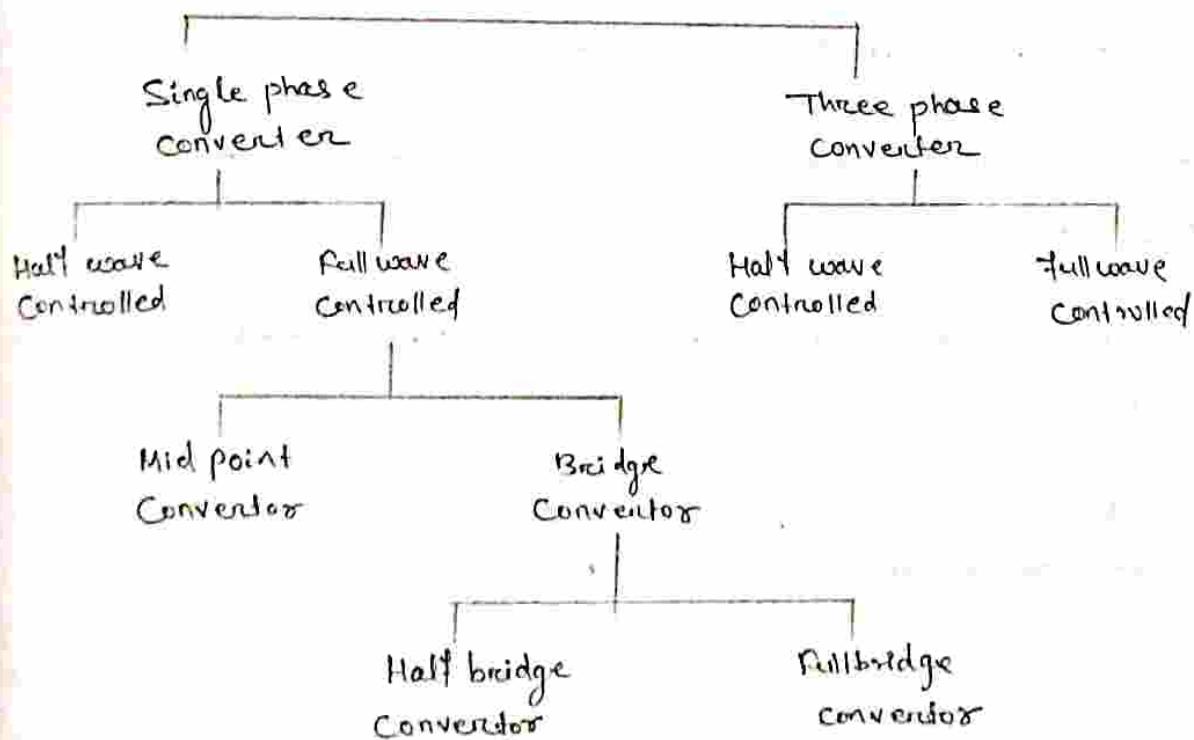



Application of Converter :

- (i) For high voltage D.C. Transmission.
- (ii) Speed control of D.C. motor.
- (iii) It also used for battery charging.
- (iv) Magnetic power supply
- (v) Excitation control of alternator

Principle of operation of Converter

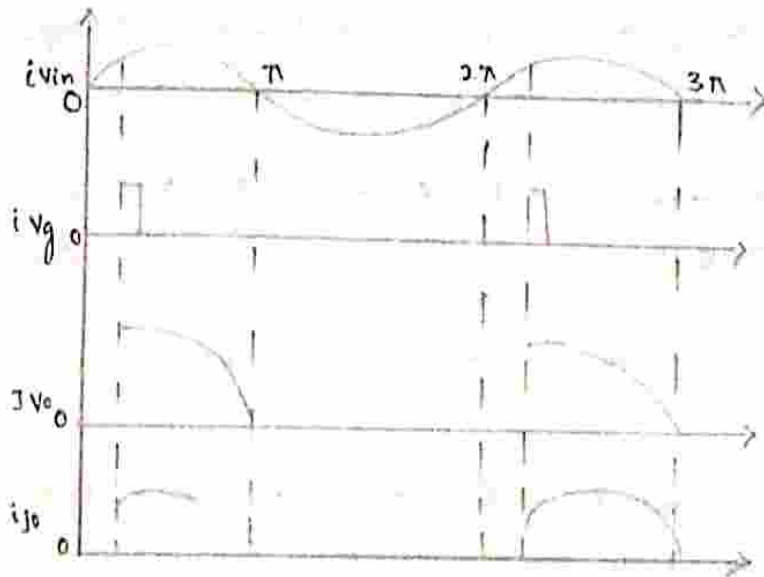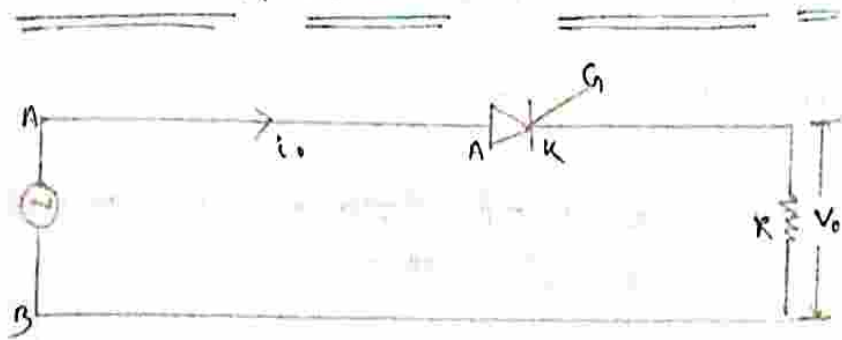- (i) A SCR can be conducts only when anode voltage is +ve & cathode is -ve & Gate signal is applied.
- (ii) The load current blocks upto it is not triggered.
- (iii) When we applied gate pulse with some delay angle / firing angle (α) it would start conducting.
- (iv) So a thyristor may conduct during +ve half cycle i.e. $\alpha - \pi$, $2\pi + \alpha - 3\pi$ and so on.
- (v) If thyristor is replaced by a diode then it conduct $0 - \pi$, $2\pi - 3\pi$ and soon as it is a Un-Control device.
- (vi) So by varying the firing angle α of thyristor which a vary rough o/p voltage as per requirement.

2 ϕ half wave control rectifier or converter with R-Load



- (i) The above CLK shows 2 ϕ half wave converter with R-Load.
- (ii) The SCR is connected to a load Resistance (R) which is fed by a.c supply $V_s = V_m \sin \omega t$.
- (iii) So the SCR is F/W biased when the +ve half cycle appear across it i.e. $0-\pi$ and $2\pi-3\pi$ and so on.
- (iv) During the half cycle A-point +ve, B point is -ve & the thyristor is subjected to F/W biased.

(V) So as soon as gate pulse is given with firing angle α it starts conducting and o/p voltage appears across the load.

(VI) So it is conduct upto $\alpha - \pi$ & $2\pi + \alpha - 3\pi$

(VII) When -ve cycle appears at πR of SCR subjected to reverse bias condⁿ and hence it is off.

(VIII) And again able to trigger with +ve cycle seen across it so by the conduction of SCR we element -ve half cycle and o/p seen is pulsating dc or unidirectional a.c

(ix) The o/p voltage seen across load is given by the

$$V_o = I_o R$$



(x) The different current & voltage curve are shown in the above fig.

(xi) ~~Since thyristor is a control device it is available in high current, high voltage, high power rating.~~

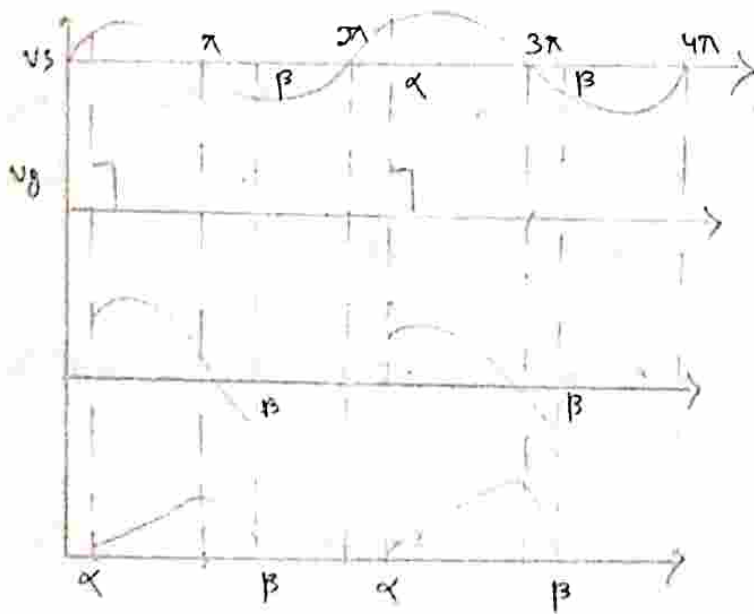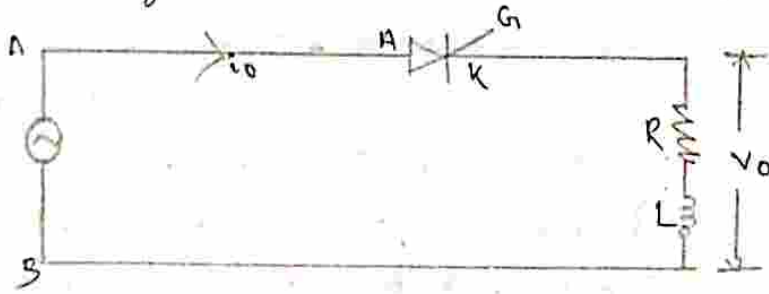(xii) \rightarrow

Single phase half wave converter with R-L Load :

- When load have inductive then the resistance and inductance are fed by source.
- Inductor has a property which does not allow sudden changes of current i.e either increasing or decreasing.
- The current vary across the inductor is according to exponentially.



Operation



- The above CKT diagram show semi converter or 1ϕ half wave converter with R-L load so it is conduct only during +ve half cycle.
- At angle α when gate pulse is given to SCR it start conducting & voltage across the load is same as the source voltage with R-L load.
- The SCR conduct upto π and $\pi - \beta$ since the load inductance L forces the load current to in gradually reaches max^m and then begins to decrease (inductor dose not allow the sudden change of current), so even through ~~of~~ the source voltage comes to zero and the current reduces slowly to zero.
- From $\alpha - \pi$ V_o & I_o which is appearing & flowing through load from source is +ve hence power is +ve hence power flow from source to load.
- From $\pi - \beta$ I_o is +ve but V_o is -ve the power is hence -ve.
- Hence the power is feed back to source. This is called recycling.
- The recycling is continuous the energy in the inductor given back to the source. The average o/p voltage get reduces due to -ve segment.

∴ If larger the inductance then larger the -ve area & hence lesser is the average o/p voltage & vice-versa.

→ When SCR is triggered due to V_o , it starts flowing from $\omega t = \alpha$ & gradually increases & reaches max^m .



→ And after π it start decreasing upto ' β ' known as extinction angle and hence the SCR conducts $\beta - \alpha = \gamma$ known as conduction angle.

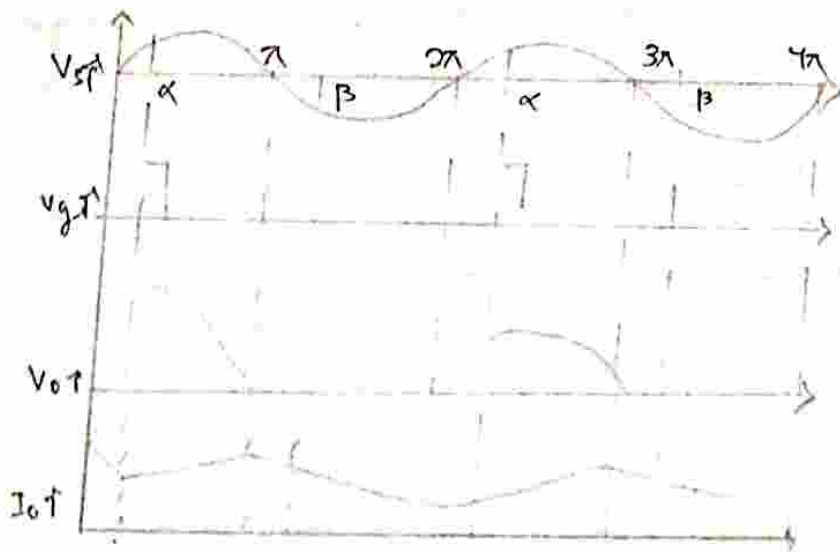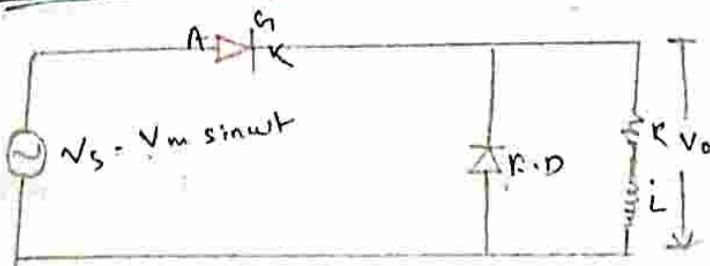1 ϕ half wave control rectifier with R-L load & free wheeling diode



-) Here a P.D connected across the load for free wheels (easy move charge of inductor inside itself).
-) During +ve half cycle at angle SCR is triggered by giving gate pulse and source voltage V_s appears across load i.e V_o
-) At $\omega t = \pi$ source voltage is zero & tends to reverse now P.D is fully biased.
-) As a result load current I_o immediately transfers from SCR to P.D & SCR is turn off and o/p voltage V_o became zero.
-) Now P.D recycle or free wheeling the load current as the ckt passes high inductance.
-) And it maintain to a certain load current until it does not decay to zero.
-) Again when SCR is triggered at $\omega t = 2\pi + \alpha$ o/p voltage seen again across the load to maintain the load current.
-) Advantages the of using P.D:-
 - ① Now the wave form of load current is improve.
 - ② Improvement of o/p. voltage.
 - ③ Input P.F also improved
 - ④ Load performance improve due to more power.

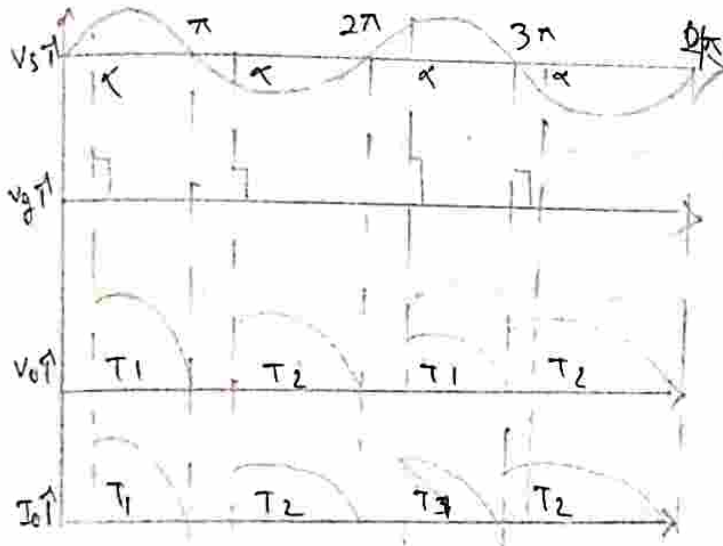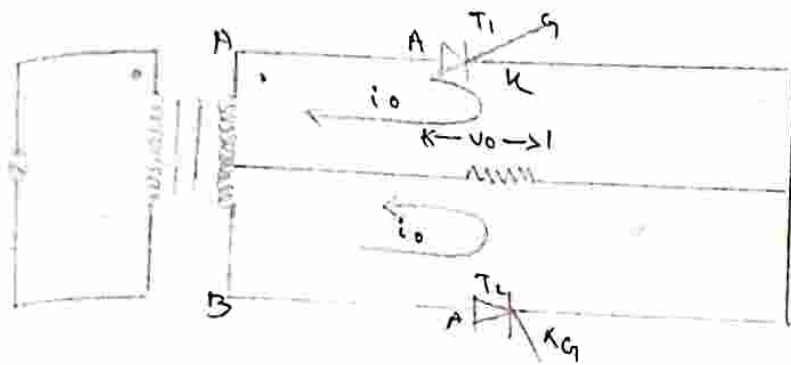Midpoint full wave type Converter with R-Load





∴ In full wave midpoint type convert with resistive load the circuit T_1 & T_2 connected in 2nd disting branch (A & B) & feed current to resistive load 'R' which is get centre tap.

1) During the half cycle A-point is +ve B-point is -ve, hence SCR T_1 is f/w biased & T_2 is reverse biased.

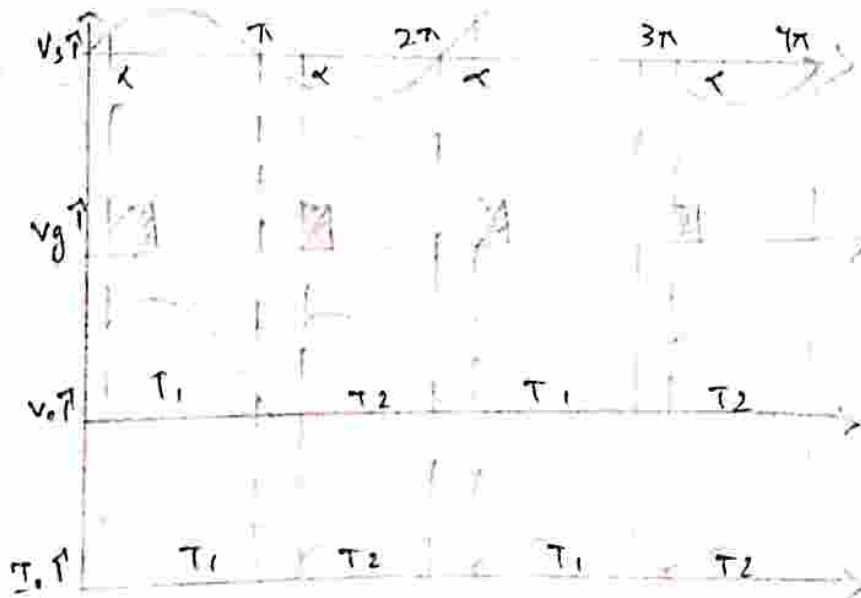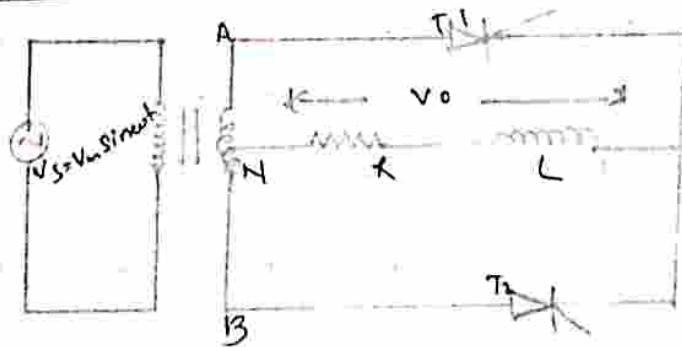2) T_1 turn on at $\omega t = \pi$ by giving gate pulse so load current start flow in o_f across appearing upto $\omega t = \pi$.

- At $\omega t = \pi$ the source voltage $V_s = 0$ and T_1 turn off & -ve half cycle starts.
- During -ve half cycle B-point is +ve circuit point so T_2 is forward biased and T_1 is turn off.
- At $\omega t = \pi + \alpha$ T_2 turn on by giving gate pulse & load current start flowing across the load R is same direction in at that of before.
- So o/p voltage is also same as that of before i.e. undistorted.
- T_2 conducts upto $\omega t = 2\pi$ and turn off As reverse voltage reached zero.
- Again T_1 turn on at $\omega t = 2\pi + \alpha$ and above cycle repeated.
- This assume same α firing angle (α) and hence they share same load current.

Mid point Full wave Converter with R-L Load



The ckt diagram shows a full wave converter with R-L load.

During the half cycle 'A' is the circuit B. So T_1 is F/W biased and T_2 is reverse biased.

At $\omega t = \alpha$ gate is given and T_1 is fired & o/p voltage seen across load and current is flowing through the load shown in the fig.

During the interval $\omega t = \pi - \pi + \alpha$ before triggering of T_2 (as -ve half cycle start + T_2 is F/W biased)

The load current is handed over from T_1 to F.D. and flow in same direction by reducing α as a result the -ve half cycle seen during this duration is get eliminating.


Again $\omega t = \pi + \alpha$ " T_2 " is triggering by giving gate pulse and load current is maintain by T_2 instead of F.D till $\omega t = 2\pi$

At $\omega t = 2\pi$ there is initiation of +ve half cycle hence T_2 is F/W

During the interval $\omega t = 2\pi - (2\pi + \alpha)$ again to maintain by F.D instead of T_2 by eliminating -ve

half cycle and current direction same.

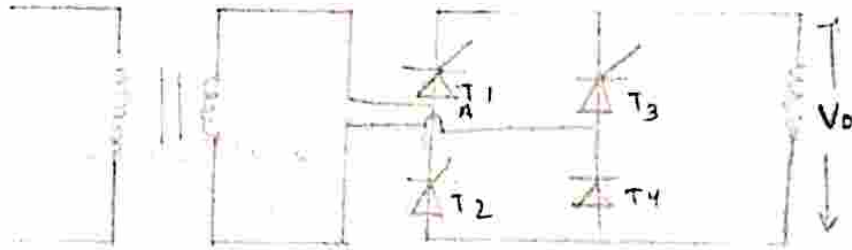1 ϕ Fully Control Bridge Converter with R-Load



- =) The above fig. Shows 1 ϕ fully control bridge converter with R-load
- =) Here 4 nos of SCR is (T_1, T_2, T_3, T_4) are connected and form a bridge ckt such that T_1, T_2 & T_3 are in same branch.
- =) The T/F secondary is connected to bridge ckt at point A & B and the bridge ckt is connected across R load.
-) During +ve half cycle A-point +ve w.r.t B-point.
-) Hence T_1 & T_4 are fwd biased.
-) When gate pulse are given to T_1 & T_4 it start conducting and load current flow through.
 $A \rightarrow T_1 \rightarrow R \rightarrow T_4 \rightarrow B$.

nce off voltage seen across the load. They conduct upto $\pi - \alpha$.
 -ve half cycle starts.

During -ve half cycle B-point is +ve w.r.t A-point Hence T_2 & T_3 are f/w biased.

When gate pulses are given to T_2 & T_3 Current starts flowing
 $B \rightarrow T_3 \rightarrow R \rightarrow T_2 \rightarrow A$ and o/p voltage (V_o) seen across the load
 which is shown in the wave form.

T_2 & T_3 conducts upto end of -ve half cycle and this cycle
 repeats for other half cycle.



As the current direction is same across the load hence the o/p
 is unidirectional.

1 ϕ Half control Bridge Converter with R-L load :

It has 02 alternate configuration i.e (1) Symmetrical configuration.
 (2) Asymmetrical configuration.

In this case 02 SCR are replaced by 02 power diodes



(1) Symmetrical configuration

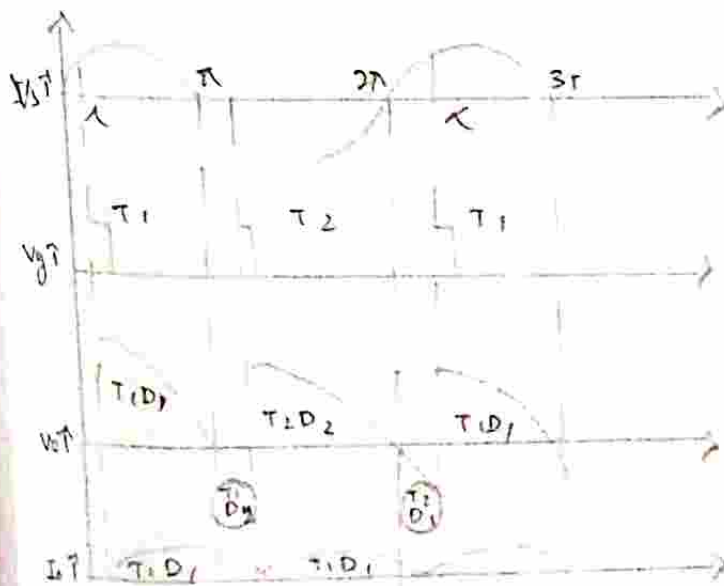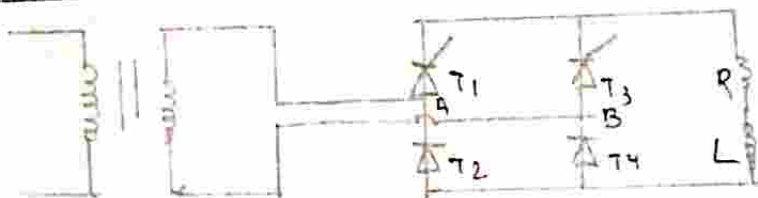

(Symmetrical configuration)

- During the half cycle the SCR (T_1) turn on at firing angle α .
- The current start flowing in the path $A \rightarrow T_1 \rightarrow R \rightarrow L \rightarrow D_1 \rightarrow B$
- And source voltage appears across the load. Assume that the load inductance is very high to produce continuous a constant load current.
- T_1 & D_1 flow upto $\omega t = \pi$, as source voltage is reverse so D_2 is now forward biased.
- D_1 turn off due to reverse biased condition.
- Hence the charge of inductor free wheels by the T_1 & D_2 and the load current flow in the path $T_1 \rightarrow R \rightarrow L \rightarrow D_2$.
- The load is s.c. ~~reduces to zero~~ during interval $(\pi + \alpha)$ and voltage reduces to zero.
- At $\omega t = \pi + \alpha$ T_2 turn on & reverse voltage flow through. $B \rightarrow T_2 \rightarrow R \rightarrow L \rightarrow D_2 \rightarrow A$
- T_1 turn off when T_2 fired & o/p voltage seen across the load during -ve half cycle due to T_2 & D_2 upto $\omega t = 2\pi$
- During the interval $\omega t = 2\pi - \alpha$ & d before triggering of T_1 & ωt off as reverse biased but D_1 turn on and current flow through. $R-L \rightarrow D_1 \rightarrow T_2$ which is s.c.R the load and this above cycle is repeated.

Asymmetrical Configuration

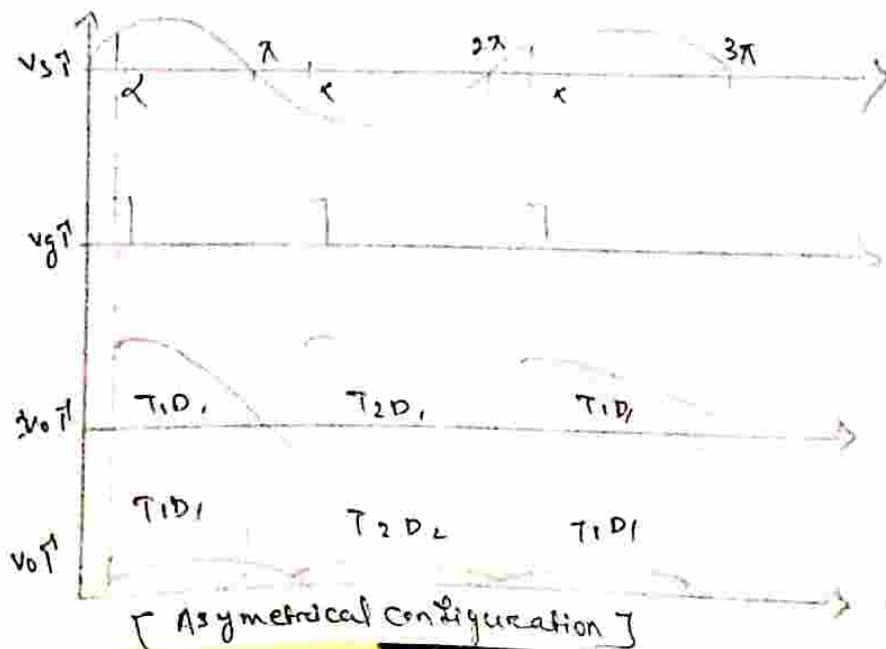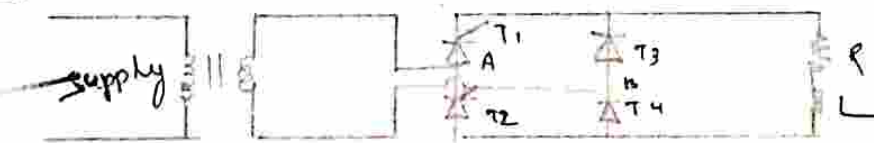

In this configuration the 2 thyristors T_1, T_2 and 2 Diodes D_1, D_2 are placed in same branch.

For the above bridge configuration is connected across load R & L . During +ve half cycle "A-point" is +ve w.r.t "B-point" so T_1 & D_2 are fwd biased.

When T_1 fired load current to start flowing through.
 $A \rightarrow T_1 \rightarrow R \rightarrow L \rightarrow D_2 \rightarrow B$ which are conducts upto $\pi + \alpha$.

During -ve half cycle at B-point +ve w.r.t A-point so D_1 is fwd biased.

2. The charge contain by the inductor is free wheel D_1 & D_2 from $\pi + \alpha$ to 2π when " T_2 " fired at " $\pi + \alpha$ " during -ve half cycle the load current gradually increased and flow through the path

$B \rightarrow D_1 \rightarrow L \rightarrow T_2 \rightarrow A$ and the off v_s & i_o are seen in the above wave form.


3) As the current direction across load is same as that of before so the v_o is unidirectional.

4) Again during the initiation of +ve half cycle from $2\pi - 2\pi + \alpha$, D_2 is fwd biased and charged store in inductor free wheels by D_1 & D_2 .

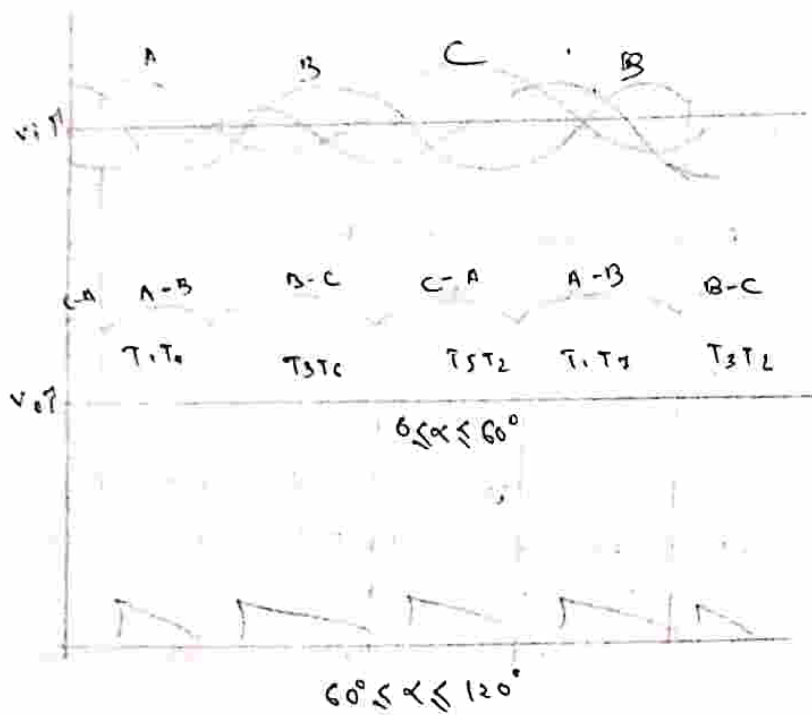3) Full wave converter

Self fully control bridge converter with R-LOAD!





- The above CKT shows 3 ϕ fully Converter with R-load
- Here pairs of SCR T_1T_4 , T_3T_6 & T_5T_2 are placed in same branch
- There are 3 points A, B, C where 3 ϕ supply is fed to the above bridge CKT.
- The 3 ϕ wave form of source is shown in the above fig.
- There are 6-mins mark on source voltage wave form i.e. P, G, C, S, T, U
- At point 'P' A & C are same polarity i.e. A-C=0 or C-A=0 after point - P, A is more +ve and 'B' is more -ve so now T_1 & T_4 are fwd biased.
- As soon as they are triggered i.e. $0 \leq \alpha \leq 60^\circ$ then the o/p seen is a continuous mode and if $60^\circ < \alpha < 120^\circ$ then the o/p wave form is a discontinuous mode
- During the interval pf a current flow through $A \rightarrow T_1 \rightarrow R \rightarrow T_4 \rightarrow B$ and the o/p voltage seen across the load.
- After point - B 'B' is higher polarity and 'C' is more -ve so T_3 & T_6 are fwd biased and the load current start flowing $B \rightarrow T_3 \rightarrow R \rightarrow T_6 \rightarrow C$

At point-Q the T_1 & T_4 SCR are automatically turned off due to voltage commutation & T_3, T_6 are conduct Q to R.

The mode of o/p of both the SCR are depend upon the firing angle

And the interval from 'R' to 'S', 'c' is positive and 'A' is more -ve so T_5 & T_2 are p/w biased and the current start flowing.

$C \rightarrow T_5 \rightarrow R \rightarrow T_2 \rightarrow R$

The current direction across the load is same at every interval (P \rightarrow a, Q \rightarrow R, R \rightarrow S, S \rightarrow T) hence the o/p is unidirectional.

INVERTER


Inverters!

- Inverters are derived from the word inversion i.e. to change from one state to another state.
- So inverters are power electronics devices which convert d.c. electrical energy to A.C. electrical energy.
- Inverter is a device which convert d.c. power to A.C. power at desired voltage + frequency.


Application of Inverter Ckt

- ① Variable speed of AC motor drives
- ② Induction heating in the industrial for melting of ores.
- ③ UPS (Un-interruptable power supply)
- ④ Stand by aircraft power supply.
- ⑤ HVDC transmission line where long dist d.c. voltage converted into a.c. voltage.


Classification of Inverter :

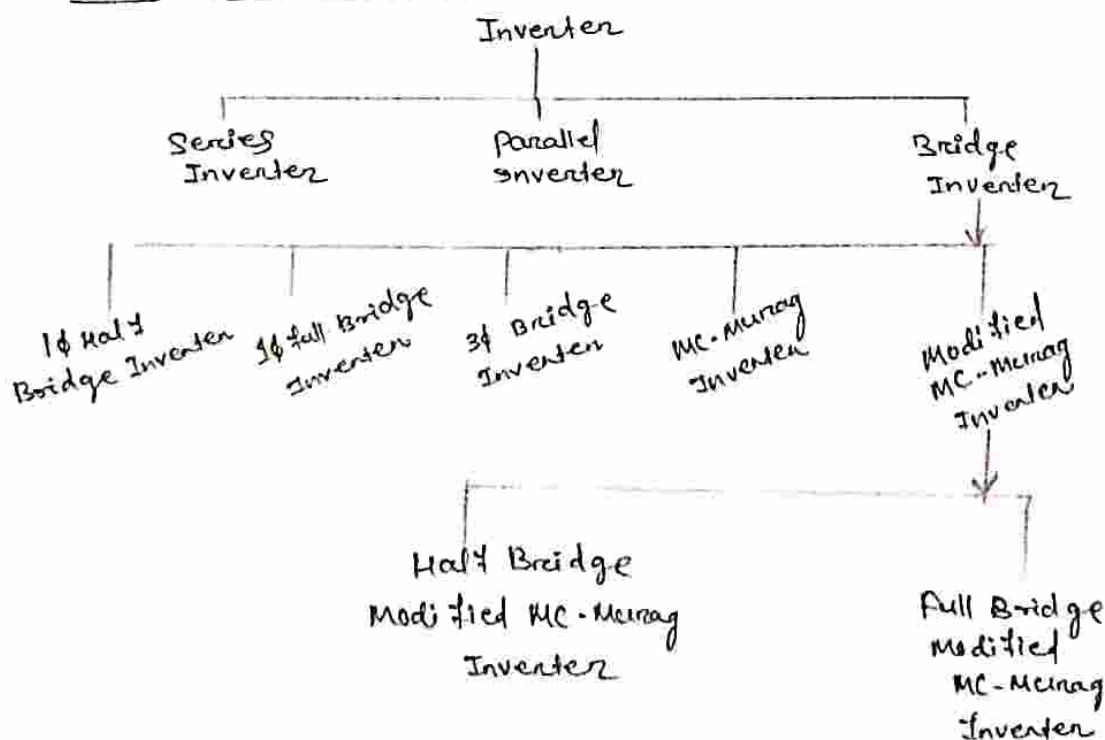


Source Inverter

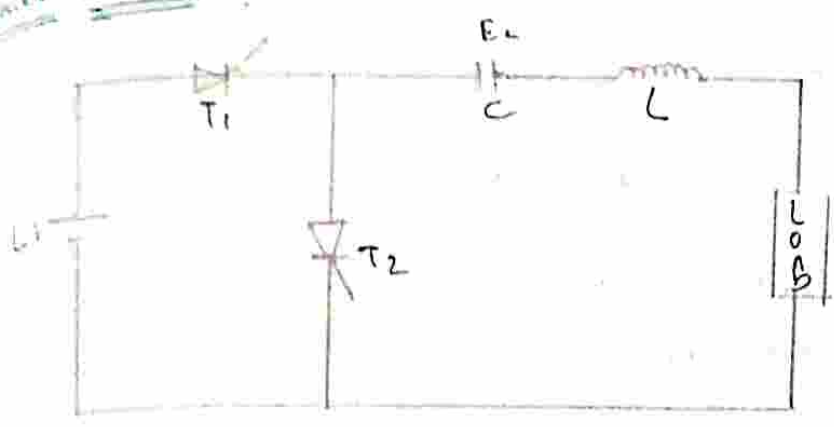


Mode-I

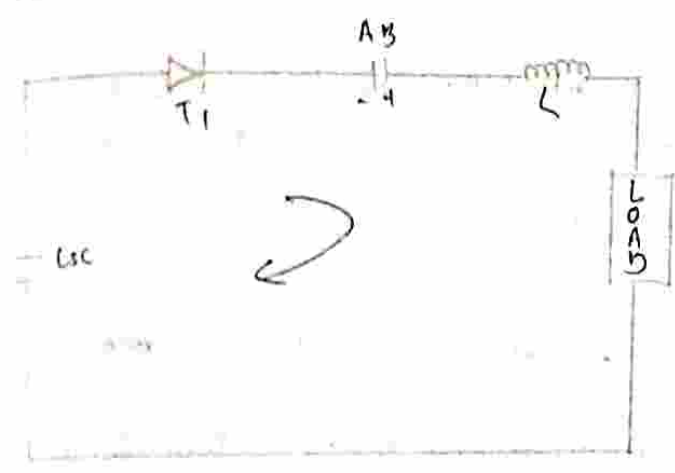

Mode-II

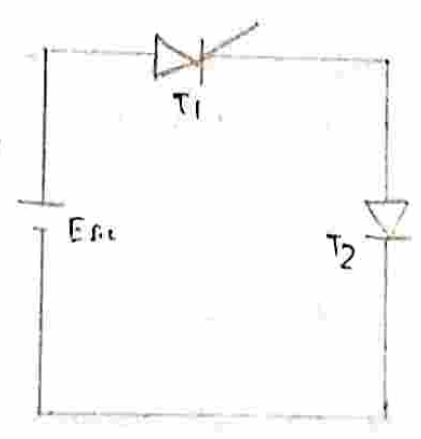

Mode-III

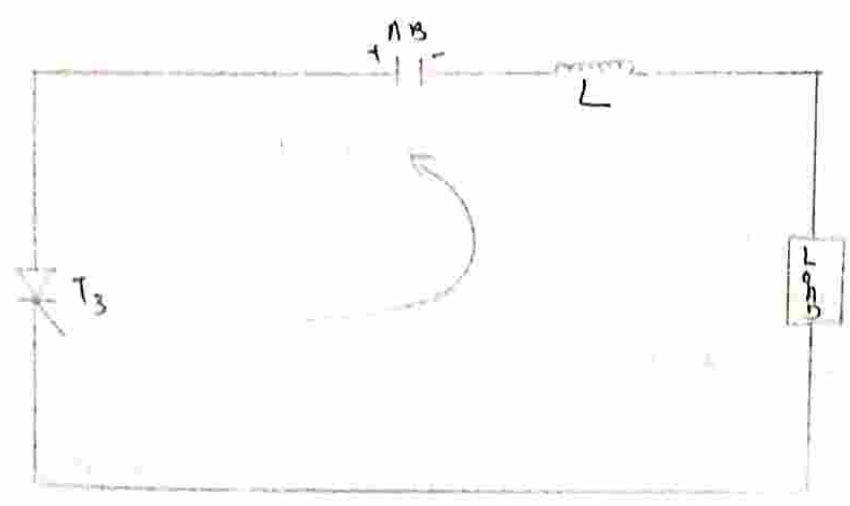

CKI Description

- ⇒ Here 2 SCR $T_1 + T_2$ are used for inverting purpose.
- T_1 is the main SCR connected across d.c supply.
- L & C are commutating element which are connect in series with load resistance R_L .
- T_2 is connected betⁿ T_1 terminal & load terminal for free wheel the charge of capacitor.
- As the commutating component L & C are connected in series with load resistance R_L so it is known as series inverter.
- The series R-L-C ckt formed a underground ckt.
- The op frequency of inverter ranges from 800 Hz to 100 kHz.
- So the size of commutating components reduced for this high frequency.

Principle of operation of the ckt

Mode-I

- ⇒ Let capacitor have initial charge of E_c .
- When SCR ' T_1 ' is triggered by giving gate pulse T_1 start conducting & current flow through R-L-C ckt.
- So load current flow through $+E_d \rightarrow T_1 \rightarrow A \rightarrow B \rightarrow L \rightarrow R_L \rightarrow E_d^-$
- ⇒ As the current flow through R-L-C series ckt it produced oscillation/frequency associated with load current.
- ⇒ When load current reaches it peak value (I_m), the capacitor voltage reaches to E_d .

When the capacitor has voltage of " $V_{dc} + E_{dc}$ " and it does not allow for there current flow towards load as source voltage is less than capacitor voltage & T_1 is turn off.

Mode - II

The SCR ' T_2 ' should not be triggered immediately after the current through T_1 reduces to zero.

If T_2 triggered without time delay, the battery source get shorted through T_1 & T_2 & get damaged the battery.


So in mode II operation no SCR in conduction mode.

Mode - III



In mode III operation SCR ' T_2 ' triggered after some time delay which cause initiation of -ve half cycle as current through the load is reverse.

The capacitor discharge through ' T_2 ' which cause giving rise to -ve half cycle across load. So current flow through the path,
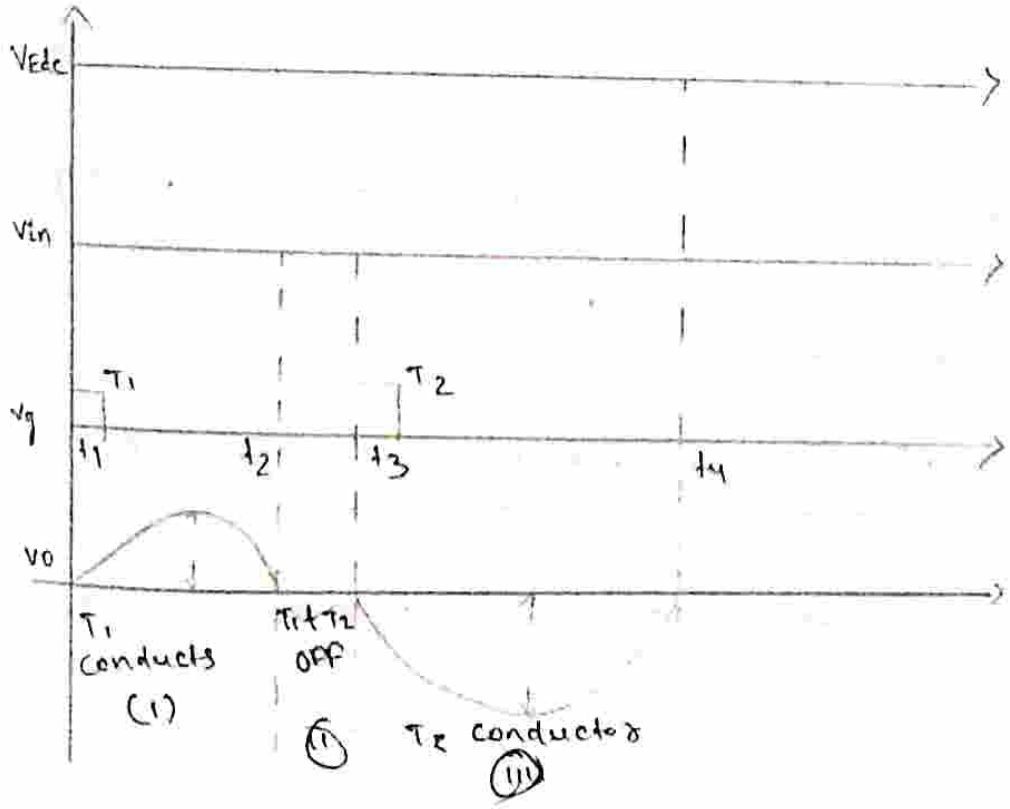
$$A \rightarrow T_2 \rightarrow \text{Load} \rightarrow L \rightarrow B$$



Parallel Inverter

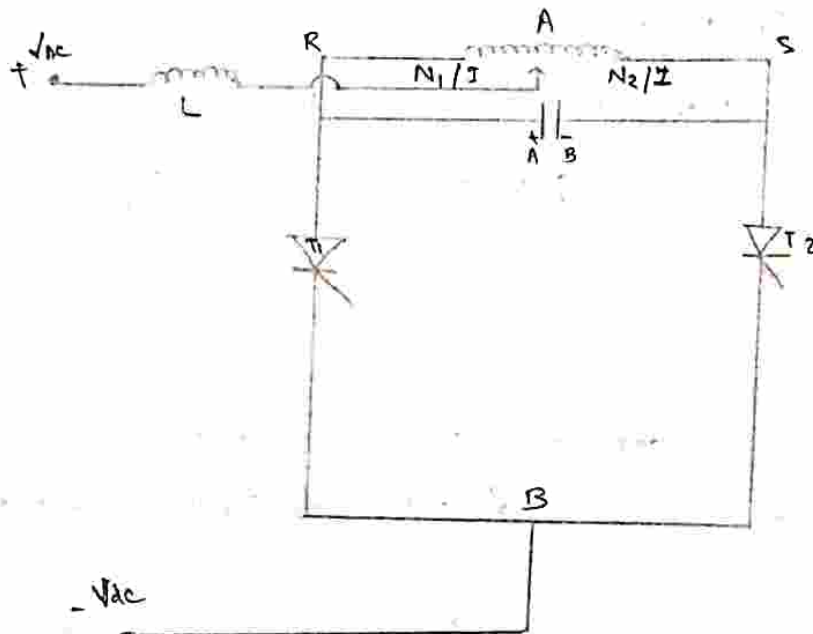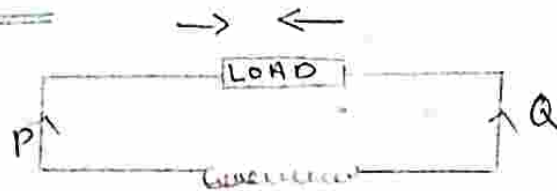

This is known as parallel inverter then 'c' is connected ^{inverting} parallel across the load.

Ckt description

- ⇒ There is a center tap T/P i.e. the primary is centre tap where 2 thyristors T_1 & T_2 are connected.
- ⇒ Here capacitor 'c' is connected parallel with load via T/P
- ⇒ The inductor 'L' connected series with supply which is centre tap in the primary wdg.
- ⇒ The function of L is to make the source current constant in order to avoid instant discharge of capacitor.
- ⇒ The o/p wave form of this inverter is in the form of square.

Principle of operation


Mode-I

- At the time $t = 0$ T_1 turns on.
- The current starts flowing through the left half of the primary $+V_{dc} \rightarrow L \rightarrow A \rightarrow R \rightarrow T_1 \rightarrow B \rightarrow -V_{dc}$
- Initially capacitor has "A-plate +ve and B-plate -ve"
- As primary wdg's are closely coupled and they are same no. of turns ($N_1/2$) so same voltage induced in the right half.
- Now capacitor is charged by $2E_{dc}$ of primary wdg which cause changing of polarity of capacitor "A-plate is +ve & "B-plate" is +ve.

Mode-II

- At time $t = t_0$ commutating capacitor 'C' applied a voltage $2E_{dc}$ across T_1 so due to rfv biased condition and T_1 is turn off.
- Now T_2 turns on by giving Gate pulse so current starts flowing in the right half primary wdg in the direction $+V_{dc} \rightarrow L \rightarrow A \rightarrow S \rightarrow T_2 \rightarrow B \rightarrow$

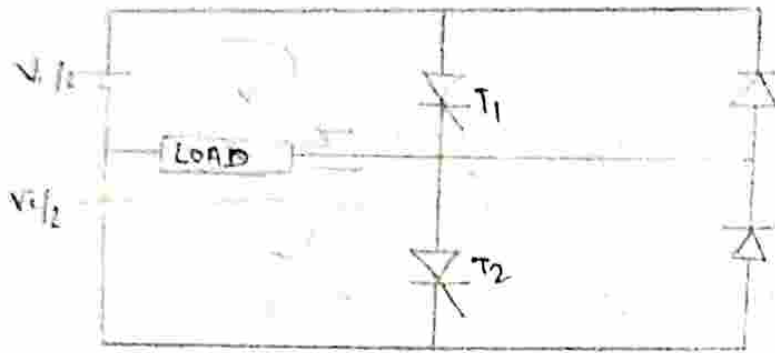Single phase half Bridge Inverter with R-Load



Ckt description

- ⇒ The above ckt shows 1 ϕ half wave bridge inverter with R-load.
- ⇒ This type of inverter is very popular and commonly used for DC to AC conversion because it is easily extended for multiphase operation.
- ⇒ In the 1 ϕ bridge inverter there is no need transformer because the o/p voltage can be stabilised by the help of bridge ckt.
- ⇒ It consist of 02 source i.e $V_i/2$
- ⇒ There are 02 switches D_1 & D_2 diodes for freewheeling action. If the load is inductive or Capacitive.
- ⇒ The 02 SCR T_1 & T_2 acts as 02 switches for controlling the o/p voltage.
- ⇒ Here the 02 thyristors T_1 & T_2 able to generate ac by using 02 difference source for giving rise to 02 individue half cycle so it is known as 1 ϕ half bridge inverter.

Operation

When T_1 triggered is by giving gate pulse at time T_m to T_1 ,
start conducts and it is conducts up to $T = t_1$ which is the
interval $(t_1 - t_0)$ & having frequency $f = \frac{1}{t_2 - t_0}$

$$= \frac{1}{T} = (\text{half of period})$$

and commuted after $T = t_1$ as a result it gives half cycle of
operation having frequency

$$F = \frac{1}{T}$$

At $T = t_1$ again gate pulse is given to SCR T_2 . The current start
flowing through the load is opposite direction as that of previous
one.


and it again conducts upto $T = t_1$ such that the time period
 $T = t_2 - t_1$ which is same as that of before and in decuss a
opposite cycle across the load having frequency

$f = \frac{1}{T}$ and forcibly commutated at


$T = t_2$ and above cycle repeated

the diodes are used for if the load is inductive but if the
load is non inductive the diodes are not use.

Wave form :

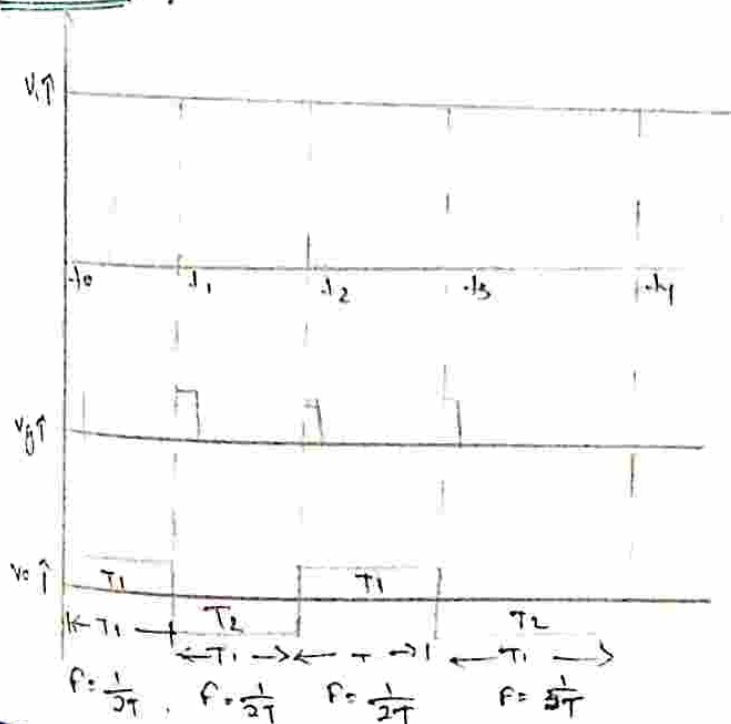

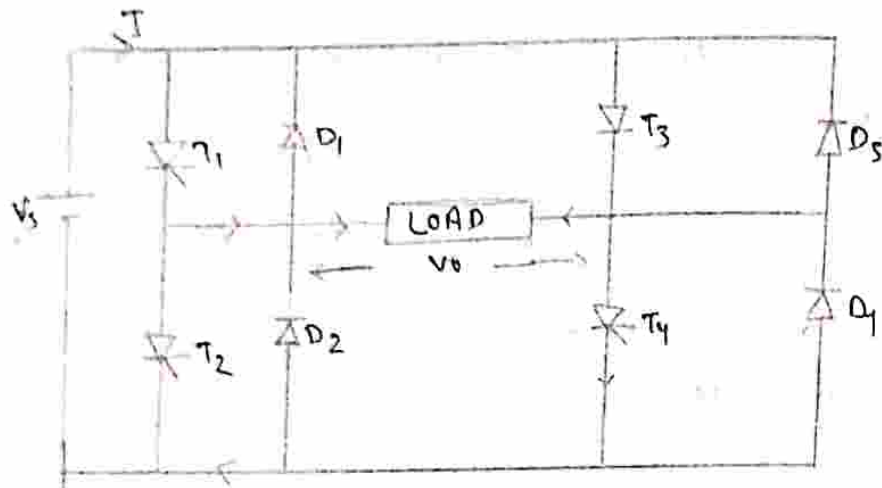Single phase Full Bridge Inverter with R-Load



- ⇒ In case of half bridge inverter or different sources & leads, of supply are required for converting D.C to A.C so for overcome this problem the full bridge inverter is used.
- ⇒ As there is single source is used for inverting so it is known as full bridge inverter.

Ckt description

- ⇒ The ckt contain 02 pairs of SCR and 02 pair of diode.
- ⇒ The load is bridge connected i.e. it is center tap betⁿ two pair of SCR.
- ⇒ There are also 02 pairs of diodes antiparally connected across the load for free wheeling purpose if the load is inductive or capacitive.
- ⇒ Separate, firing ckt and commutated ckt is required for pair of SCR.
- ⇒ As the load is resistive so there is no need of D₁, D₂ & D₃, D₄.

Operation

For conduction through load simultaneously or SCR is to fired.

At time $t = t_0$ gate pulse is given T_1 & T_4 hence the current I start flowing

$V_s^+ \rightarrow T_1 \rightarrow \text{load} \rightarrow T_4 \rightarrow V_s^-$ and the voltage V_0 seen across the load.

Both T_1 & T_4 conducts upto

$T = t_1$ i.e. $t_1 - t_0 = T/2$ i.e. half of time period.

So the opp wave form is given for a half cycle of frequency f .

At time $T = t_1$, T_1 & T_4 are forcibly commutated and T_2 & T_3 are fired by giving gate pulse.

Now current start flowing in the direction.


$V_s^+ \rightarrow T_3 \rightarrow \text{Load} \rightarrow T_2 \rightarrow V_s^-$

which is opposite direction of previous one by including the opp voltage V_0 appears across the load for time period $T = T/2$ and giving rise to opposite half cycle as that of previous.

T_1 conducts upto $T = t_2$ i.e.

$t_2 - t_1 = T/2$ and forcibly commutated T_2 & T_3 and the above cycle repeated further.

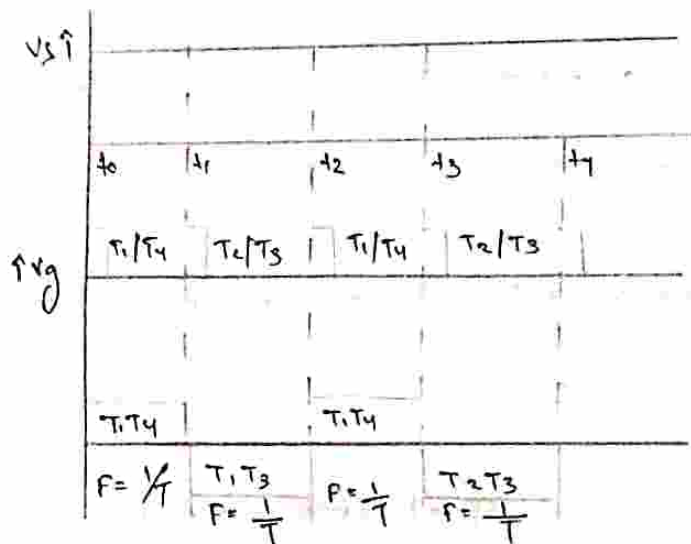As there is no inductive and capacitive load so D_1, D_2 & D_3, D_4 are not conduct.



CURRENT SOURCE INVERTER (CSI) :

Current source inverter (CSI) in which the i/p current is constant and adjustable.

The current feeding to the ckt by CSI does not depend upon nature of load.

The nature of the current is d.c which may be obtained from a a.c source having fixed voltage & connected by means of a bridge rectifier.


VOLTAGE SOURCE INVERTER (VSI)

→ In this type of inverter the i/p voltage is maintain constant whatever the load connected to the ckt.

⇒ Amplitude of voltage remain constant and does not depend upon the load.

→ So this may be obtained from battery and d.c shunt generator.

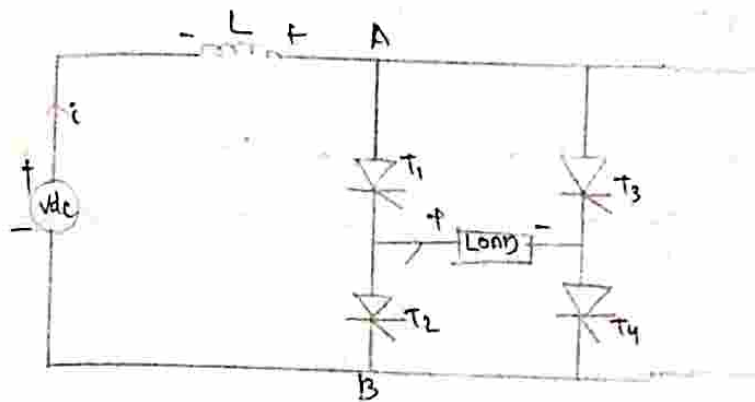1 ϕ current source inverter with ideal switches




Ckt Description

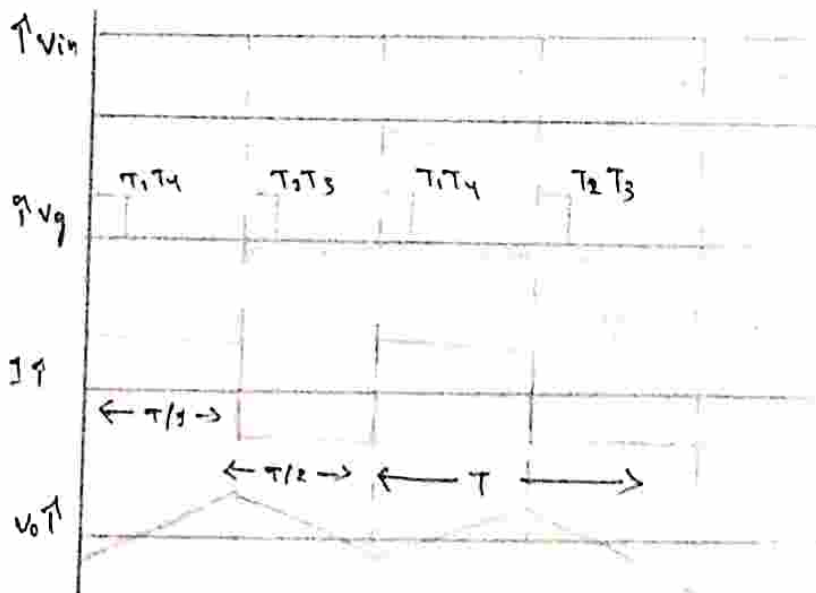- 1) The above ckt shows 1 ϕ CSI with ideal switches.
- 2) The ideal switches are T_1, T_2, T_3 & T_4 having zero commutation time.
- 3) The ckt consist of a voltage source (V_{dc}) which is series with the L .
- 4) The function of high impedance reactor (L) is to maintain current constant at i/p terminal of CSI.
- 5) In other word the voltage source (v) with inductor " L " feeding a d.c const current to CSI.
- 6) There are 02 branch where 4 ideal switches (T_1, T_2, T_3 & T_4) are connected in bridge manner and load is centre tap.

Operation


- When T_1 & T_4 are on the current i --- starts flowing through $+V_{dc} \rightarrow L \rightarrow T_1 \rightarrow \text{Load} \rightarrow T_4 \rightarrow -V_{dc}$ and o/p voltage v_i seen across load.
- After time $t = T/2$ ' T_1 ' & ' T_4 ' are automatically off and T_2 & T_3 are automatically on, giving rise opposite direction of load current. \therefore
- i.e. $+V_{dc} \rightarrow L \rightarrow T_3 \rightarrow \text{Load} \rightarrow T_2 \rightarrow -V_{dc}$
and -ve o/p voltage (-V) appears the load.
- Here the direction of current fed to CSI is always unidirectional.
- If V_{in} is the i/p voltage to CSI and average value of V_{in} is +ve then power flow is source to load or if it -ve then power flow is load to source which is known as regulation of power



1 ϕ Capacitor Commutated CSI with R-Load

NOTE:- Full wave Rectifier
frequency - 100 Hz
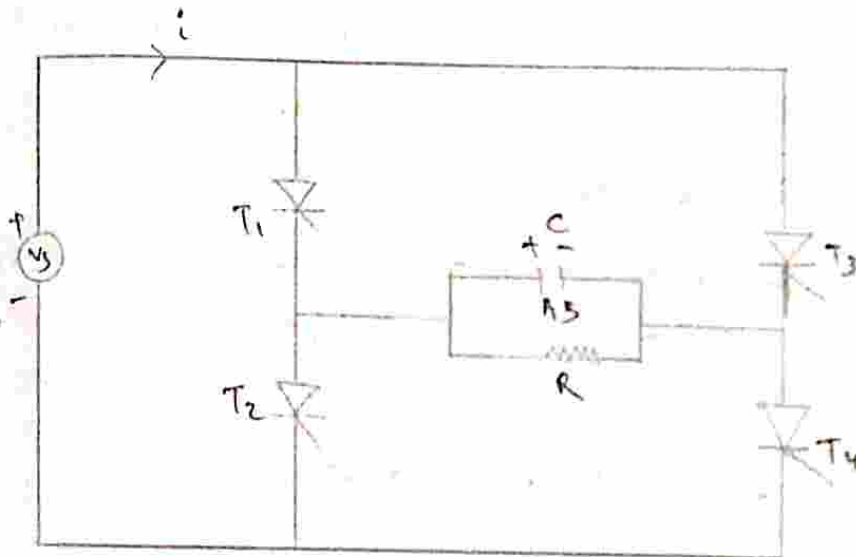
$$1/T_2 = \frac{2}{T} = 2 \times f = 2 \times 50 = 100 \text{ Hz}$$



1) The above circuit shows capacitor commutated 1 ϕ CSI.

2) Here a capacitor is connected across load resistance (R) which is identifying the capacitor commutated CSI.

3) The source connected to the circuit is a constant current delivering to the CSI but it is an adjustable source.

4) There are two pairs of SCR T₁T₄ & T₂T₃ which provides simultaneously the gate current for turn on.

5) A capacitor (C) is connected parallel with load resistance R which A-plate is -ve & B-plate is +ve.

Operation

⇒ At time $t=0$ T_1 & T_4 are on by giving gate pulse.

⇒ As capacitor plate - A -ve so current " i " starts flowing through.

$$V_s^+ \rightarrow T_1 \rightarrow R+C \rightarrow T_4 \rightarrow V_s^-$$

⇒ As a result capacitor charges to V_c which is at time $t = T/2$


⇒ As polarity is reversed and biased. The SCR in r/v biased so they are automatically turn off.

⇒ This need to turn on T_2 & T_3 fired simultaneously & load current " i " start flow through $+V_s \rightarrow T_3 \rightarrow R+C \rightarrow T_2 \rightarrow V_s^-$ and again charge up the capacitor a opposite voltage $-V_c$


⇒ Hence T_2 & T_3 automatically turn off after time $t = T$

⇒ In duration $0 < t < T/2$ T_1 & T_2 left to right through load in the time duration $T/2 < t < T$.

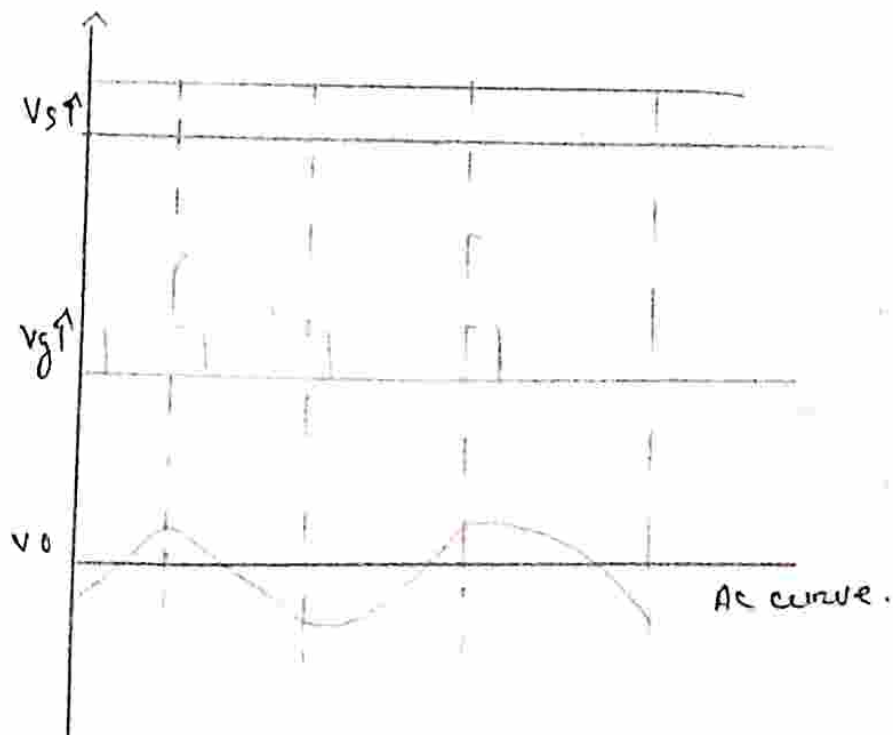T_1 & T_3 are conducts & load current " i " flow right to left hence the o/p is in alternating in nature.



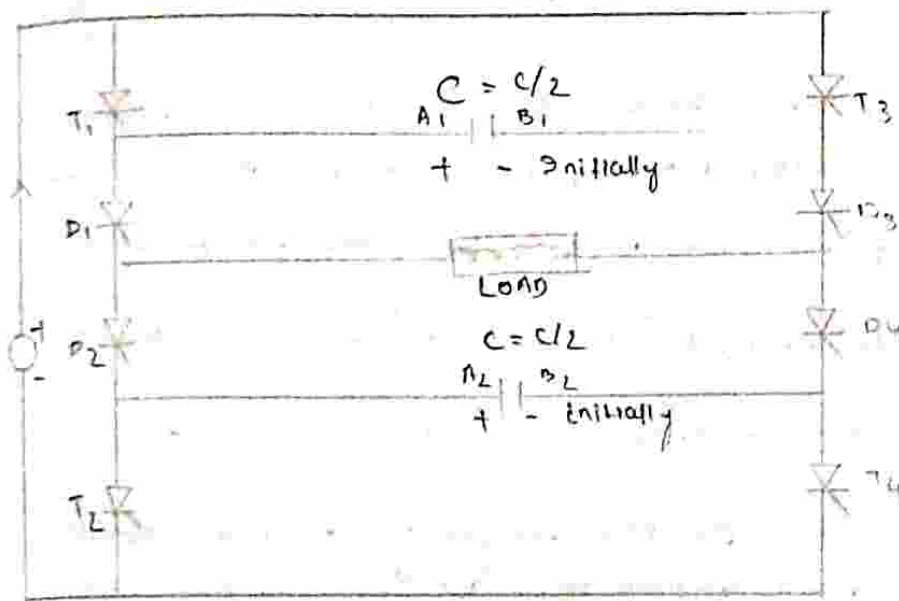Auto sequential Commutated inverter (ASCI) :-



The above ckt shows 1 ϕ auto sequential commutated inverter which is widely used in industries.

It is more popular than force commutated CSI.

Here a constant current source 'i' is feed to load 'L' through a bridge inverter ckt.

The SCR T_1, T_4 & T_2, T_3 are alternatively switch for getting a square wave.

There are 02 commutating capacitor C_1 & C_2 having capacitance $C/2$ connected lower half & upper half of the above fig.


There are 4 diodes D_1, D_3 avoided C_1 to discharge through L.

Similarly D_2, D_4 avoided C_2 to discharge through L.

Operation

- > At time $t=0$ T_3 & T_2 are conducts by giving gate pulse.
- > Hence 'i' start flowing $\cdot i \rightarrow T_3 \rightarrow C_1 \rightarrow D_1 \rightarrow L \rightarrow D_4 \rightarrow C_2 \rightarrow T_2 \rightarrow i'$
- And charge up the capacitor $V_{C1} = V_{C2} = +V_c/2$ with reverse in polarity of capacitor & T_2 & T_3 automatically turn off at time $t = T/2$
- > At time $t = T/2$ the T_1 & T_4 are 'on' by giving gate pulse
- > Again 'i' flowing in the direction $i \rightarrow T_1 \rightarrow C_1 \rightarrow D_3 \rightarrow L \rightarrow D_2 \rightarrow C_2 \rightarrow T_4$
- > And charge the capacitor C_1 & C_2 $V_{C1} = V_{C2} = -V_c/2$
- > Hence the current direction changes by the help of capacitor polarity automatically and o/p is in the form of A.C.
- > The o/p frequency can be varied by adjusting the triggering time of either T_1, T_4 or T_2, T_3

Wave form

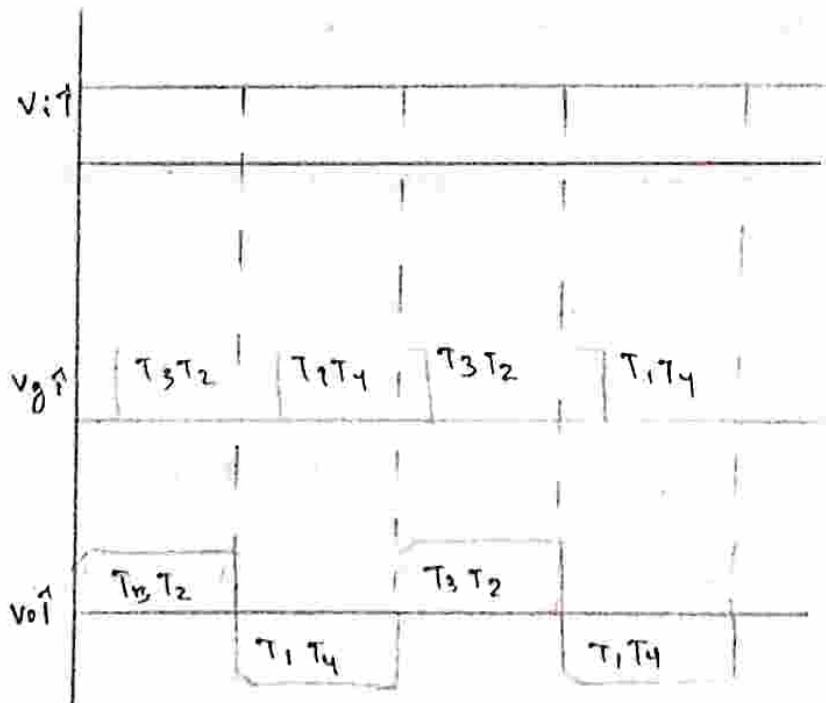

CHOPPER

is a static device.

D.C. CHOPPER

is a static device which convert fixed value of d.c. to variable value of d.c.

D.C. chopper is a nothing but A.C. T/A, i.e. it produced desired voltage at desired time.

So a d.c. chopper maybe either stepup or stepdown.

In d.c. chopper we required process commutation (Turn off)

Hence the type of chopper depend upon the nature of commutation.

Application of Chopper

Speed control of d.c. drives (Trainsif Trams)

Battery driven vehicles

Trolley car

Marine Hoists.


Advantages of Chopper

The voltage control ability of the chopper are smooth or the ckt of Chopper are smoothly operated.

High efficiency (o/p is high Losses is low)

1st response & regeneration capability.

Types of chopper.

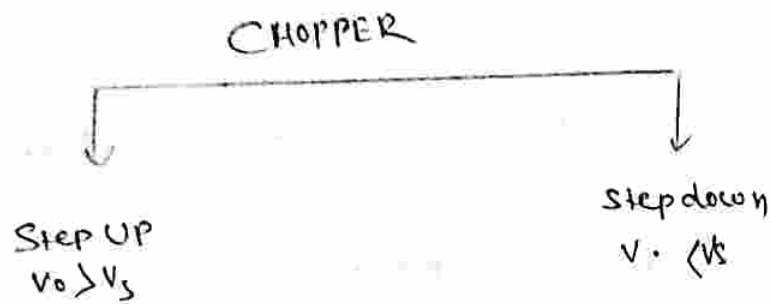


V_o = o/p voltage of chopper in d.c

V_s = D.C i/p supply voltage to chopper.

Principle of chopper


- ⇒ A chopper is a high speed ON-OFF semiconductor switch.
- ⇒ It connects & disconnects the load with source with very fast speed.
- ⇒ So generally we used power BJT, GTO, SCR & P-MOSFET.

Step down chopper { Buck chopper }

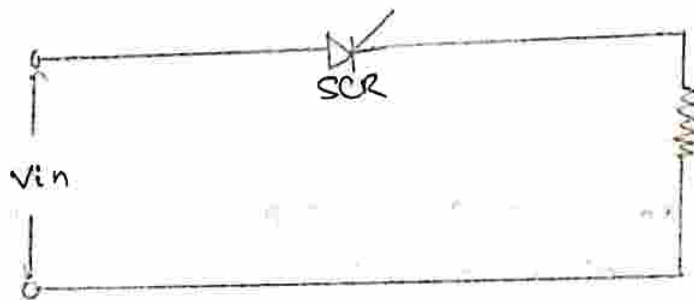

- ⇒ It is also known as Buck chopper.
- ⇒ It is a chopper in which V_o is less than V_{in} .
- ⇒ The operation of the ckt is such that when SCR is conducting.

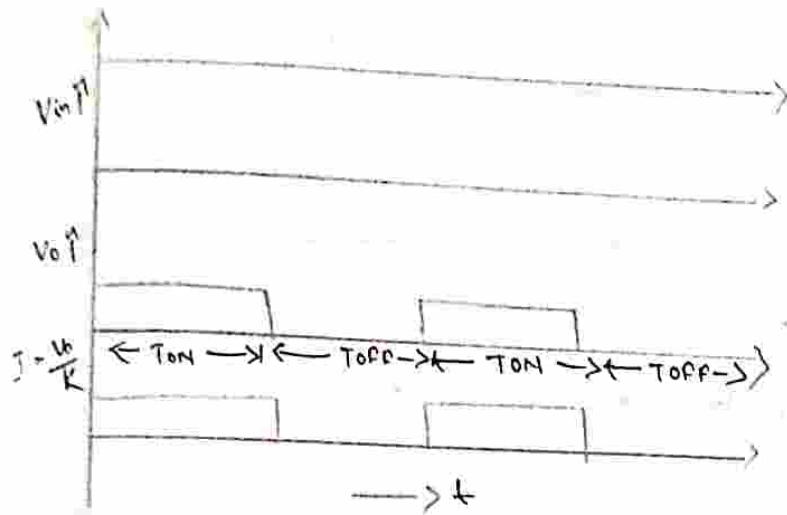Hence let T_{ON} represents "ON" time period of SCR where V_{in} is applied
 T_{OFF} represents "OFF" time of SCR



→ Here average value of i/p voltage is given greater than average value of o/p voltage.

∴ So $V_o (\text{avg}) = d \cdot V_{in} (\text{avg})$

where, $d = \text{duty cycle}$


$$d = \alpha = \frac{T_{ON}}{T} = \frac{T_{ON}}{T_{ON} + T_{OFF}}$$

where $T_{ON} < T$

Hence α is less than 1 ($\alpha < 1$)


∴ V_o is less than V_{in} ($V_o < V_{in}$)

Step up chopper { Boost chopper }

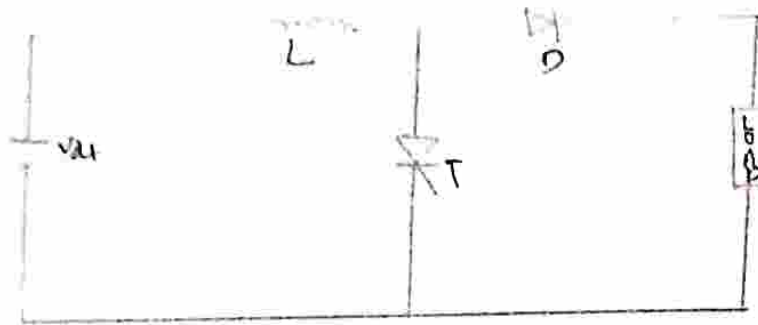

- ⇒ It is also known as Boost chopper.
- ⇒ The o/p voltage is greater than i/p voltage.


mode-I

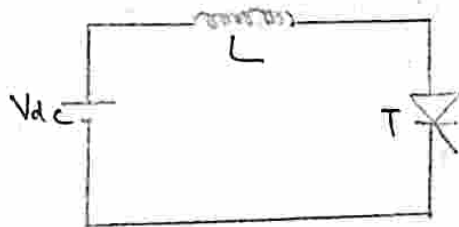

- ⇒ When SCR \$T\$ is on for the time period \$T_{ON}\$ the current from a constant voltage \$V_{dc}\$ is applied to inductor (\$L\$) & it store charges linearly to a value of \$V_L\$.
- ⇒ After time period \$T_{ON}\$ SCR turn off

mode-II

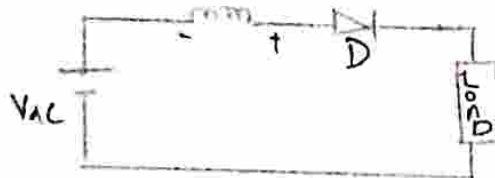- ⇒ When SCR \$T\$ is turn off the energy store by inductor is transfer to load through diode \$D\$.




Now the voltage $V_c + V_{dc}$ is applied to load during turn off

$V_c + V_{dc}$

As during turn on V_{dc} is applied to inductor & turn off $V_c + V_{dc}$ is applied to load ($V_{dc} = 0$ during T_{on})

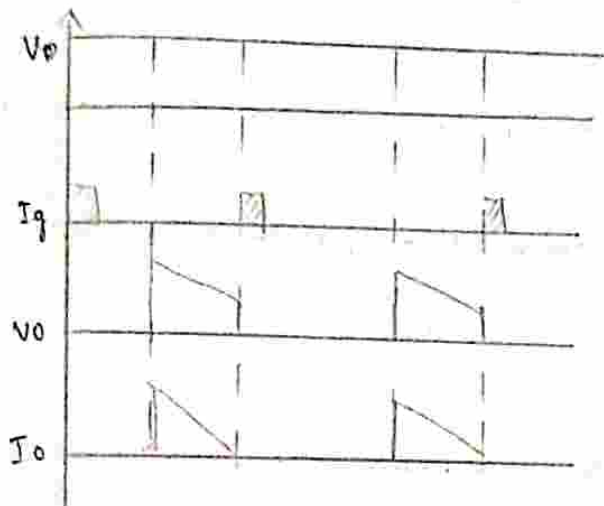Hence average o/p is greater than avg. i/p voltage




Classification chopper

According to the o/p voltage V_o & o/p current I_o the Choppers are work at different quadrants.

So this may be divided in to five sub category i.e.

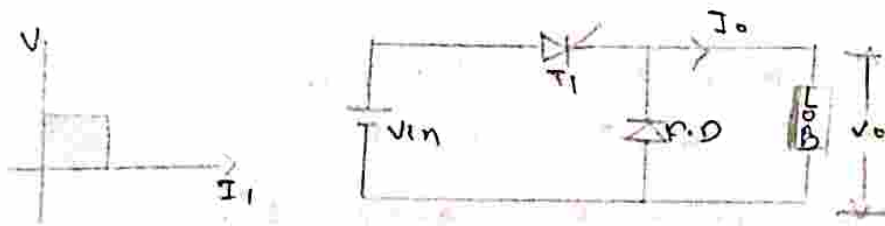
- (i) class-A / Type-A
- (ii) class-B / Type-B
- (iii) class-C / Type-C
- (iv) class-D / Type-D
- (v) class-E / Type-E

Class - A / Type - A : (Forward motoring)



- ⇒ This type of chopper give rise to 1st quadrant operation i.e. both V_o & I_o are +ve.
- ⇒ The above ckt contain a S.C.T., which is acts as a switch for load.
- ⇒ A free wheeling diode is connected antiparallel across the load.
- ⇒ The fixed d.c supply is given as i/p.
- ⇒ When T_1 is off then $V_o = 0$
Now the F.W.D is used for maintaining the load current I_o .
- ⇒ Hence a current I_o flows from source to load.
- ⇒ Hence the power applied to the load i.e. the average value of o/p power is less than i/p power & hence V_o is less than V_i
- ⇒ Here V_o & I_o are +ve i.e. (source to load) which is the 1st quadrant operation.
- ⇒ It is a step down chopper i.e. $V_o \text{ Avg} < V_{in} \text{ Avg}$

class-B / Type -B chopper.

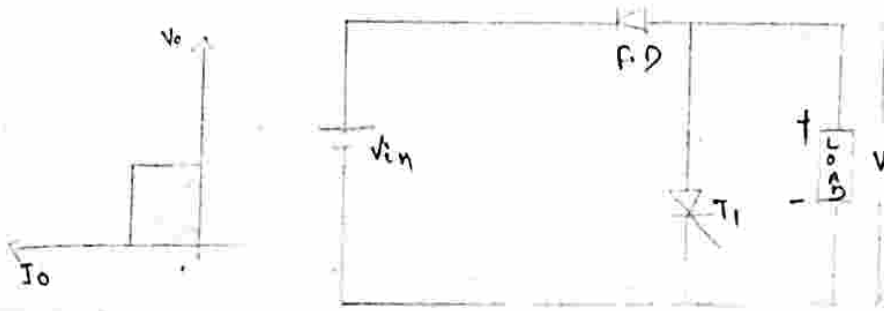

→ It is a 2nd quadrant chopper.


→ It is a step up chopper i.e. the power flow is always from load to source.

→ In the above ckt dig. T_1 is connected parallel across the load. The F.D. is connected series between load & source.

→ In the above ~~ckt~~ And the load polarity V_o is show above (General R.C. braking)

When D is ON T_1 is off the total voltage V_o across the load is equal to source voltage V_{in} i.e. $V_o = V_{in}$. And I_o flow from load to source ($-I_o$)

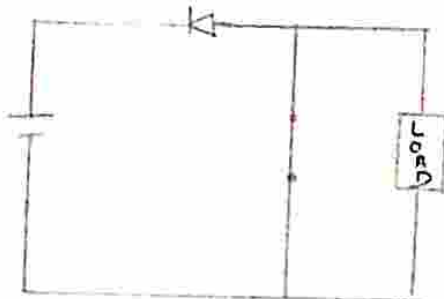→ when T_1 is ON $V_i = 0$ (i) and I_o continuous flowing from load through T_1 .




\Rightarrow Hence the average load voltage gain is less than the source voltage since v_o is +ve and I_o is -ve the power flow is allowed from load to source.

-) As the power flow is from load to source so it is known as step up chopper.
-) Reversal of power flow (source to load) possible if load is active an example of active load is d.c motor acting on Regenerating Breaking mode.

Note:-



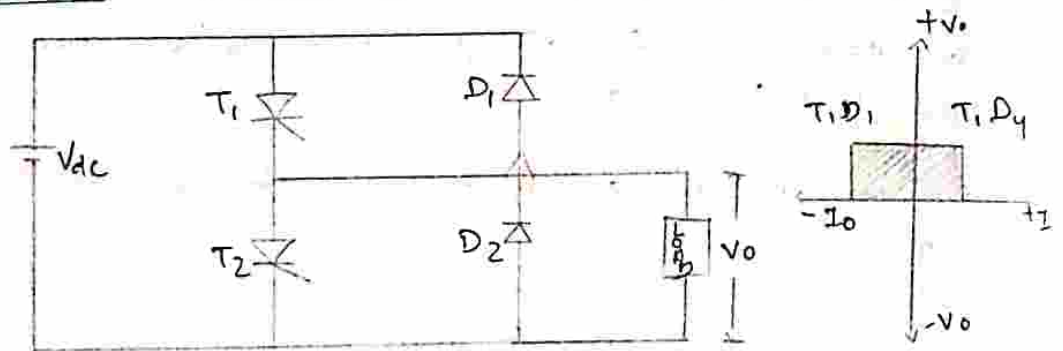Class-C (Type-c / Two Quadrant Class-A chopper



\Rightarrow In this type of chopper is the combination of class-A + class-B type chopper i.e power flow may be from source to load or from load to source.

\Rightarrow So this type of chopper is used where P/w motoring + Regenerating Breaking is required.

\Rightarrow When T_1 ON during ON periods to current start flowing from source towards load + current direction is shown in the above.

After turn off the T_1 the load free wheels through D_2 maintaining current direction is same.



Hence power flow is from source to load, which gives rise to 1st quadrant operation.

When due to any reason V_o is greater than V_{dc} ($V_o > V_{dc}$ or V_{in})

then any device among D_1 & T_2 used for return back power to load to source.

Hence the above CKT used in both f/w motoring as well as regenerative braking.

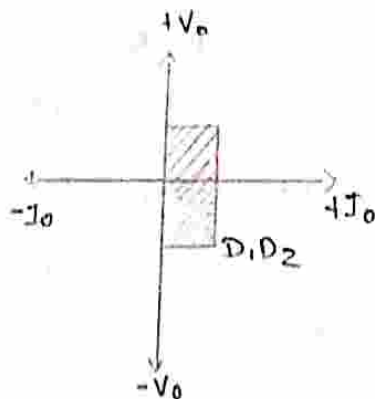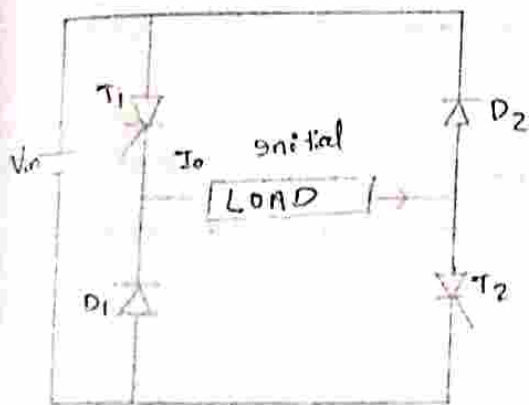Class-D / Type-D / Two quadrant class-B Type chopper



Here this CKT gives 02 quadrant operation i.e. quadrant 1 & 4 i.e. f/w motoring & reverse motoring.


Here 02 SCR T_1 & T_2 & 02 diode D_1 & D_2 which are anti parallel connected in bridge manner the load is centre tap.

When T_1 & T_2 are ON load voltage V_o is +ve & I_o also +ve

When T_1, T_2 off but D_1, D_2 conducts at that time the V_o across load is reversed i.e. -ve but current flow is same.

Hence we say that here power flow is both +ve & -ve (Source to load or load to source).

Class-E / Type-E / 4 quadrant chopper

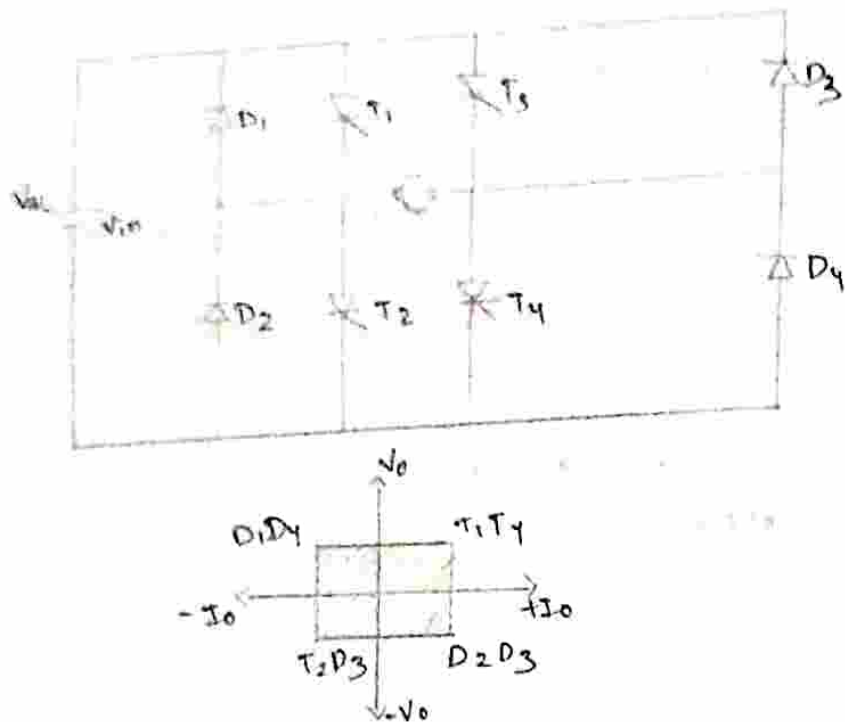

→ This CKT is used for 4 quadrant operation i.e 1, 2, 3 & 4 i.e
 4 no. Q_2 operation is possible.

→ Hence the CKT designed for f/w motoring, regenerative
 braking reverse motoring + reverse regenerative braking.

1st quadrant:

When T_1 & T_4 is ON the V_o & I_o are +ve gives rise to 1st
 quadrant operation which indicates f/w motoring.

2nd quadrant:

When D_1 & D_4 are conducts the current direction reversed i.e
 (- I_o), but V_o polarity is same V_o is +ve which 2nd quadrant operation
 This indicate regenerative braking (CP power in greater than
 supply power).

3rd quadrant :

when T_2 & T_3 are conducts voltage applied across the load is reversed i.e. V_o is -ve & also the current direction is change, hence I_o is -ve which gives rise to 3rd quadrant operation, hence indicate reverse motoring.

4th quadrant

when D_2 & D_3 are conducts the voltage polarity is -ve but current polarity is +ve hence power flow is -ve that indicates reverse regenerative braking.

CYCLE CONVERTER

A device which converts ^{fixed} ~~field~~ voltage, fixed frequency of AC supply to variable voltage.

Variable frequency at one stage of conversion known as cycle converter.

We also convert fixed voltage fixed frequency into variable voltage, variable frequency by rectifier - inverter ckt which is two-stage conversion but cycle converter converts it one-stage.

Application


- ① Induction heating
- ② Static VAR (volt Ampere Reactive generation.)
- ③ Speed control of A.C drives.

Disadvantages



- (i) As the o/p is variable frequency hence o/p voltage contains harmonics.
- (ii) Smooth variation of o/p frequency is not possible.
- (iii) A complicated firing ckt is required.

Types

CYCLO CONVERTER

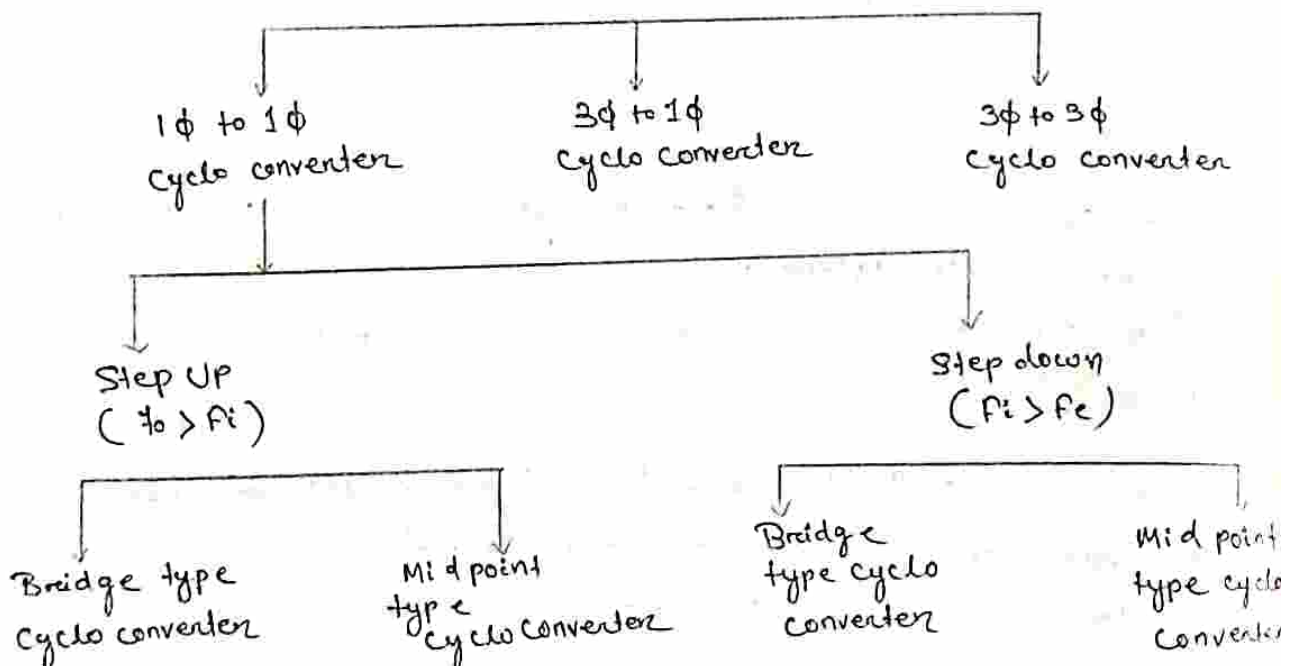

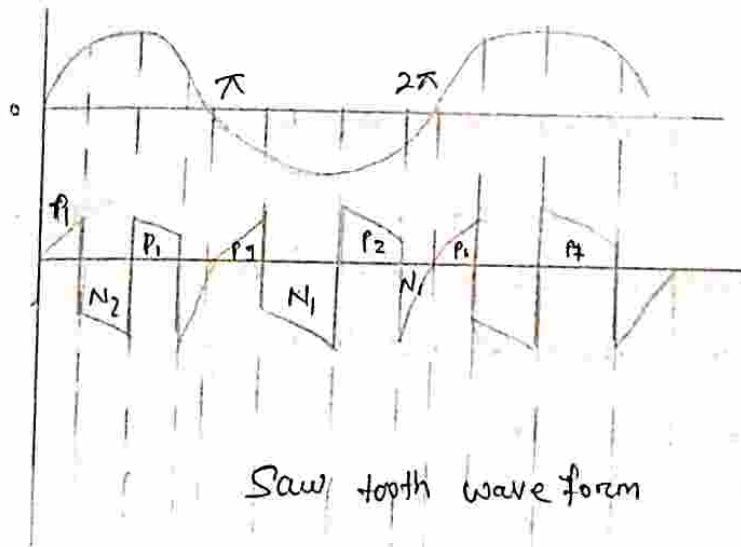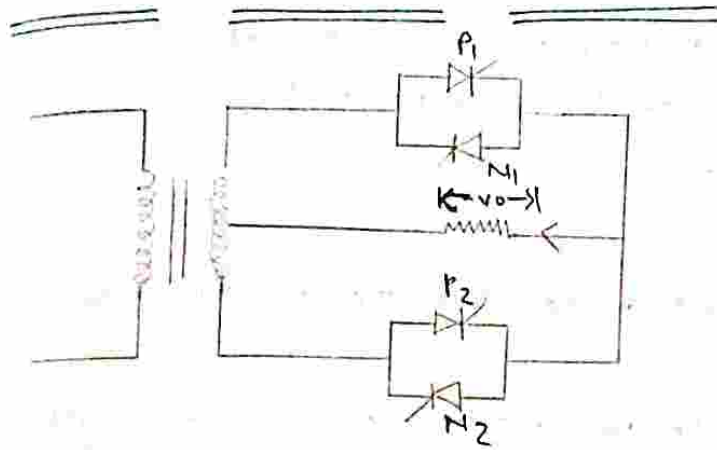Mid point type step up cyclo converter with R-load



Ckt description

The ckt represent of mid point type step up cyclo converter with R-load i.e o/p frequency (f_o) is greater than i/p frequency (f_i).

The ckt consist of 2 sets of antiparallel SCR's which have Centre tap T/P which is connected by means of load.

The ckt required firing ckt as well as forcibly commuted ckt.

The SCR P_1 & P_2 constitute the group but N_1 & N_2 constitute -ve group.

Operation

Mode-I ($0 < \omega t < \pi$)

→ During +ve half cycle P_1 & N_2 are f/w biased at $\omega t = 0$, P_1 trigger by giving gate pulse for giving +ve half cycle & turn off at $\omega t = \omega t_1$ & gate pulse given to N_2 .

⇒ Hence N_2 give -ve half cycle then the above repeated for $\omega t = \omega t_2, \omega t_3, \omega t_4$.

→ Result one +ve half cycle split into 2 no. of complete cycle.


Mode-II ($\pi < \omega t < 2\pi$)


⇒ During -ve half cycle N_1 & P_2 are f/w biased.

→ The similar process is repeated i.e. P_2-N_1, P_2-N_1 "ON" which again split -ve half cycle into 02 no. of complete cycle.

⇒ So the o/p frequency is 4 times of i/p frequency.

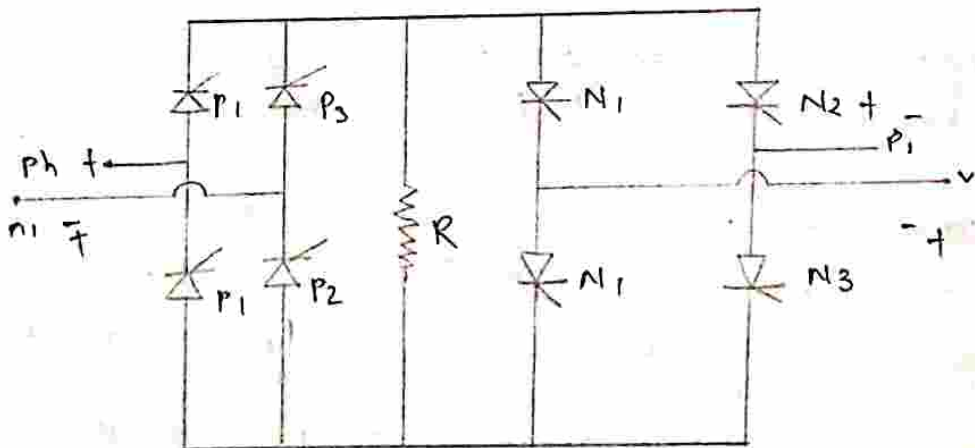Bridge type step up cyclo converter with R-Load



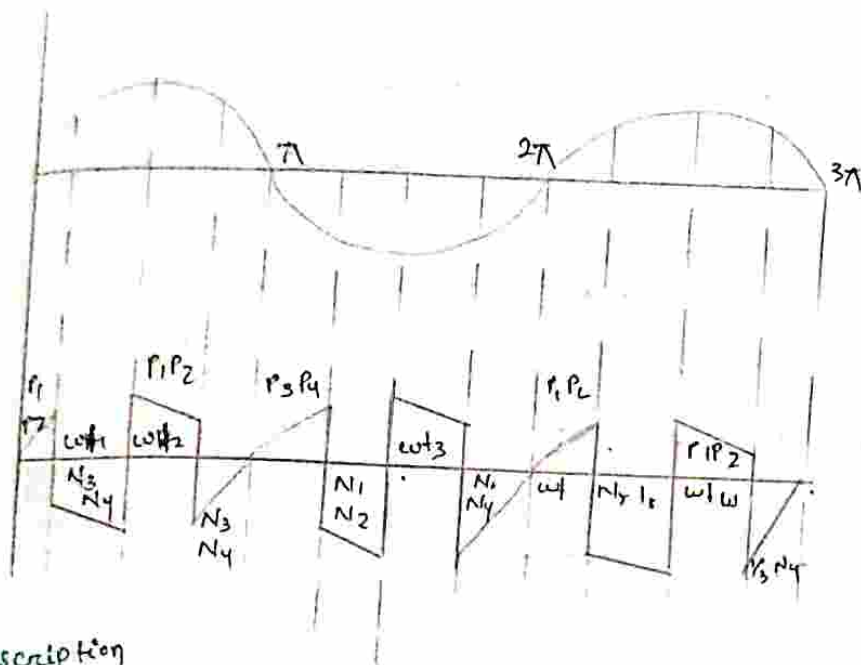

ckt description

- Here there are 4 nos of SCR's constitute the group as well as -ve group i.e P₁P₂ P₃P₄ and give rise to the half cycle & N₁N₂N₃N₄ are gives rise to -ve half cycle.
- here again 02 mode of operation.

Operation

Mode-I ($0 < \omega t < \pi$)

During the half cycle P₁P₂ & N₃N₄ are F/W biased.

During 0 to ωt_1 , P₁ P₂ fires and conducts at $\omega t = \omega t_1$, P₁P₂ off & N₃N₄ are fires & conducts upto $\omega t_1 \rightarrow \omega t_2$.



At P₁P₂ gives ~~rise~~ rise to the half cycle then N₃N₄ gives rise to -ve half cycle.

This cycle is repeated for $\omega t = \omega t_2$ & $\omega t = \omega t_3$ of the wave from shown in the above.

Mode-II ($\pi < \omega t < 2\pi$)

-) During this half cycle $P_3 P_4$ + $N_1 N_2$ are F/W biased.
-) $P_3 P_4$ gives rise to +ve half cycle + $N_1 N_2$ gives rise to -ve half cycle.
-) The triggering of $P_3 P_4 \rightarrow N_1 N_2 \rightarrow P_3 P_4 \rightarrow N_1 N_2$ repeated for -ve half cycle + the wave form when in the above fig.
-) Hence one cycle of i/p will be converted into 4 no. of o/p cycle hence frequency step up.

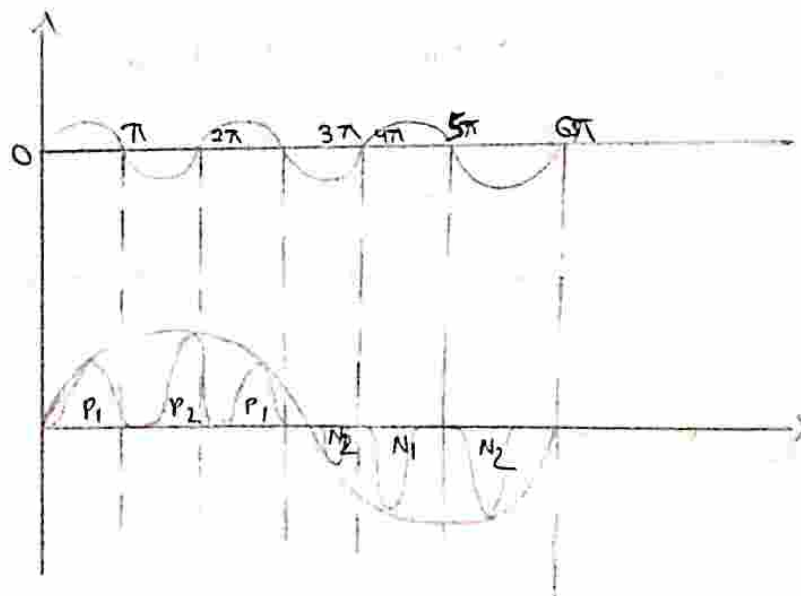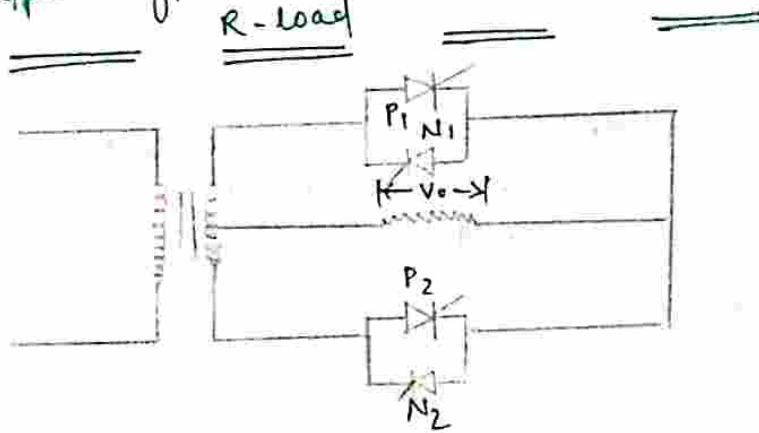Midpoint type step down cycle converter with R-load



Ckt description

- The ckt represent of midpoint type stepdown cycle converter with R-load i.e o/p frequency (f_o) is less than i/p frequency (f_i)
- The ckt consist of 2 sets of antiparallel SCR's which have centre tap T/A which is connected by means of load.
- The ckt required firing ckt as well as forcibly commutated ckt
- The SCR P_1 & P_2 constitute +ve group but N_1 & N_2 constitute -ve group.

Mode-I ($0 < \omega t < 3\pi$)

- As we know that during +ve half cycle of i/p P_1 & N_2 are f/w biased and during -ve half cycle P_2 & N_1 f/w biased.

→ During $0 \rightarrow \pi$, P_1 "ON" & N_2 "ON" & again $2\pi \rightarrow 3\pi$, P_2 "ON" & N_1 "ON".

→ The o/p of 3 half cycle combinly gives one +ve half cycle.

Mode-II ($3\pi < \omega t < 6\pi$)

→ In this mode we turn on only "ve" groups of SCR.

→ During $3\pi \rightarrow 4\pi$, N_2 "ON" & $4\pi \rightarrow 5\pi$, N_1 "ON" & $5\pi \rightarrow 6\pi$, N_2 "ON".


→ If we combine the o/p of above half cycle it gives rise a one -ve half cycle.

→ Hence we step down the frequency.

THYRISTOR APPLICATIONS

SMPS :

- ① It stands for switch mode power supply.
- ② It is based on a d.c chopper with a rectifier & possible transform o/p.
- ③ It is used for medium to high power application & also used for power supply to computer.
- ④ It is prefer because of small size & low weight.
- ⑤ In general rectifier operates on 50 Hz or 60 Hz A.C supply and in order to obtain negligible ripple & disturbance (frequency) in o/p of rectifier the filter ckt is required and the ckt is become quite large & losses is high, hence efficiency is less.
- ⑥ To avoid this bulky ckt smps is develop.
- ⑦ ON/OFF switch vary rapidly A.C ripple rises this is now checked by L & C. Such are used for operation power electronic devices power MOSFET, power, power BJT etc.
- ⑧ Due to this SMPS became small in size & less weighty.
- ⑨ It is develop by NASA, for use in its space vehicle.

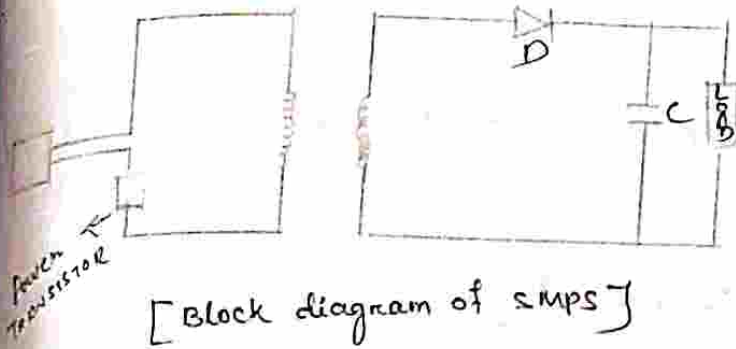

- (i) Here A.C supply is give to a Thyristor rectifier which is used for control d.c o/p.
- (ii) The AC supply is given by inverter ckt which is acts as inverter as well as filter.
- (iii) Now the ripples checked by own ckt filter ~~and~~ elements like L & C.
- (iv) The d.c o/p is applied power transistor for amplification at desired value.
- (v) Now the d.c o/p regulated by T/F connected in the amplification ckt and applied to load.
- (vi) Hence SMPS perform 4 no. of operation i.e.
 - (i) Rectification
 - (ii) Controlling
 - (iii) Transformation
 - (iv) Filtration.


UPS !

- Stand for uninterruptible power supply.
- UPS mean there is no interruption (failure) of power supply to the equipment or device.
- Compensation during failure of grid.


Uses :

- Hospital I.C.U
- Air lines and Railway reservation.
- Computer system.
- Process control in plant.
(Different s/w control like P.L.C & Scada)
- UPS convert bad quality commercial signal or supply of const. voltage & constant frequency.

Types

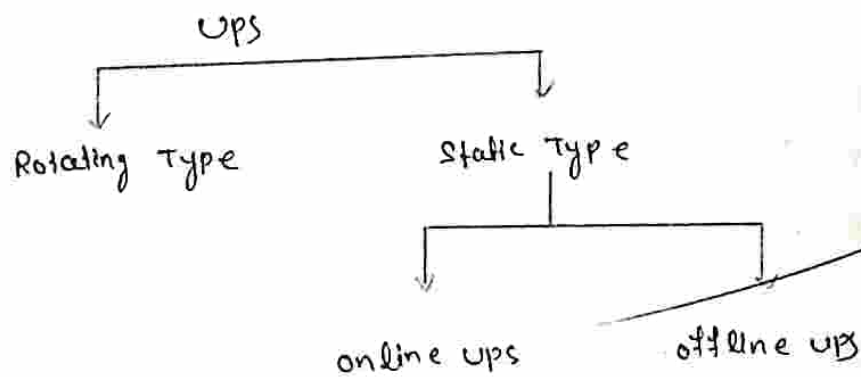


OFF LINE UPS

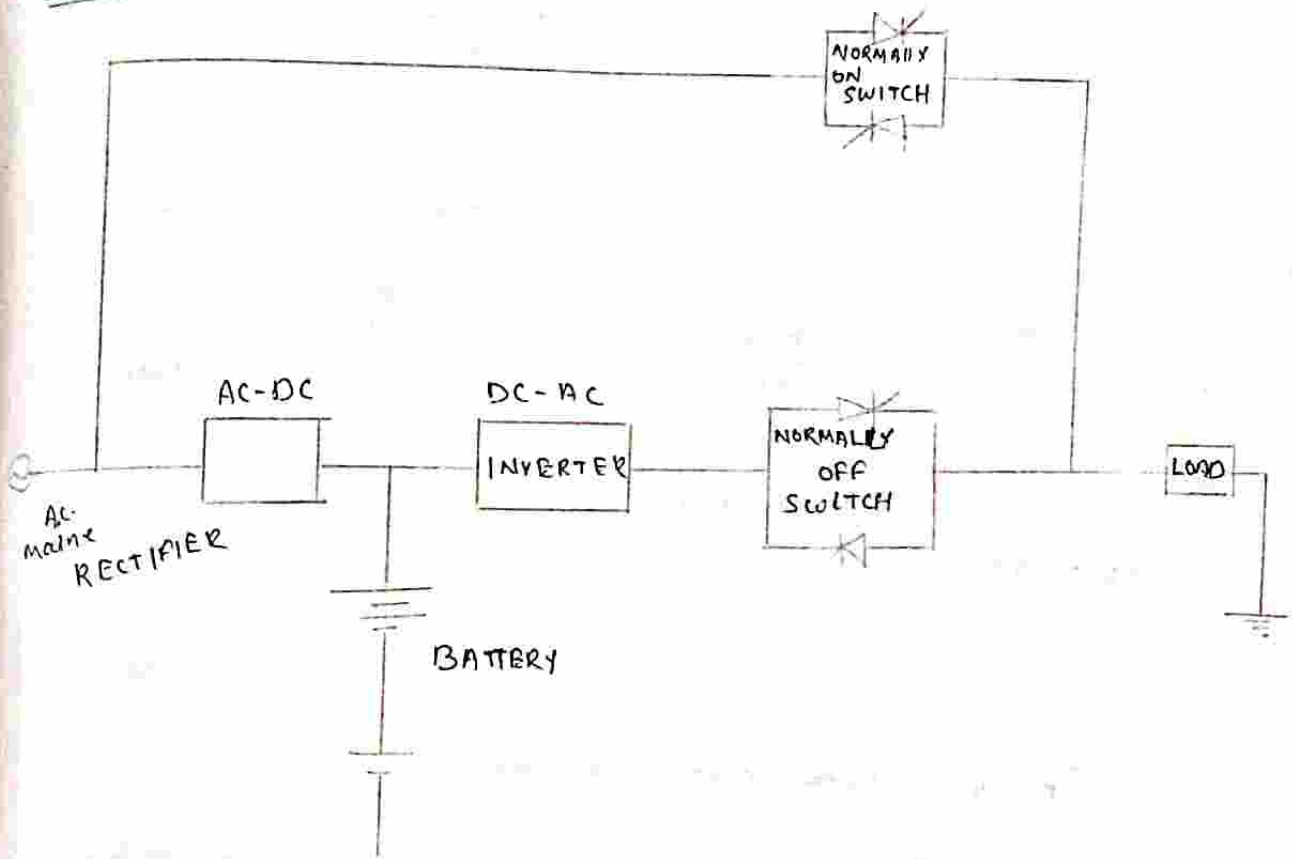

[BLOCK DIAGRAM OF OFF LINE UPS]

- This type of UPS the converter ckt is normally in off state so it is named as off line UPS.
- The load is fed by direct main through normally ON static switches.
- During n.c power available rectifier convert A.C to D.C of charge up the battery.
- When there is a power failure low the battery supply the store power to inverter which convert d.c to A.C.
- During power switches which is off position become 'on' automatically & A.C supply is fed to load.

* ON LINE UPS :

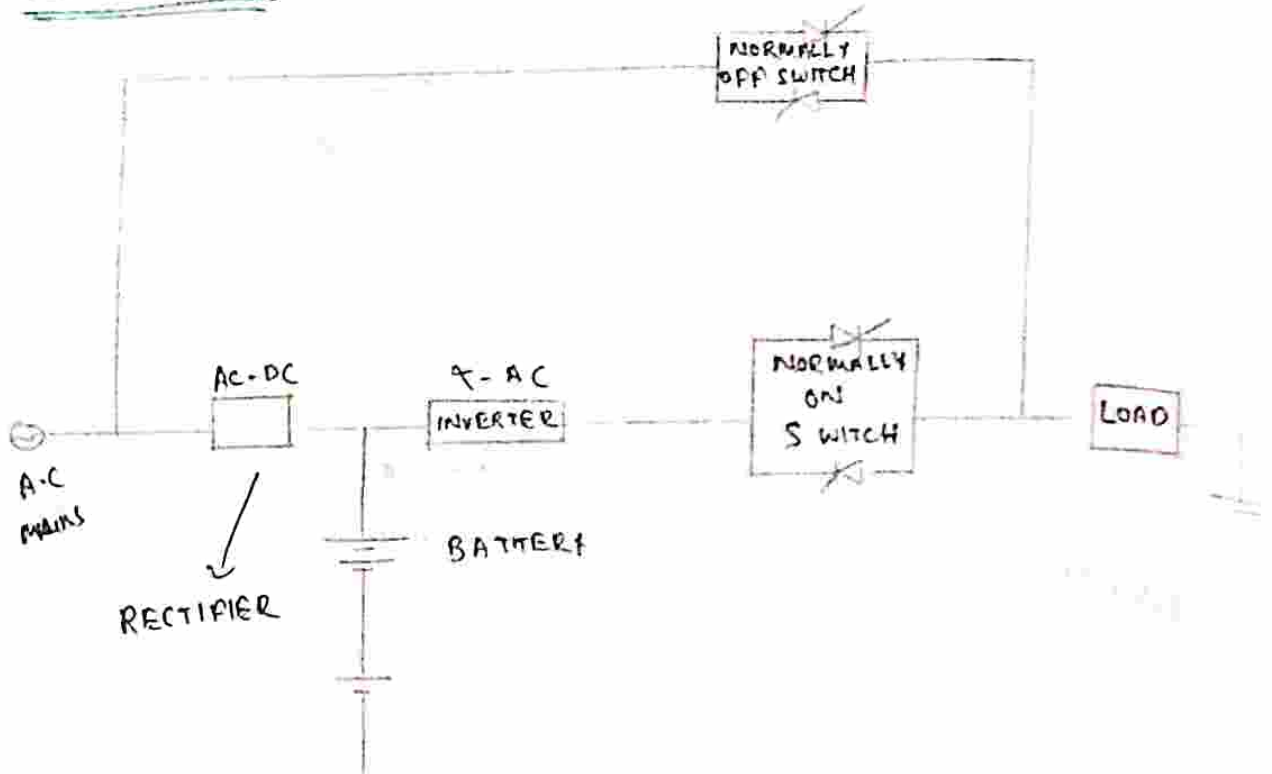

[BLOCK DIAGRAM OF ON LINE UPS]

- (i) In this type of UPS the inverter ckt is normally on by static switch. Continuous i/p is fed to load by inverter ckt so it is named as online UPS.
- (ii) When AC supply is available it is rectified by rectifier. a.c to d.c is fed to both for charging battery and inverter ckt.
- (iii) The inverter inverting by D.c to A.c and by the help normally on static switch to load.
- (iv) During power failure battery by necessary power to the inverter & by the help normally on static switch fed to load.

There is a fault occurs inverter ckt then normally on switch became off and normally off switch become on. direct A.c power is fed to load.

POWER SEMICONDUCTOR DEVICES AND ITS PROTECTION

Power Transistors :

The transistor which operate as high voltage & high current known as power transistor which is available recent years.

① In power electronics the power transistor are used as a switch.

② The transistor are operate f/w biased.

③ Hence during this mode the voltage drop is minimum i.e. 0.5V to 0.8V

④ For faster turn on & keep conducting mode of power transistor access base current as well as continuous Base current is required.





⑤ If Base current is removed the transistor is turn off & the value of base collector voltage predict about the time of turn ON.

⑥ There are 3 types.

1- Power BJT

2- Power MOSFET

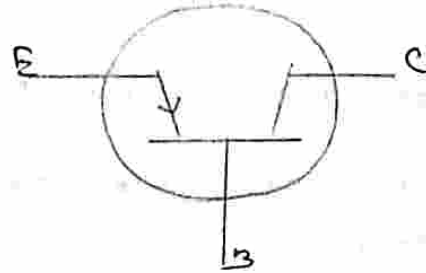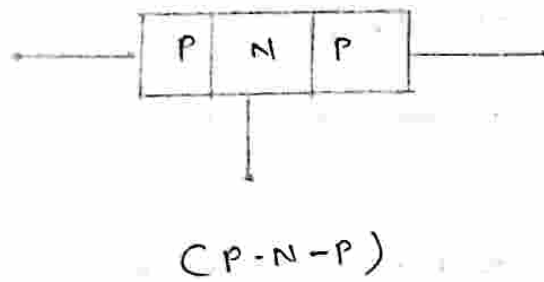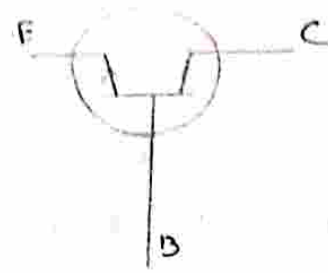
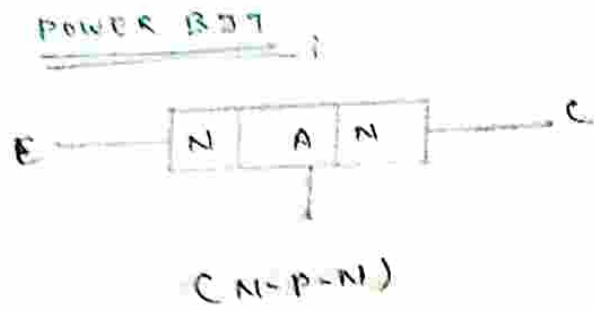
3- IGBT (Insulated Gate Bipolar Transistor)



- ① Power BJT is a 3 layer 3 terminal 2 junction semiconductor devices,
- ② It is known as Bipolar junction transistor because there are 02 types of bipolar are involved for current flow i.e. holes & electron.


Steady state characteristic :-

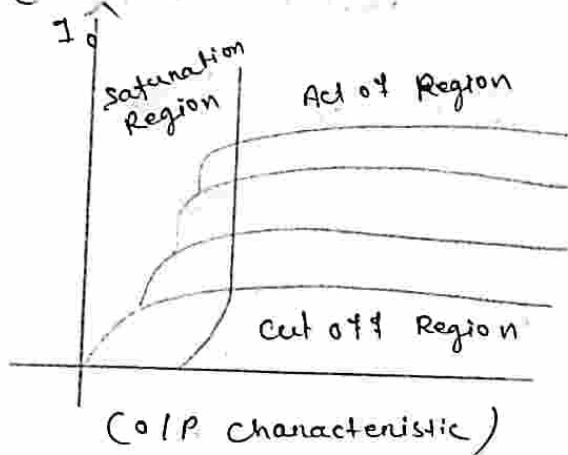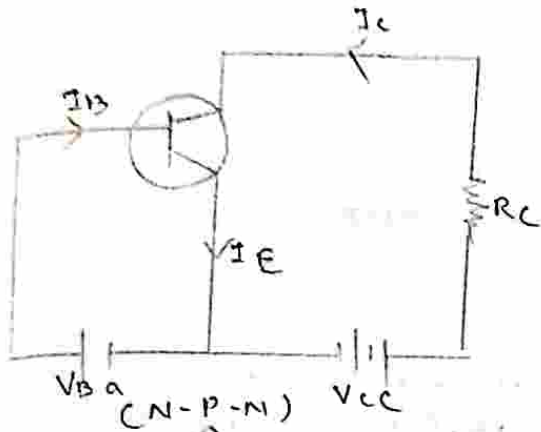- > The 3 possible configurations i.e. Common Emitter, Common Base, Common Collector.
- > The common emitter configuration is widely used for switching application.




I/P characteristic :

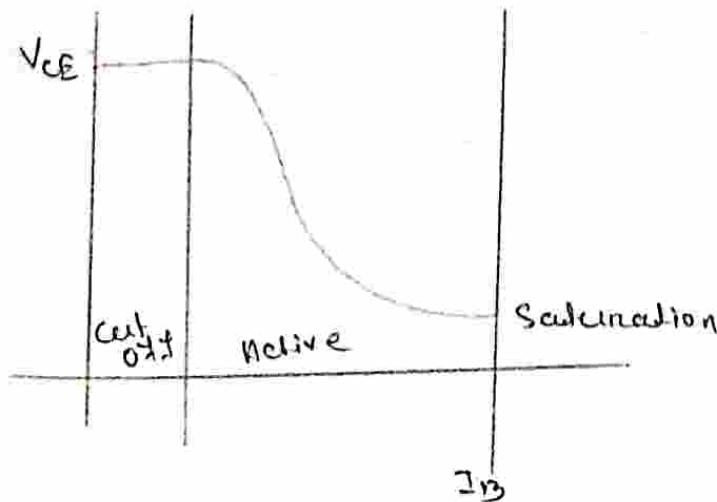- 1) The i/p characteristic of BJT is obtained by plotting the graph between I_B & V_{BE} .
- 2) This characteristic is same as that of diode i.e. if forward voltage increases then base current increases. Hence the curve form is like a hyperbola.




Types:

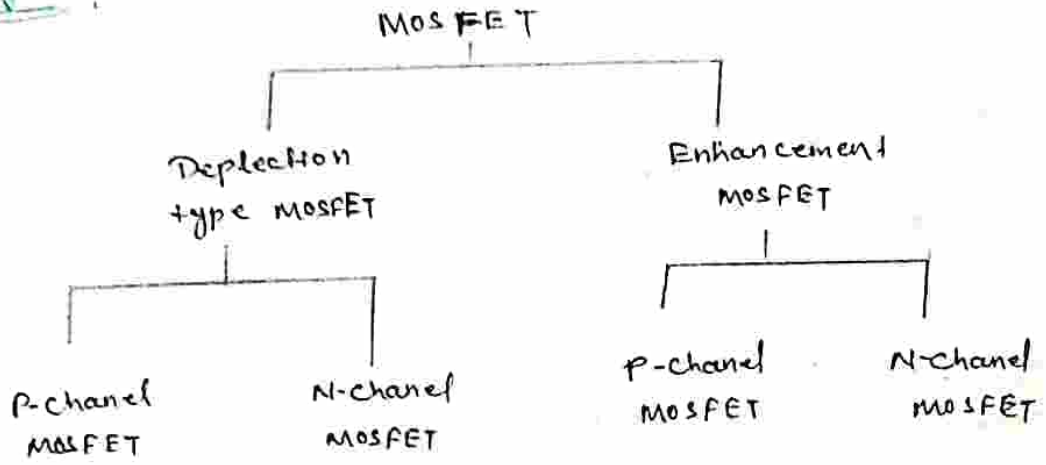


The power MOSFET is generally enhancement type

Construction:

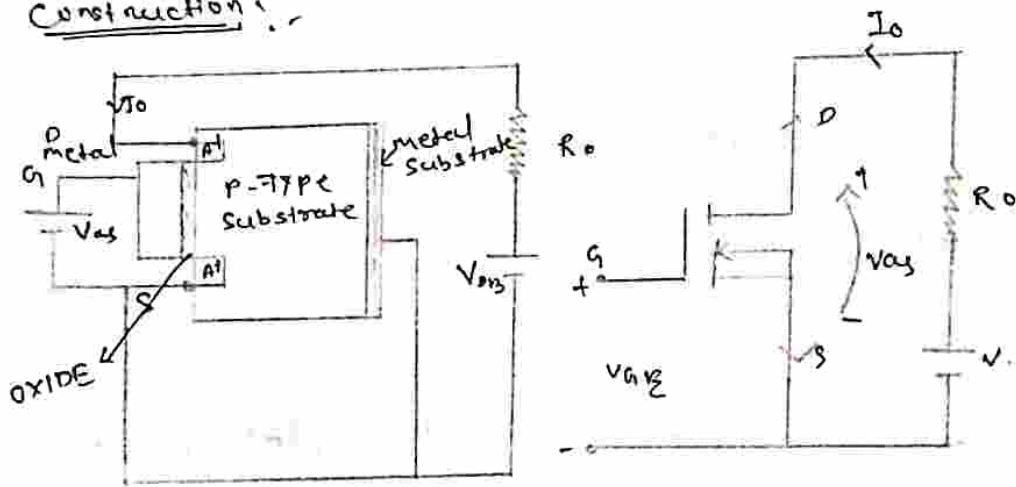

[n-channel type MOSFET]

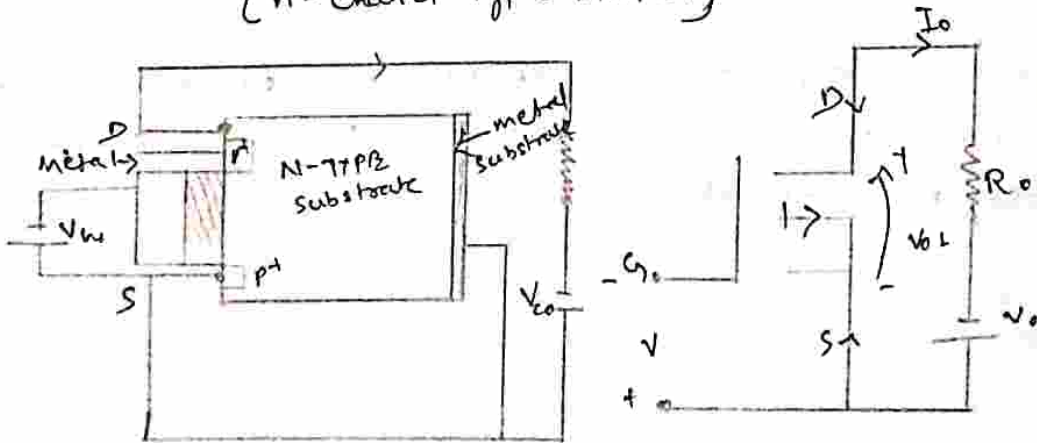


• N channel Enhancement type MOSFET having p-type substrate where we found higher mobility e^{-} 's.

• In p-channel Enhancement type MOSFET having n-type substrate where we found as mobility of e^{-} 's

• Due to higher mobility of electron N-channel Enhancement type MOSFET is used.

o/p characteristic :

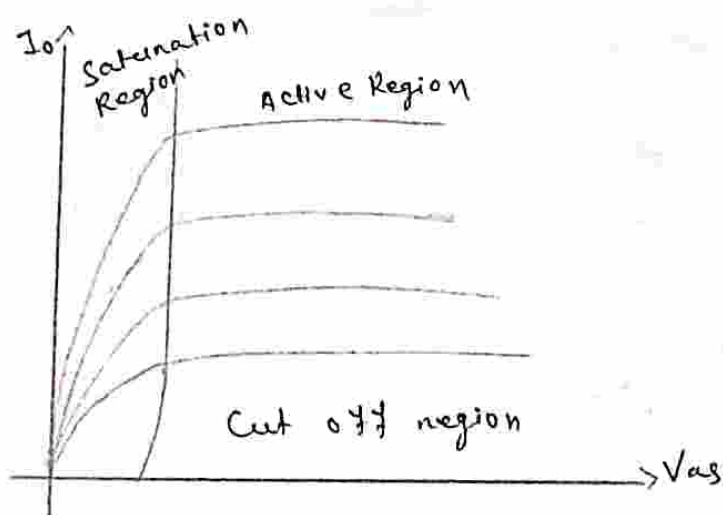• The o/p characteristic is drawn betⁿ V_{GS} & I_D



we also found 3 region particular value of V_{GS} .

Cutoff Region ($V_{GS} \leq V_T$)


V_T = Threshold voltage of V_{GS} i.e. min^m. value of V_{GS} below which MOSFET does not turn on.

Saturation Region ($V_{GS} \geq V_{GS} - V_T$)

Active Region ($V_{GS} \leq V_{GS} - V_T$)

IGBT

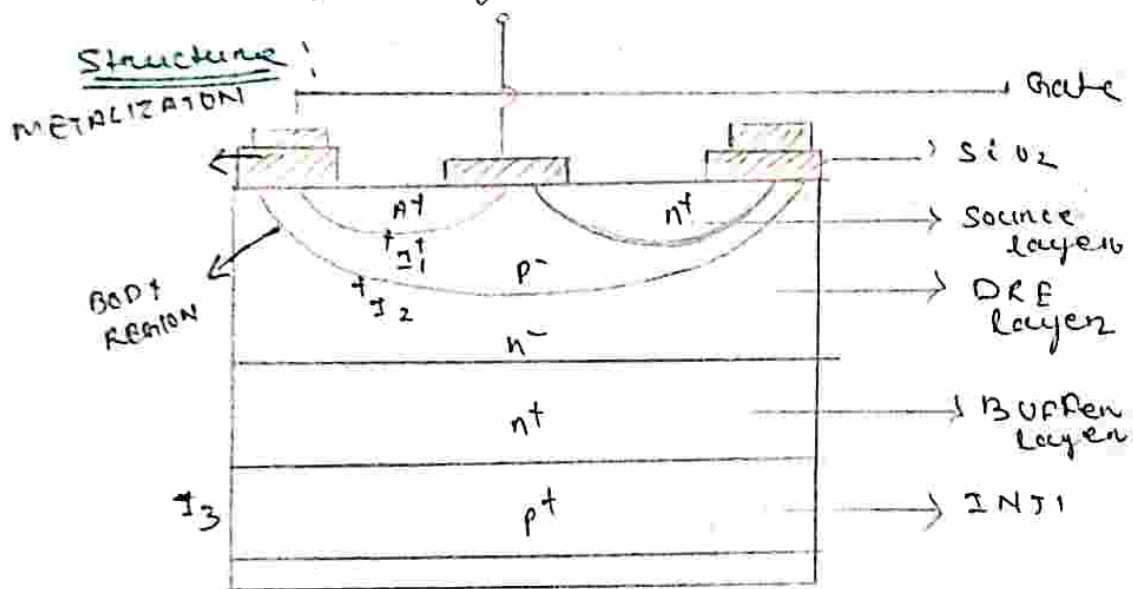- > It stand for Insulated Gate Bipolar Junction Transistor.
- > By combining the characteristic of power MOSFET & power BJT.
- > IGBT is develop i.e. It has a characteristic of voltage control similar to power MOSFET & current source similar to power BJT.
- > Hence IGBT is a voltage control current source.
- > It has significantly greater turn off time, than power MOSFET.




- > The above fig show vertical crosssection of n-channel IGBT.
- > Hence the n-layer is used for majority charge carrier which maximum the current source.
- > This will reduce the resistance offer to the current flow & hence the n-state power loss taking place in the device.
- > The IGBT is also used highly integrated Gate-Source structure in order to reduce the possible to source/emitter current crowding.

When difference in the structure MOSFET as compare to that of MOSFET is the existence of p^+ for that forms drain of the IGBT.


It is also possible to make channel IGBT by changing the doping type in each of the layer of the device.

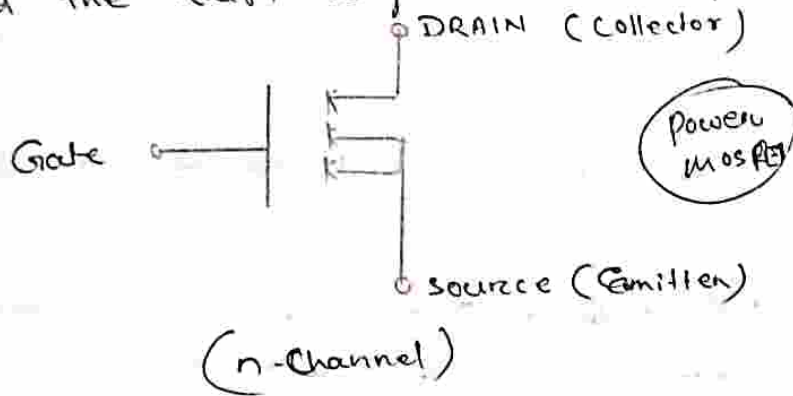The n^+ buffer layer bet p^+ drain layer & n^+ drift layer is not essential for the operation of IGBT but it insulated the drift layer + drain layer (p^+).




It is a 3 terminal devices Gate, Source & Drain.

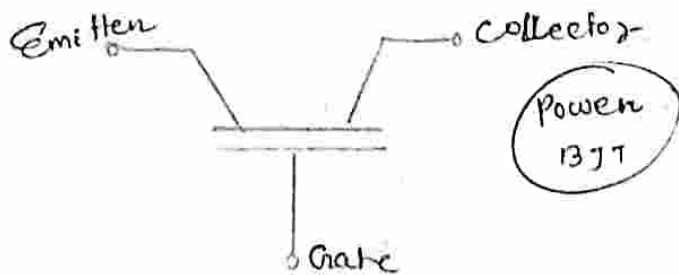In p -channel IGBT the direction of arrow head could be reversed.



The above 02 symbol are represent as power MOSFET + power BJT

V-I characteristics

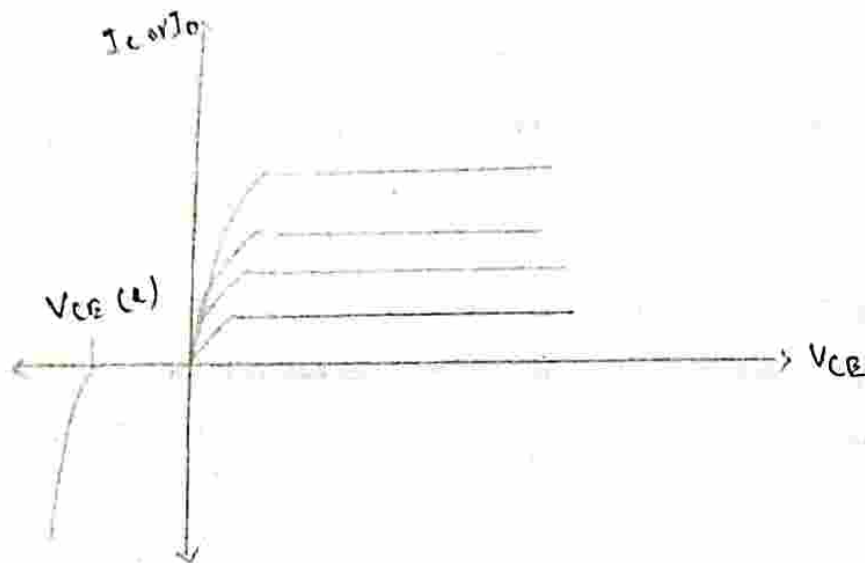


- > When there is no voltage applied to the Gate the IGBT is in off state.
- > In this state the current I_o or I_c is equal to zero & voltage across IGBT is equal to zero & voltage across IGBT is same as source voltage.
- > In ON state the voltage IGBT is equal to zero.
- => V-I characteristic the in current increase with increase in gate to source voltage for the V_{gs} & the breakdown occur when voltage is $-V_{ce(R)}$ & P/W
Breakdown occur when the voltage is $V_{ce(C)}$

Hence voltage is in belⁿ

$$V_{ce(R)} < V_{ce} < V_{ce(C)}$$

BUCK-BOOST CONVERTER :

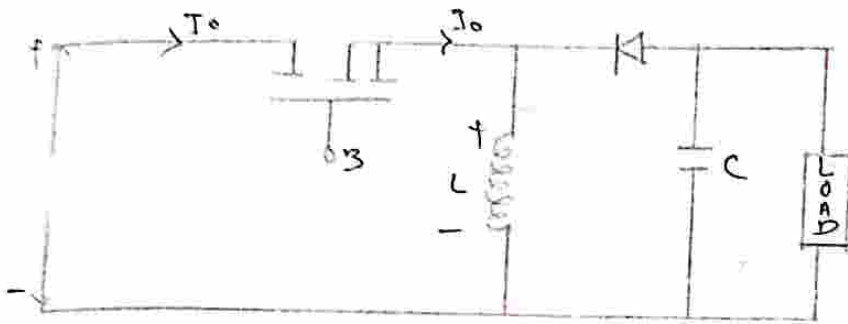


- As the name indicates the Buck-Boost Converter cascading of 2 converter one is step down other is step up.
- The main application of such a circuit or converter is in regulating the d.c power supply.
- Here in -ve polarity o/p may be desired of i/p voltage & the o/p voltage can be either higher or lower than the i/p voltage.
- When the power MOSFET is switched on the supply current flows through the path $E_{dc}^+ \rightarrow M \rightarrow L \rightarrow E_{dc}^-$ (M - MOSFET)

Construction :

- A power diode is a 2 terminal 2 layer one junction device.
- Here the symbol is a diode with a circle which represents power diode.
- The p-layer acts as anode while the n-layer acts as cathode.

V-I Characteristics (Power diode)

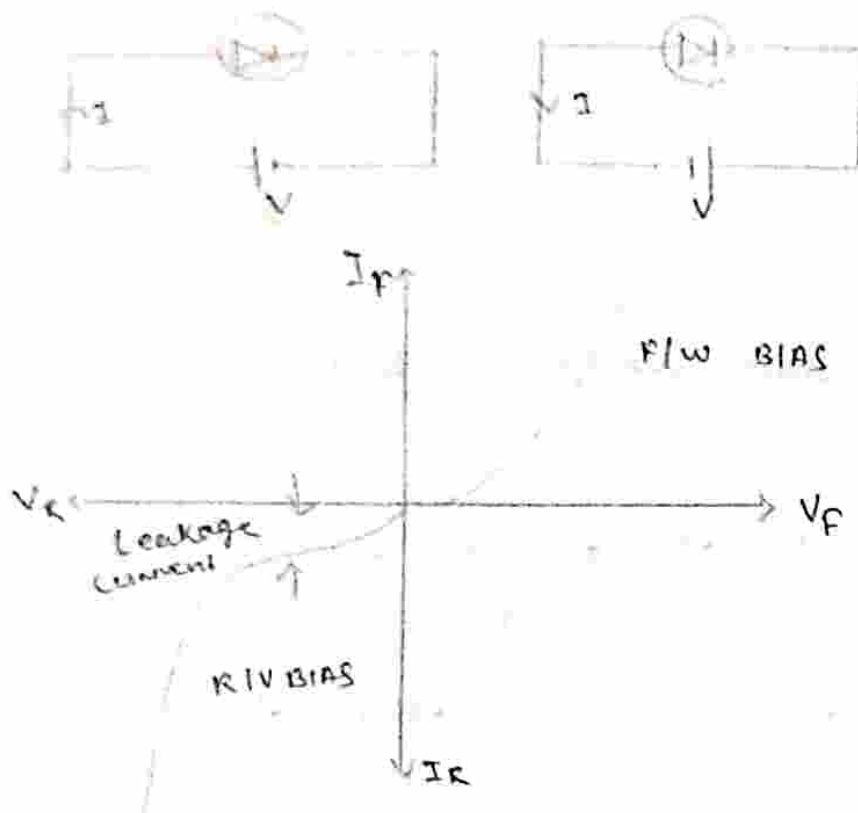

- V-I characteristic of a power diode is the curve betⁿ voltage across the junction & the CKT current.
- voltage is taken in x-axis & current is taken in y-axis.
- When the anode is +ve w.r.t cathode then the diode is known as F/W biased.
- In this condⁿ the diode conduction from anode to cathode.
- Hence the voltage drop across diode is very less or negligible.
- This voltage drop is dependanty depends up manufacturing technology as well as the metal which is used.
- So the voltage & current graph is gradually increases the voltage is increases.
- When anode is -ve w.r.t cathode then the Condⁿ is known as reverse biased Condⁿ.

reverse biased condⁿ a small reverse current (leakage current) in the range of milli ampere flow in reverse direction.



Hence the inductor 'L' stores the energy during the turn on period hence 'L' stores the energy during turn on.

When m is switch off the inductor current tends to decrease as a result the polarity of the EMF induced in 'L' is reversed & thus inductor (L) discharge the energy through load. The current flow $L^+ \rightarrow \text{load} \rightarrow 0 \rightarrow L^-$.

The ckt acts as step up or step down depending upon the turn on time.

Hence capacitor is used as filter ckt.

Power Diode

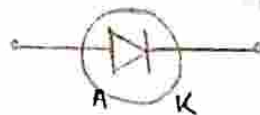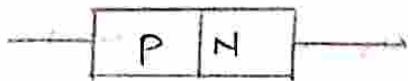

As we know that Diode is an electronic device which is used as a switch for turn on or off an electronics ckt.

Similarly in the power ckt power diodes are used which act as a switch to perform various functions these are as follows:

(A) Rectification

(B) Free wheeling in switching regulator.

(C) Energy transfer betⁿ components

(D) Voltage Isolation. (Distinguish betⁿ source voltage to load voltage).

(E) Energy feed back from load to power source.

The reverse voltage increases with increase in leakage current of reverse voltage is so high an avalanche breakdown of junction is occurs as a result reverse current increases rapidly which is shown in the above graph.

⇒ The voltage at which r/v break down occur is known as reverse breakdown voltage which is depends upon manufacturing technology as well as nature of materials.

⇒ So Power diodes mostly used as an ideal switch in a Power ext in general practice.

* Differentiate betⁿ

Power BJT

- ① Power BJT is a Bipolar device depends upon holes and electrons.
- ② It is current control device o/p current + voltage is the function of i/p.
- ③ The i/p impedance is high in the range of $k\Omega$.
- ④ Switching frequency is low in the range of KHz.
- ⑤ It is available at high power rating.
- ⑥ It is lower thermal stability.
- ⑦ More noising

Power MOSFET

- ① Power MOSFET is a Unipolar device, which charge flow is depends upon either holes or electron.
- ② It is voltage control device.
- ③ The i/p impedance is very high in the range of $M\Omega$.
- ④ Switching frequency is high in the range of MHz.
- ⑤ It is available at low power rating.
- ⑥ It is better thermal stability.
- ⑦ Less noising.

Aski's Desk
12.01.22